



Kontrollskrivning i HE1027 Ellära
Måndag 2 februari 2020, kl. 8:00 – 10:00

Ansvarig lärare: Maksims Kornevs

Ansvarig examinerator: Elias Said

Hjälpmedel: Endast utdelat formelblad samt miniräknare.

För godkänt krävs 5 poäng av 9 möjliga poäng. Godkänd kontrollskrivning ger bonus enligt kurs PM.

Fullständiga lösningar skall presenteras på alla uppgifter.


Börja varje ny uppgift på ett nytt blad, detta gör att rättningen blir säkrare. Skriv endast på en sida av papperet. Skriv namn och personnummer på varje blad. Inlämnade uppgifter skall markeras med kryss på omslaget.

Uppgift 1 [1p]


Bestäm spänningsfallet V_a och ange dess polaritet.

Determine the voltage for V_a and indicate its polarity.

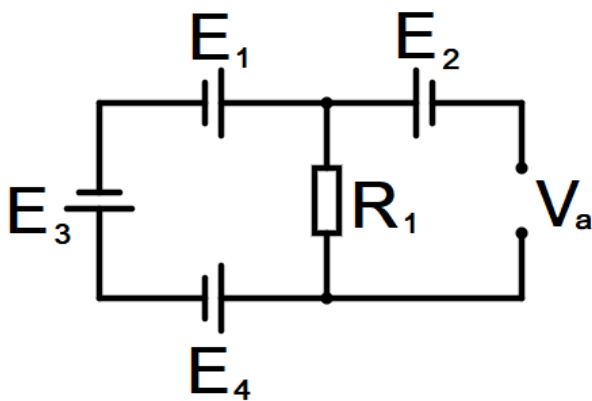$E_1=10V$, $E_2=5V$, $E_3=2V$ och $E_4=5V$




Uppgift 2 [2p]

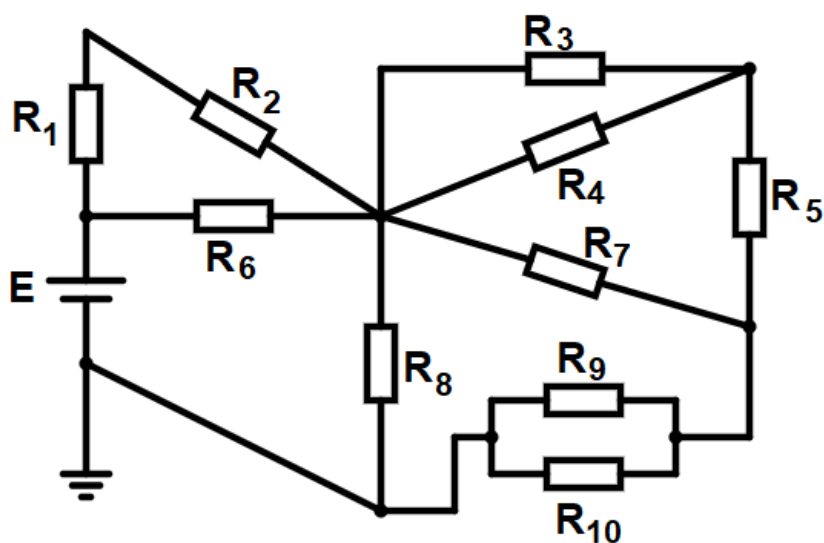

Fyll i tabellen. Fill the table.

	E	R1	R2	R3	R4	R5	R6	R7	R8	R9	R10
V (V)	27										
I (A)											
R (Ω)		7	5	2	2	7	6	8	8	10	15


Uppgift 3 [2p]

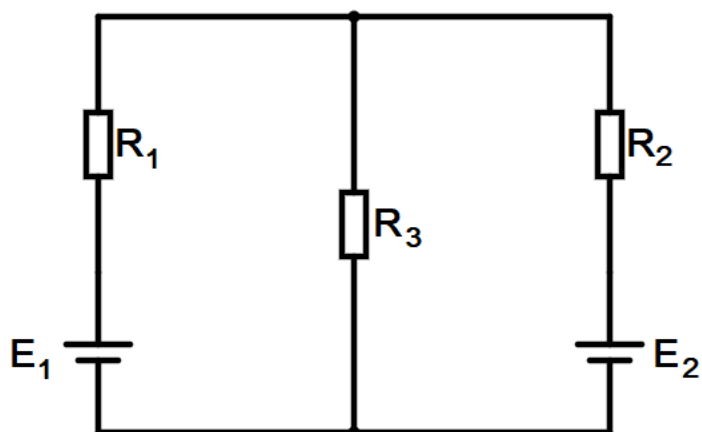

Fyll i tabellen. Fill the table.

	R1	R2	R3	E1	E2
V (V)				1	2
I (A)					
R (Ω)	1	2	3		


Uppgift 4 [2p]

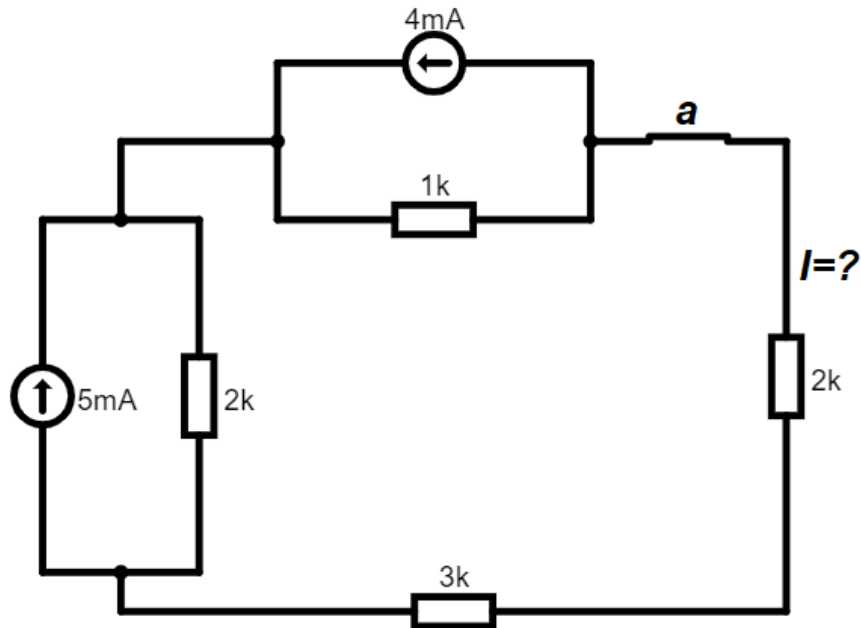

Bestäm strömmen I och ange dess riktning. Var ska man sätta jordpunkten så att det inte påverkar nätverket? Hur ström och spänning över motstånd kommer att förändras om omkopplare a skulle vara öppen?

Find current I and its direction. Where to put the ground to not affect the network? How current and voltage across resistors will change if switch a would be open?

Uppgift 4 [2p]

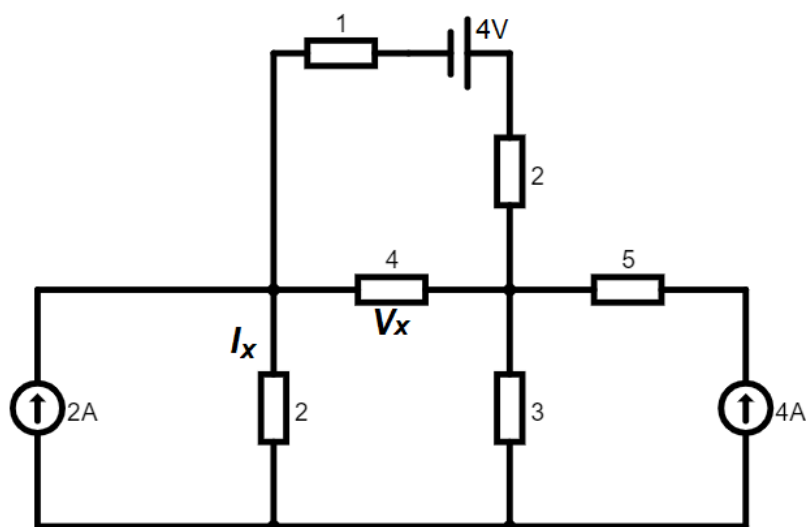


Bestäm strömmen I_x och spänningsfallet V_x (markerade i kretsen).

Find current I_x and voltage V_x .

Uppgift 1

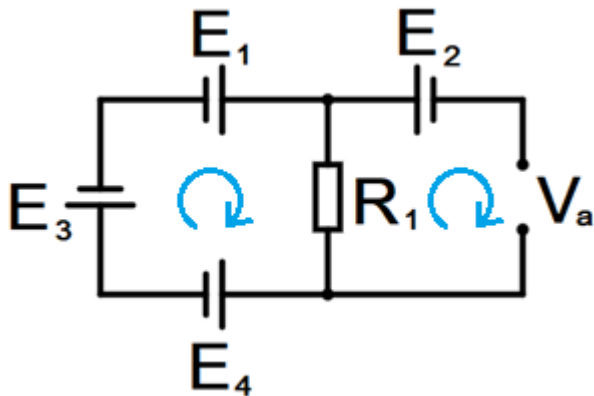Apply Kirchhoff's voltage law for both loops:



The first loop:

$$-E_3 + E_1 - V_{R1} - E_4 = 0$$

$$-2 + 10 - V_{R1} - 5 = 0$$

$$3 - V_{R1} = 0$$

$$V_{R1} = -3V$$

The second loop:

$$-R_1 - R_2 + V_2 = 0$$

$$-(-3) - 5 + V_2 = 0$$

$$3 - 5 + V_2 = 0$$

$$V_2 = -2V$$

Answer: voltage V_a is 2V and it goes 'up' towards E_2

Uppgift 2

Start by replacing pairs of resistors in series or in parallel:

$$R_a = R_1 + R_2 = 7 + 5 = 12\Omega$$

$$R_b = R_a // R_6 = (12 * 6) / (12 + 6) = 4\Omega$$

$$R_c = R_3 // R_4 = (2 * 2) / (2 + 2) = 1\Omega$$

$$R_d = R_c + R_5 = 1 + 7 = 8\Omega$$

$$R_e = R_d // R_7 = (8 * 8) / (8 + 8) = 4\Omega$$

$$R_f = R_9 // R_{10} = (10 * 15) / (10 + 15) = 6\Omega$$

$$R_g = R_e + R_f = 4 + 6 = 10\Omega$$

$$R_h = R_g // R_8 = (10 * 8) / (10 + 8) = 4,444\Omega$$

$$R_{Total} = R_b + R_h = 4 + 4,444 = 8,444\Omega$$

$$I_{Source} = E / R_{Total} = 27 / 8,444 = 3,197A$$

$$R_{Total} = R_b + R_h \rightarrow I_b = I_h = I_{Source} = 3,197A$$

$$V_b = I_b * R_b = 3,197 * 4 = 12,788V$$

$$V_h = 3,197 \cdot 4,444 = 14,207V$$

$$R_h = R_g // R_8 \rightarrow V_g = V_8 = V_h = 14,207V$$

$$I_g = V_g / R_g = 14,207 / 10 = 1,421A$$

$$I_8 = 14,207 / 8 = 1,776A$$

$$R_g = R_e + R_f \rightarrow I_e = I_f = 1,421A$$

$$V_e = I_e \cdot R_e = 1,421 \cdot 4 = 5,684V$$

$$V_f = 1,421 \cdot 6 = 8,526V$$

$$R_f = R_9 // R_{10} \rightarrow V_9 = V_{10} = 8,526V$$

$$I_9 = V_9 / R_9 = 8,526 / 10 = 0,853A$$

$$I_{10} = 8,526 / 15 = 0,568A$$

$$R_e = R_d // R_7 \rightarrow V_d = V_7 = 5,684V$$

$$I_d = V_d / R_d = 5,684 / 8 = 0,711A$$

$$I_7 = 5,684 / 8 = 0,711A$$

$$R_d = R_c + R_5 \rightarrow I_c = I_5 = 0,711A$$

$$V_c = I_c \cdot R_c = 0,711 \cdot 1 = 0,711V$$

$$V_5 = 0,711 \cdot 7 = 4,977V$$

$$R_c = R_3 // R_4 \rightarrow V_3 = V_4 = 0,711V$$

$$I_3 = V_3 / R_3 = 0,711 / 2 = 0,356A$$

$$I_4 = 0,711 / 2 = 0,356A$$

$$R_b = R_a // R_6 \rightarrow V_a = V_6 = 12,788V$$

$$I_a = V_a / R_a = 12,788 / 12 = 1,066A$$

$$I_6 = 12,788 / 6 = 2,131A$$

$$R_a = R_1 + R_2 \rightarrow I_1 = I_2 = 1,066A$$

$$V_1 = I_1 \cdot R_1 = 1,066 \cdot 7 = 7,460V$$

$$V_2 = 1,066 \cdot 5 = 5,330 \text{V}$$


Answer:

	E	R1	R2	R3	R4	R5	R6	R7	R8	R9	R10
V	27	7,460	5,330	0,711	0,711	4,977	12,788	5,684	14,207	8,526	8,526
I	3,197	1,066	1,066	0,356	0,356	0,711	2,131	0,711	1,776	0,853	0,568
R	8,444	7	5	2	2	7	6	8	8	10	15

Uppgift 3 – Branch-current method

Assign direction of flow for each branch.

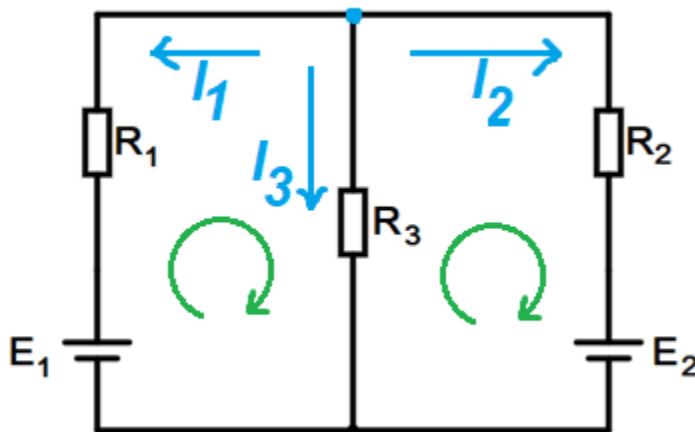Apply Kirchhoff's voltage law for both loops:



$$E_1 + V_{R1} - R_3 = 0$$

$$E_1 + I_1 \cdot R_1 - I_3 \cdot R_3 = 0$$

$$1 + 1 \cdot I_1 - 3 \cdot I_3 = 0$$

$$I_1 - 3 \cdot I_3 = -1$$

$$V_{R3} - V_{R2} - E_2 = 0$$

$$I_3 \cdot R_3 - I_2 \cdot R_2 - E_2 = 0$$

$$3 \cdot I_3 - 2 \cdot I_2 - 2 = 0$$

$$-2 \cdot I_2 + 3 \cdot I_3 = 2$$

Apply Kirchhoff's current law:

$$-I_1 - I_2 - I_3 = 0$$

Solve system of equation:

$$\begin{cases} I_1 - 3 \cdot I_3 = -1 \\ -2 \cdot I_2 + 3 \cdot I_3 = 2 \\ -I_1 - I_2 - I_3 = 0 \end{cases} \quad \begin{aligned} I_1 &= 0,091 \text{A} \\ I_2 &= -0,455 \text{A} \\ I_3 &= 0,364 \text{A} \end{aligned}$$

$$V_1 = I_1 \cdot R_1 = 0,091 \cdot 1 = 0,091 \text{V}$$

$$V_2 = I_2 \cdot R_2 = -0,455 \cdot 2 = -0,910 \text{V}$$

$$V_3 = I_3 \cdot R_3 = 0,364 \cdot 3 = 1,092 \text{V}$$


$$R_{E1} = E_1/I_1 = 1/0,091 = 10,989\Omega$$

$$R_{E2} = E_2/I_2 = 2/(-0,455) = -4,396\Omega$$

Answer

	R1	R2	R3	E1	E2
V (V)	0,091	-0,910	1,092	1	2
I (A)	0,091	-0,455	0,364	0,091	-0,455
R (Ω)	1	2	3	10,989	-4,396

Uppgift 3 - Nodal method

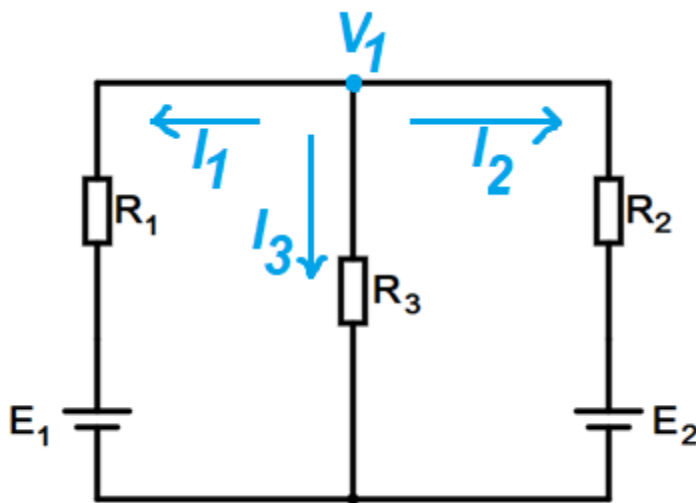

Assign direction of flow for each branch

Find each current based on node V1

$I_1 = (V_1 - E_1)/R_1$	$I_2 = (V_1 - E_2)/R_2$	$I_3 = V_1/R_3$
$I_1 = (V_1 - 1)/1$	$I_2 = (V_1 - 2)/2$	$I_3 = V_1/3$
$I_1 = V_1 - 1$	$I_2 = 0,5V_1 - 1$	$I_3 = 0,333V_1$

Apply Kirchhoff's current law at node V1

$$-I_1 - I_2 - I_3 = 0$$

$$-V_1 + 1 - 0,5V_1 + 1 - 0,333V_1 = 0$$

$$-1,833V_1 + 2 = 0$$

$$V_1 = 2/(1,833) = 1,091V$$

$$I_{E1} = I_1 = V_1 - 1 = 1,091 - 1 = 0,091A$$

$$I_{E2}=I_2=0,5V_1-1=-0,455A$$

$$I_3=0,333V_1=0,363A$$

$$V_{R1}=V_1-E_1=1,091-1=0,091V$$

$$V_{R2}=V_1-E_2=1,091-2=-0,909V$$

$$V_{R3}=V_1=1,091V$$

$$R_{E1}=E_1/I_{E1}=1/0,091=10,989\Omega$$

$$R_{E2}=E_2/I_{E2}=2/(-0,455)= -4,396\Omega$$

Answer:

	R1	R2	R3	E1	E2
V (V)	0,091	-0,909	1,091	1	2
I (A)	0,091	-0,455	0,363	0,091	-0,455
R (Ω)	1	2	3	10,989	-4,396


Uppgift 4 – Replacing sources

Current source with resistor in parallel can be replaced with voltage source and resistor in series

$$E_1=I_1 \cdot R_1=0,005 \cdot 2000=10V$$

$$E_2=I_2 \cdot R_2=0,004 \cdot 1000=4V$$

Redraw network with new information

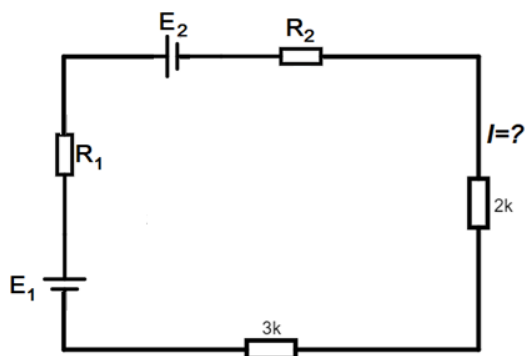

$$E_{Total}=E_1-E_2=10-4=6V$$

$$R_{Total}=R_1+R_2+R_3+R_4=2k\Omega+1k\Omega+2k\Omega+3k\Omega=8k\Omega$$

$$I_{Total}=6/8000=0.00075A=750\mu A$$


Answer: 750 μ A

Since E_1 is more powerful than E_2 it means that current flows clockwise. It also means that right before E_1 voltage is 0 and ground can be placed there.

To understand what will happen when switch a we need to look on original network. If switch a would be open, resistors with $2k\Omega$ and $3k\Omega$ (the ones that in series) will be 0A and 0V. For resistors that are in parallel to source current sources, the current will be the same as its source: current through resistor with $2k\Omega$ is 5mA (its voltage will be $2k\Omega \cdot 5mA = 10V$) and current through resistor with $1k\Omega$ is 4mA (its voltage will be $1k\Omega \cdot 4mA = 4V$).

Uppgift 4 – Nodal method

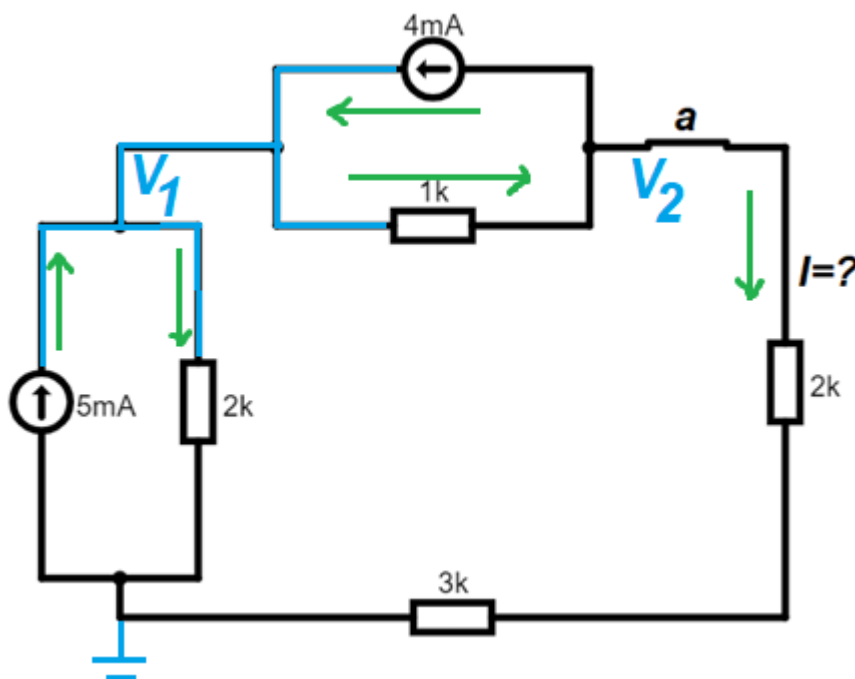There are three nodes defined: V_1 , V_2 and reference point (ground). Blue lines show where the V_1 is. Green lines show selected current flows.



Apply Kirchhoff's current law at nodes V_1 and V_2

$$\begin{array}{ll} 5mA + 4mA - V_1/2k\Omega - (V_1 - V_2)/1k\Omega = 0 & -4mA + (V_1 - V_2)/1k\Omega - V_2/(2k\Omega + 3k\Omega) = 0 \\ 0.009 - 0.0005V_1 - 0.001V_1 + 0.001V_2 = 0 & -0.004 + 0.001V_1 - 0.001V_2 - 0.0002V_2 = 0 \\ -0.0015V_1 + 0.001V_2 = -0.009 & 0.001V_1 - 0.0012V_2 = 0.004 \end{array}$$

Solving both equations as a system, $V_1 = 8.5V$ and $V_2 = 3.75V$

$$I = V_2 / (2k\Omega + 3k\Omega) = 3.75 / 5000 = 0.00075A = 750\mu A$$

Answer: 750 μA

Current goes the same way as shown in the network.

Ground can be anywhere between the resistor with $3k\Omega$ and source with $5mA$ and its parallel resistor with $2k\Omega$. Example, ground shown in the network.


If switch a would be open, resistors with $2k\Omega$ and $3k\Omega$ (the ones that in series) will be $0A$ and $0V$.

For resistors that are in parallel to source current sources, the current will be the same as its source: current through resistor with $2k\Omega$ is $5mA$ (its voltage will be $2k\Omega \cdot 5mA = 10V$) and current through resistor with $1k\Omega$ is $4mA$ (its voltage will be $1k\Omega \cdot 4mA = 4V$).

Uppgift 5 – Mesh method

Assign current flow clockwise.

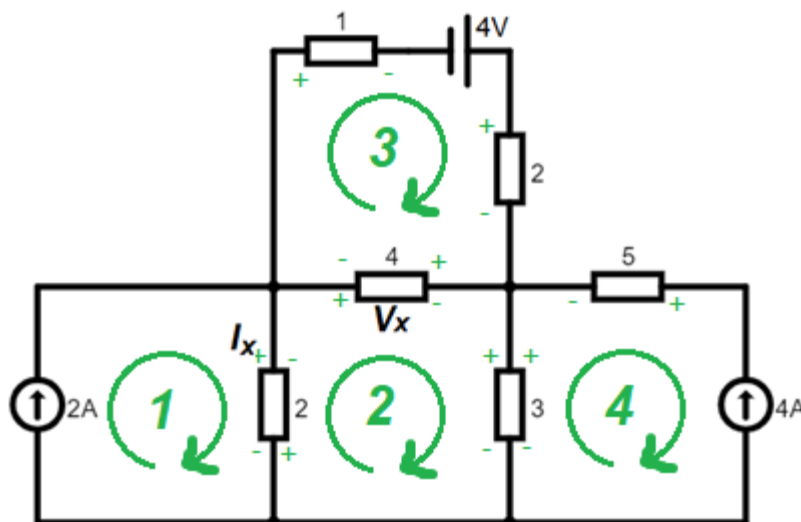Determine polarity of all elements. Pay attention that current in loop 4 goes counter clockwise.



Apply Kirchhoff's voltage law for each loop.

Loop 1: current I_1 is known from the current source: $I_1 = 2A$

Loop 4: current I_4 is known from the current source: $I_4 = 4A$

Loop 2:

$$\begin{aligned} -2(I_2 - I_1) - 4(I_2 - I_3) - 3(I_2 + I_4) &= 0 \\ -2I_2 + 2 \cdot 2 - 4I_2 + 4I_3 - 3I_2 - 3 \cdot 4 &= 0 \\ -9I_2 + 4I_3 - 8 &= 0 \end{aligned}$$

Loop 3:

$$\begin{aligned} -1I_3 + 4 - 2I_3 - 4(I_3 - I_2) &= 0 \\ -1I_3 + 4 - 2I_3 - 4I_3 + 4I_2 &= 0 \\ 4I_2 - 7I_3 + 4 &= 0 \end{aligned}$$

Solving both equations as a system, $I_2 = -0.851A$ and $I_3 = 0.085A$

The current of any branch is equal to the algebraic sum of associated mesh currents. I_1 is in the opposite direction of I_x and I_2 is in the same direction as I_x . Therefore:

$$I_x = I_2 - I_1 = -2.851 \text{ A}$$


Voltage V_x can be found based on current through the resistor:

$$I_{R2} = I_2 - I_3 = -0.936 \text{ A}$$

$$V_{R2} = I_{R2} \times R_2 = -0.9362 \times 4 = -3.744 \text{ V}$$

Answer: current $I_x = -2.851 \text{ A}$ and voltage $V_x = -3.744 \text{ V}$

Uppgift 5 – Nodal method

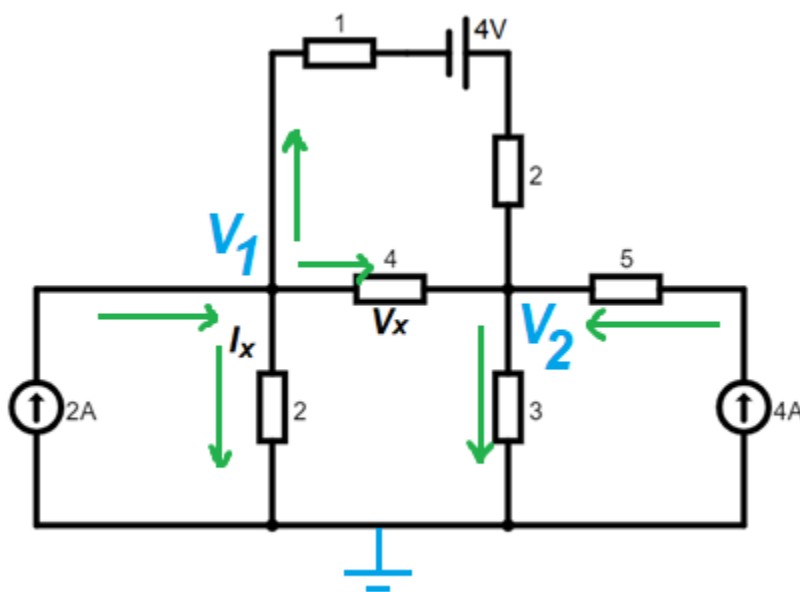

Apply Kirchhoff's current law at nodes V1 and V2

Node V1:

$$2 - V_1/2 - (V_1 - V_2)/4 - (V_1 + 4 - V_2)/(1+2) = 0$$

$$2 - 0.5V_1 - 0.25V_1 + 0.25V_2 - 0.333V_1 - 1.333 + 0.333V_2 = 0$$

$$-1.083V_1 + 0.583V_2 + 0.667 = 0$$

Node V2:

$$(V_1 - V_2)/4 + (V_1 + 4 - V_2)/(1+2) - V_2/3 + 4 = 0$$

$$0.25V_1 - 0.25V_2 + 0.333V_1 + 1.333 - 0.333V_2 - 0.333V_2 + 4 = 0$$

$$0.583V_1 - 0.916V_2 + 5.333 = 0$$

Solving both equations as a system, $V_1 = 5.704 \text{ V}$ and $V_2 = 9.453 \text{ V}$

$$V_x = V_1 - V_2 = 5.704 - 9.453 = -3.749\text{V}$$

$$I_x = V_1/2 = 5.704/2 = 2.852\text{A}$$

Answer: current $I_x = 2.852\text{A}$ and voltage $V_x = 3.749\text{V}$