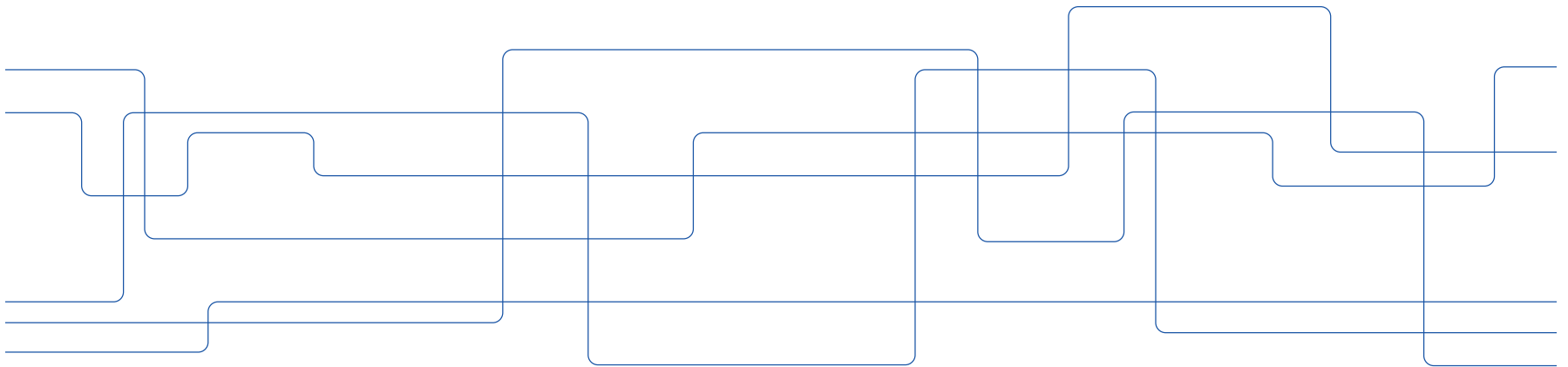




HE1027 Electrical Principals

Lecture 1: Basic concepts







Course Structure

- 10 lectures (digital)
- 7 exercises (physical)
- 6 online quizzes (optional)
- 5 labs (physical)
 - book times in the calendar
- 2 partial exams (optional, physical)
 - April 11
 - May 16
- written exam (physical)
 - June 3

Maksims Kornevs (kornevs@kth.se)

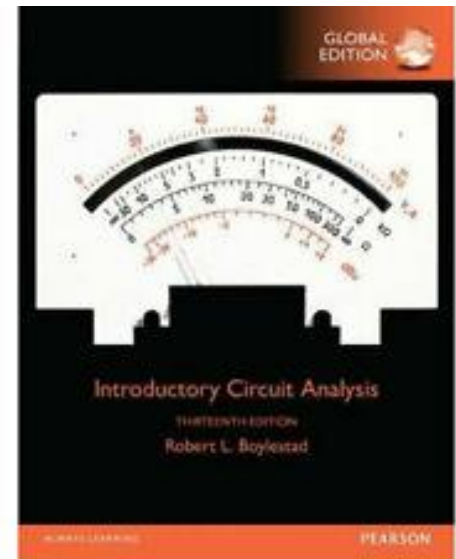

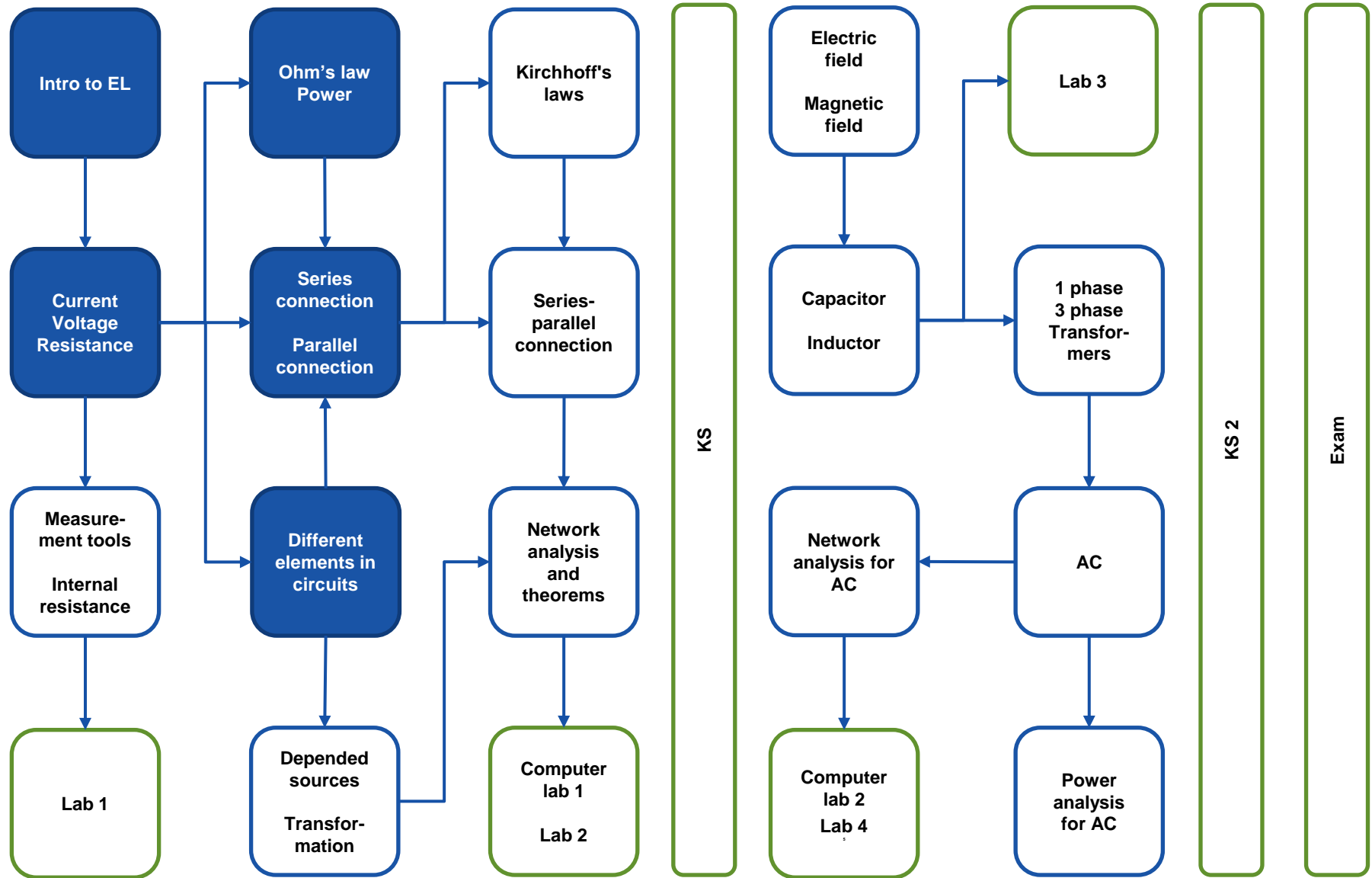

Already covered

Is covered today

Will be covered



What is ELECTRICITY?

Electricity is a form of energy that can be changed into other forms





Two Types of Electricity

Static electricity produced when some materials are rubbed together

Current electricity is caused by electrons that move through metal



Where does Electricity come from?

Power Stations

Supply a lot of energy



Power generators

Similar to power stations




Electric batteries

Supply a little electricity
Portable
Safe



Electrical Units

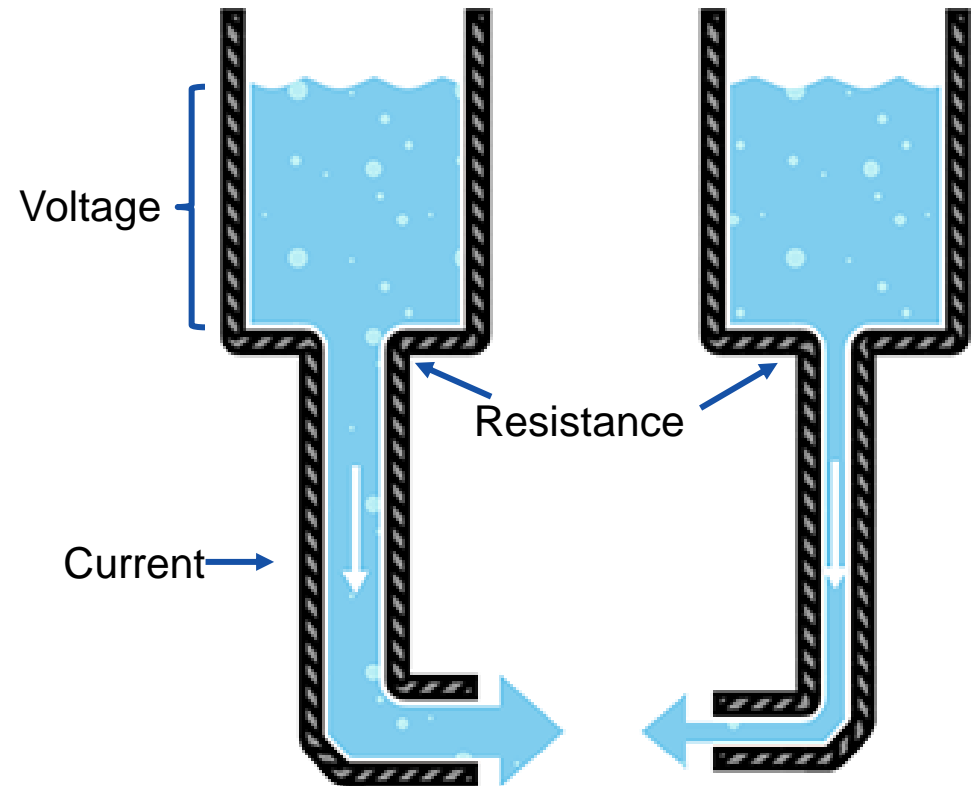- Basic units of measurement
 - Current (amperes A)
 - Voltage (volts V)
 - Resistance (ohms Ω)






Current


- To make an electrical appliance work, electricity must flow through it
 - The flow of electricity is called an ***electric current***
 - An electric current is the rate of flow of ***electric charges*** in a circuit
 - The path along which the electric current moves is called the ***electric circuit***
-

Electric Charge and Current

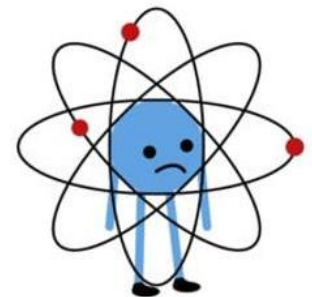- Atoms have positive protons and negative electrons, where $Nr_{\text{protons}} = Nr_{\text{electrons}}$
- Some electrons can leave their atoms and flow without any specific direction




I lost an electron.

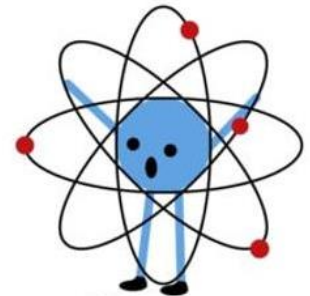


**No way.
Are you Positive?**

Electric Charge and Current

- Atoms have positive protons and negative electrons, where $Nr_{\text{protons}} = Nr_{\text{electrons}}$
- Some electrons can leave their atoms and flow without any specific direction
- Charge (Q) is measured in **coulombs (C)**
1 coulomb = 6 242 000 000 000 000 000 electrons
- When wire is connected to an electric source, electrons in the wire start to move from negative terminal to positive. This flow is **electric current**

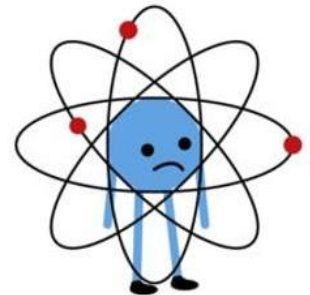


I lost an electron.

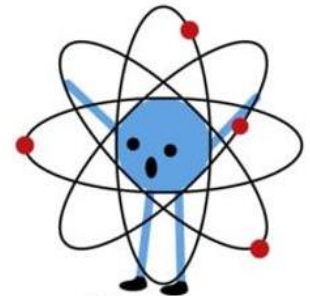


No way.
Are you Positive?

Electric Charge and Current

- Atoms have positive protons and negative electrons, where $Nr_{\text{protons}} = Nr_{\text{electrons}}$
- Some electrons can leave their atoms and flow without any specific direction
- Charge (Q) is measured in **coulombs (C)**
1 coulomb = 6 242 000 000 000 000 000 electrons
- When wire is connected to an electric source, electrons in the wire start to move from negative terminal to positive. This flow is **electric current**
- Electric current (I) is measured in **amperes (A)**
1 ampere = 1 coulomb / 1 second

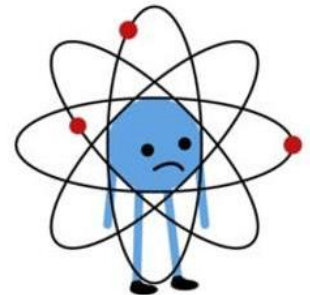


I lost an electron.

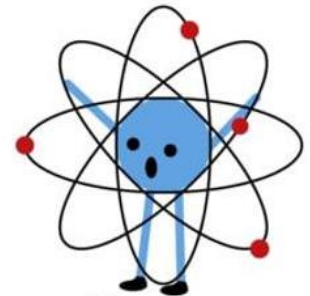

No way.
Are you Positive?

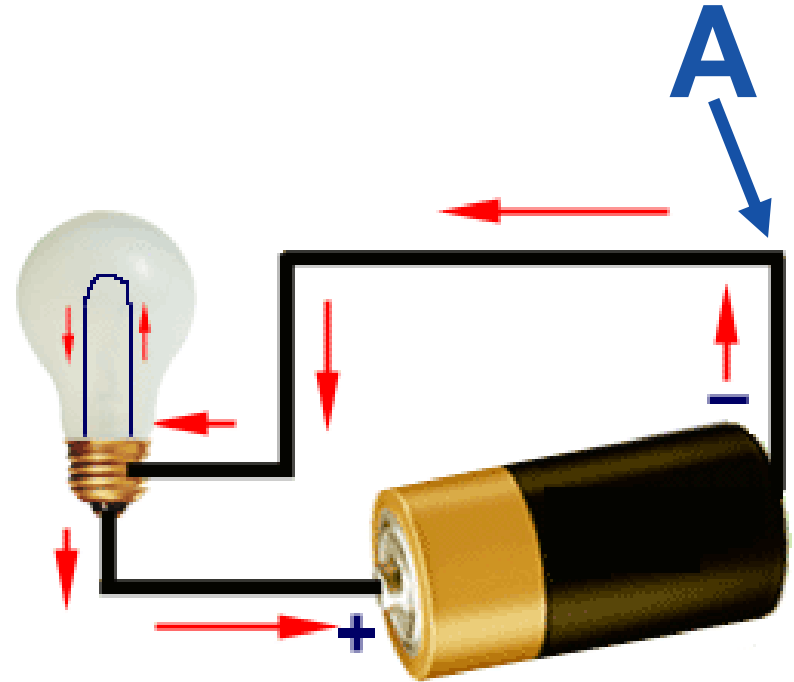Example 1

- The charge in point A is 0.16 C
- The charge flows every 64 ms.
- *What is a current in that point?*



$$I = \frac{Q}{t} = \frac{0,16}{0,064} = 2,5 A$$




Example 2

- The current is 5mA
- *How long it will take for $4 \cdot 10^{16}$ electrons to pass?*


$$Q = \frac{4 \cdot 10^{16}}{6.242 \cdot 10^{18}} = 6.41 \cdot 10^{-3} C$$

$$t = \frac{Q}{I} = \frac{6.41 \cdot 10^{-3}}{5 \cdot 10^{-3}} = 1,28s$$

Current Flow

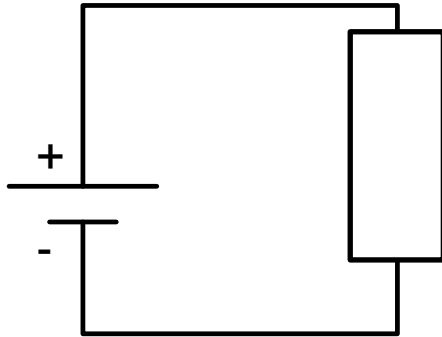

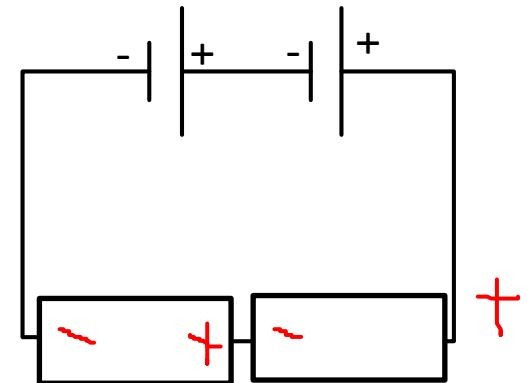- Electron flow goes from negative to positive
- However, in analysis is used **convention flow**
- Convention flow goes from highest to lowest (from positive to negative)
- Similar high and low we can determine for all elements by determine by looking how element changes potential



Voltage

- An electric cell gives energy to the electrons and pushes them round a circuit. Voltage is a measure of how much energy the electrons receive
- Voltage (V) = $\frac{\text{energy (W)}}{\text{charge (Q)}}$
- Different voltages are supplied by different cells and batteries



Resistance: Conductors and Insulators

- When an electric current flows through a circuit, there will be some resistance that opposes it

Low resistance


Good conductors

Superconductor $\rho=0$
Silver $\rho= 1.59 \times 10^{-8}$
Copper $\rho=1.68 \times 10^{-8}$
Gold $\rho=2.44 \times 10^{-8}$
Aluminium $\rho=2.65 \times 10^{-8}$
Iron $\rho=9.7 \times 10^{-8}$

High resistance

Poor conductors

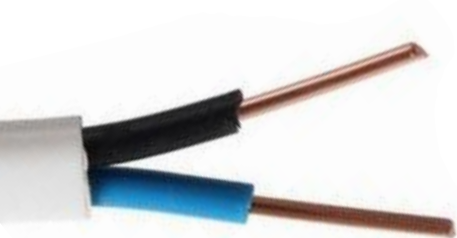Superinsulators $\rho=\infty$
Teflon $\rho=10^{24}$
Dry wood $\rho=10^{15}$
Air $\rho=10^{12}$
Rubber $\rho=10^{13}$
Diamond $\rho=10^{12}$



$$\text{Resistance}(R) = \frac{\text{resistivity}(\rho) * \text{length}(L)}{\text{cross sectional area (A)}}$$

Resistors

- Resistors are electrical components that are specially made to have a certain resistance
- Resistors are connected in a circuit to resist the current flow
- Resistors can be:
 - fixed resistors (only one resistance value)
 - variable resistors (resistors can be adjusted to change the resistance)




Resistor Color-coding

- Thin-film resistors use colour coding based on 4, 5 or 6 bands
- If 4 bands: 1st digit, 2nd digit, multiplier, tolerance
- If 5 bands: 1st digit, 2nd digit, 3rd digit, multiplier, tolerance
- If 6 bands: 1st digit, 2nd digit, 3rd digit, multiplier, tolerance, temp coef



$100\Omega \pm 5\%$

1 0 x 10 ± 5%

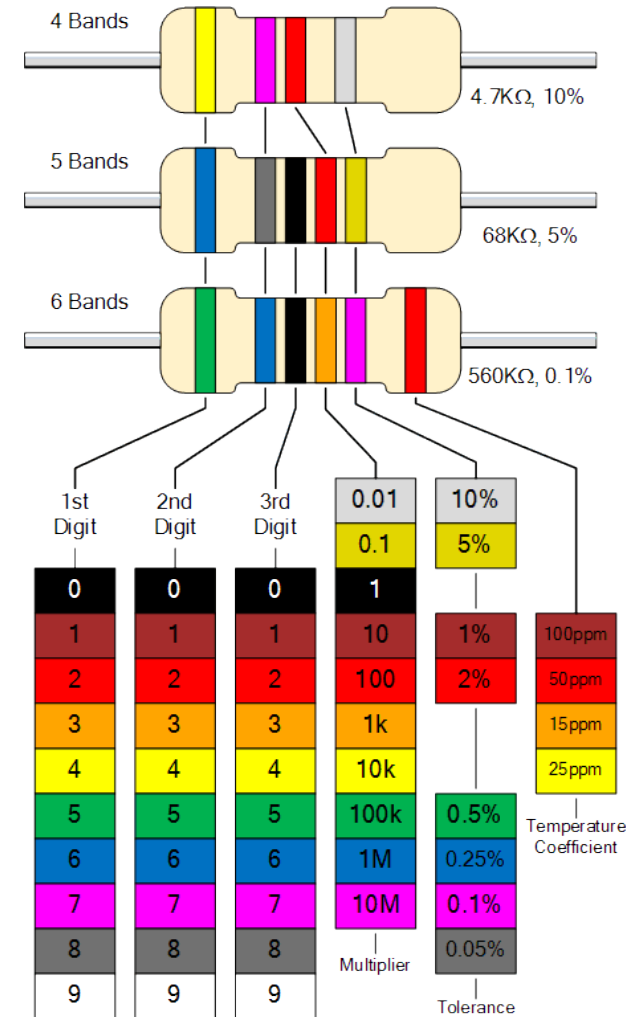




Drawing Circuits




wire



inductor

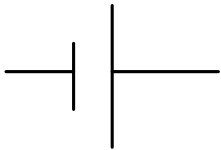


Voltage source

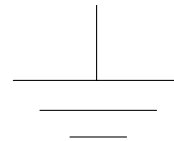


earth




power supply

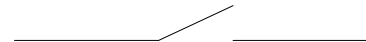

switch

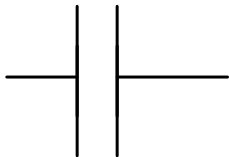

capacitor

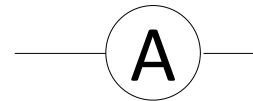

ammeter








resistor



voltmeter

Examples

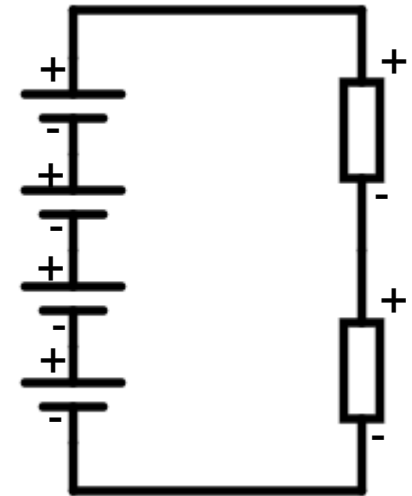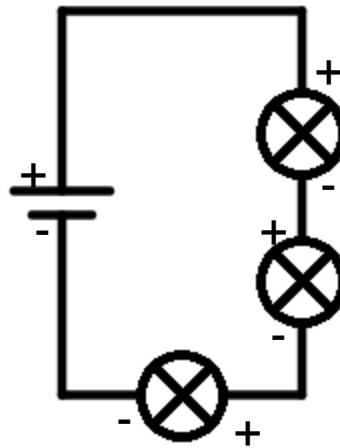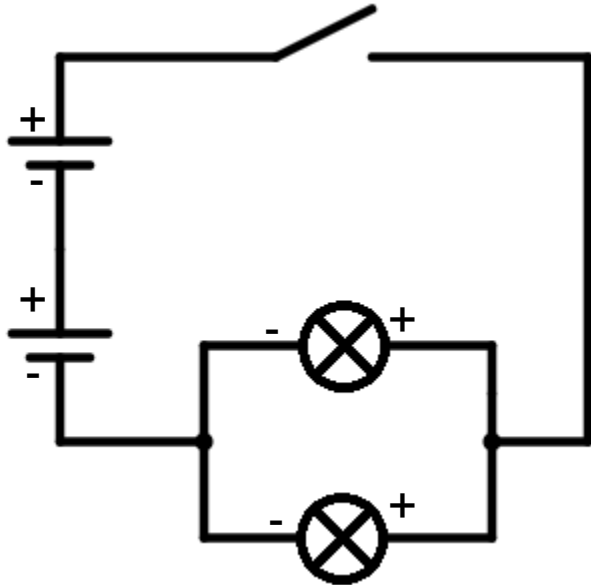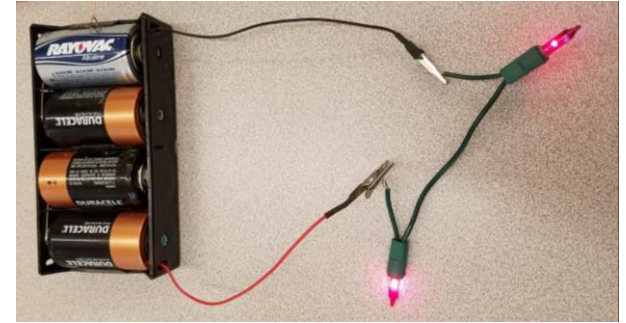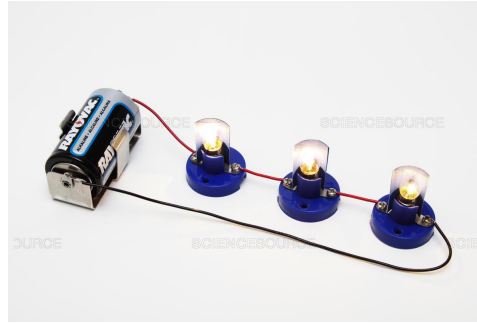

Ohms Law


- Current through a conductor between two points is directly proportional to the voltage across the two points

- Current (I) = $\frac{\text{Voltage (V)}}{\text{Resistance (R)}}$

- $I = \frac{V}{R}$

$$V = I * R$$

$$R = \frac{V}{I}$$

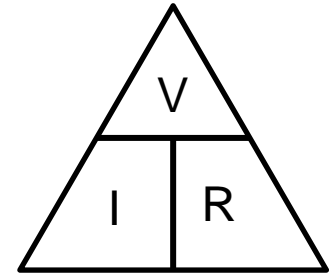

- V is applied to voltage drops
- E is applied to voltage sources

$$V=E$$




Example 1

What is a resistance of a light bulb if current is 500 mA and voltage is 220V?

$$I = \frac{V}{R} \rightarrow R = \frac{V}{I} = \frac{220}{0,5} = 440\Omega$$

Example 2


- What is a current?

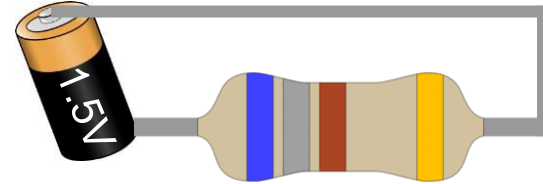


$$I = \frac{V}{R} = \frac{1,5}{68 \cdot 10} = \frac{1,5}{680} = 2,2mA$$

Power

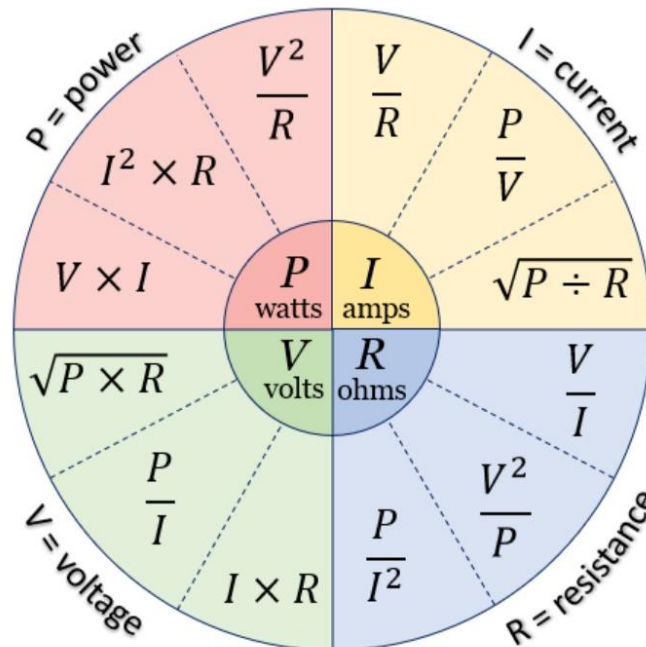- Power shows how much work (energy conversion) can be done in a specific amount of time
- Power (P) = $\frac{\text{energy (W)}}{\text{time (t)}}$



Different Types of Connection

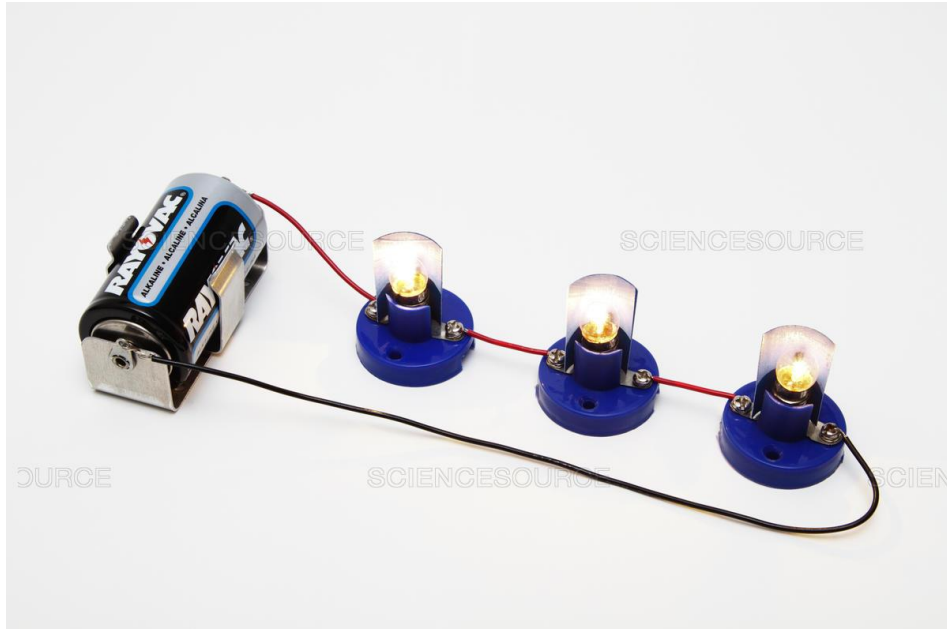


Series Connection



Parallel Connection

Series Circuits

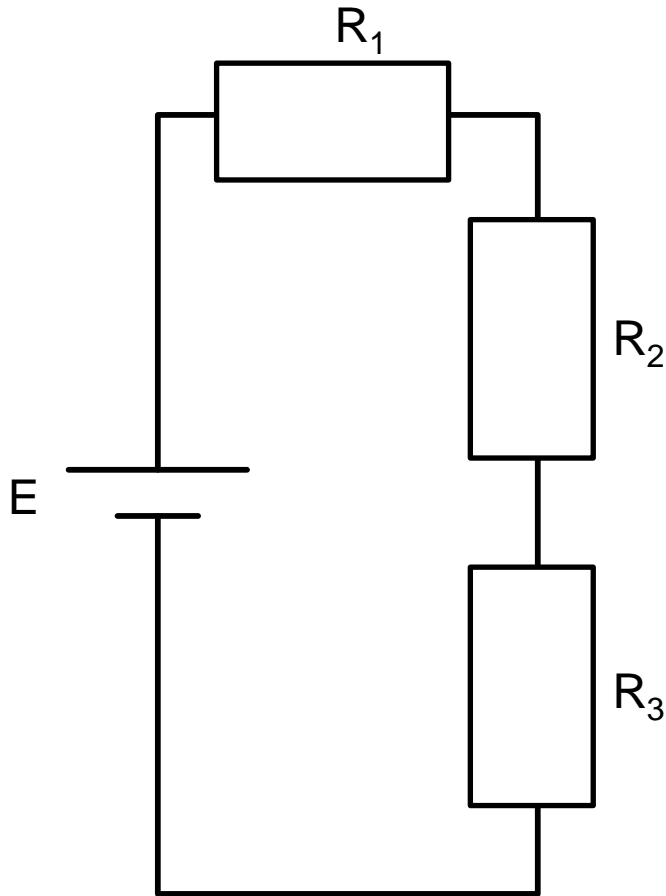

- The total resistance of a series configuration is a sum of the resistance levels


$$R_T = R_1 + R_2 + R_3$$

- The current is the same at every point in a series circuit

$$I_T = I_1 = I_2 = I_3 \qquad I_T = \frac{E}{R_T}$$

- Voltage is calculated for each element

Example

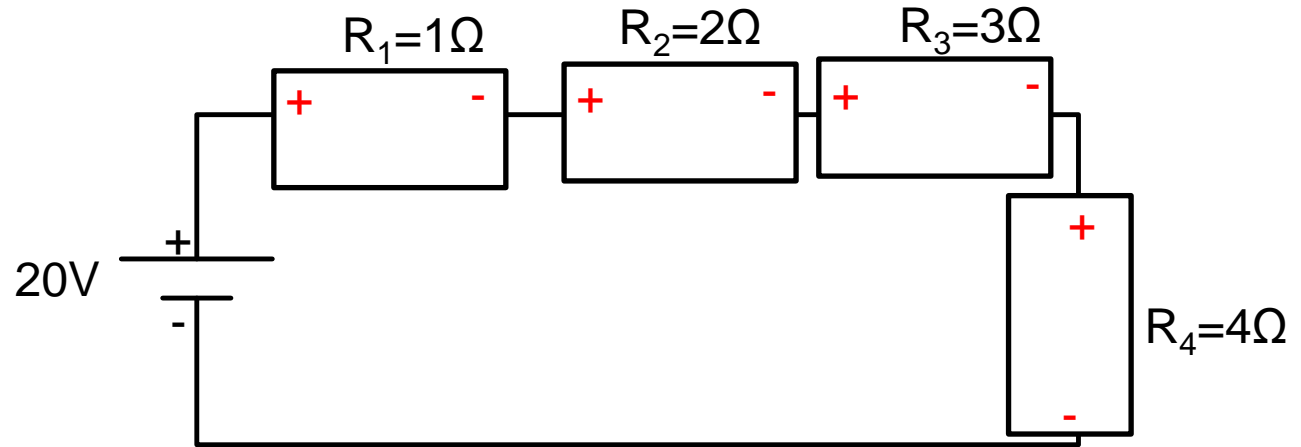

Determine the voltage across each resistor and indicate their polarity

$$R_{Total} = 1\Omega + 2\Omega + 3\Omega + 4\Omega = 10\Omega$$

$$I_{Total} = I_1 = I_2 = I_3 = I_4 = \frac{E}{R_{Total}} = \frac{20}{10} = 2A$$


$$V_1 = R_1 \cdot I_1 = 2V$$

$$V_3 = R_3 \cdot I_3 = 6V$$

$$V_2 = R_2 \cdot I_2 = 4V$$

$$V_4 = R_4 \cdot I_4 = 8V$$

Parallel Circuits

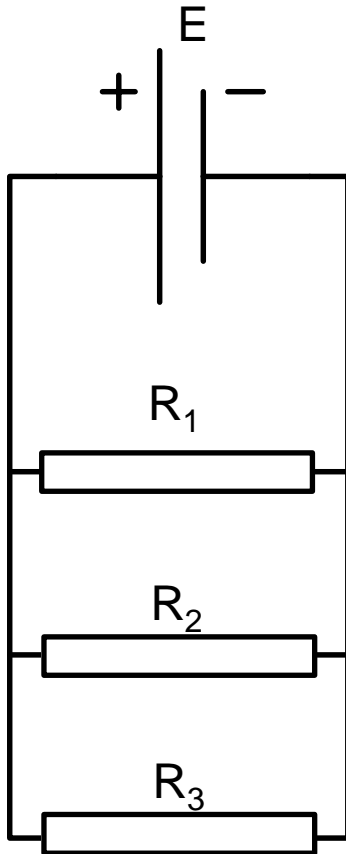

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$


Voltage is the same for all branches

Current is calculated for each element

For two parallel resistors: $R_T = \frac{R_1 \cdot R_2}{R_1 + R_2}$



Example

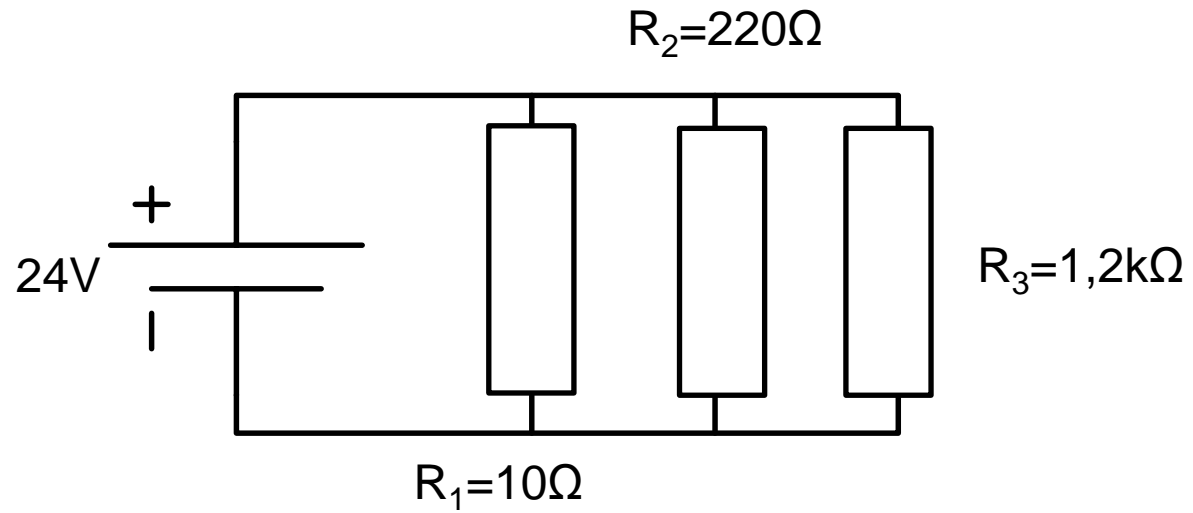

Determine the voltage through each branch

Since it is parallel connection, $V_1 = V_2 = V_3 = V_{Total} = 24\text{V}$

Find the total resistance

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{10} + \frac{1}{220} + \frac{1}{1200} = 0,10538 \quad R_T = \frac{1}{0,10538} = 9,49\Omega$$

Calculate the source current

$$I = \frac{V}{R_T} = \frac{24}{9,49} = 2,53\text{A}$$

Determine the current through each branch

$$I_1 = \frac{V}{R_1} = \frac{24}{10} = 2,4\text{A} \quad I_2 = \frac{V}{R_2} = \frac{24}{220} = 0,11\text{A} \quad I_3 = \frac{V}{R_3} = \frac{24}{1200} = 0,02\text{A}$$



Suggested reading

Introductory Circuit Analysis

- Kap 1: 1.6 – 1.8
- Kap 2: 2.2 - 2.12, **2.2 - 2.8**
- Kap 3: 3.4, **3.5 - 3.8**, 3.9
- Kap 4: **4.2 - 4.5**
- Kap 5: **5.1 - 5.5**
- Kap 6: **6.2 - 6.4**



Suggested exercises

- Kap 1: 30-33
 - Kap 2: 8-11, 14-17
 - Kap 3: 34-35, 44
 - Kap 4: 1-12, 24-28
 - Kap 5: 3, 7, 10
 - Kap 6: 7, 13, 15, 17
-