
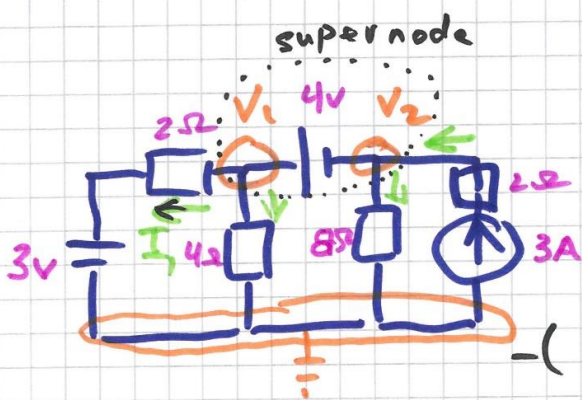


Supernode example

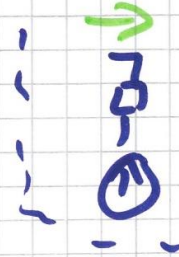

~~12~~

$$V_2 + 4 = V_1$$



$$\dots -(-3) = 0$$

$$-\left(\frac{V_1 - 3}{2}\right) - \left(\frac{V_1}{4}\right) - \left(\frac{V_2}{8}\right) + \left(\frac{3}{1}\right) = 0$$

$$-\frac{V_1 + 3}{2} - \frac{V_1}{4} - \frac{V_2}{8} + 3 = 0$$

$$\frac{-4V_1 + 12}{8} - \frac{2V_1}{8} - \frac{V_2}{8} + \frac{24}{8} = 0$$

$$-4V_1 + 12 - 2V_1 - V_2 + 24 = 0$$

$$-6V_1 + V_2 = -36$$

$$6V_1 + V_2 = 36$$

$$V_2 + 4 = V_1 \Rightarrow V_2 = V_1 - 4$$



$$6V_1 + V_1 - 4 = 36$$

$$7V_1 = 40$$

$$V_1 = \frac{40}{7} = 5.7V$$

$$V_2 = 5.7 - 4 = 1.7V$$


Superposition Theorem

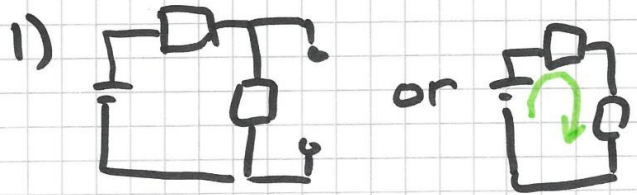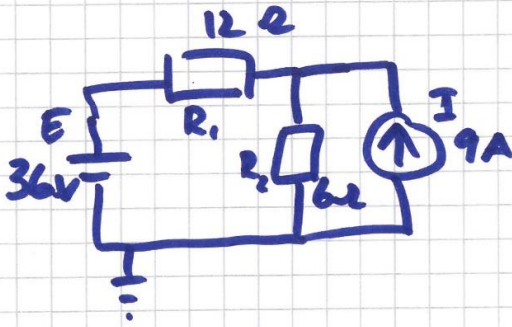

$$R_T = 12 + 6 = 18 \Omega$$

$$I_T = \frac{36}{18} = 2A$$
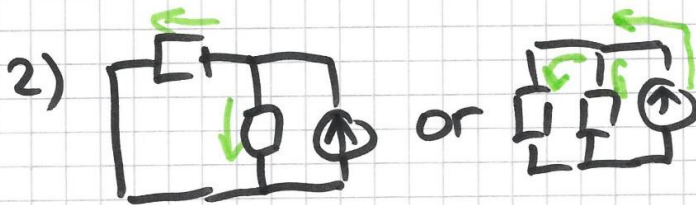
$$\rightarrow I'_{R_1} = 2A \quad \downarrow I'_{R_2} = 2A$$



$$R_T = \frac{12 \cdot 6}{12 + 6} = 4 \Omega$$

$$V_T = 4 \Omega \cdot 9A = 36V$$

$$\leftarrow I''_{R_1} = \frac{36}{12} = 3A$$



$$\downarrow I''_{R_2} = \frac{36}{6} = 6A$$

3)


$$\overleftarrow{I}_{R_1} = \overleftarrow{I}'_{R_1} + \overleftarrow{I}''_{R_1} = -2 + 3 = 1A$$

$$\downarrow I_{R_2} = \overleftarrow{I}'_{R_2} + \overleftarrow{I}''_{R_2} = 2A + 6A = 8A$$

Thevenin Theorem

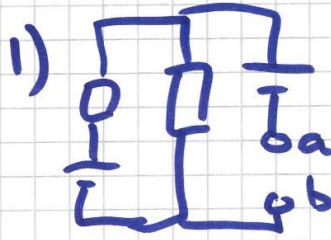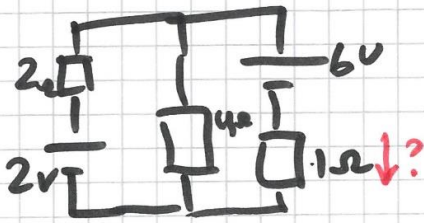


2) R_{TH}

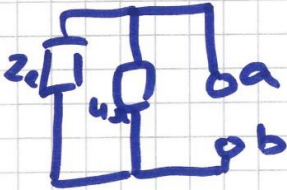


$$\underline{R_{TH} = R_{ab} = \frac{4 \cdot 2}{4+2} = \frac{8}{6} = 1.333 \Omega}$$

3) E_{TH}

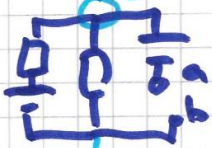

$$E_{TH} = E_{ab} = E_a - E_b = E_a$$

$$E_a = E_c - 6$$

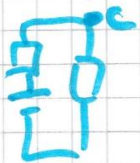

$$R_T = 2 + 4 = 6 \Omega$$




$$I = 2/6 = 0.333 A$$

$$V_R = 2 \cdot 0.333 = 0.666 V$$

$$V_c = 2 - 0.666 = 1.333 V$$



$$V_a = 1.333 - 6 = -4.667 V$$

$$\underline{E_{TH} = V_a = -4.667 V}$$

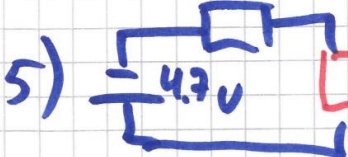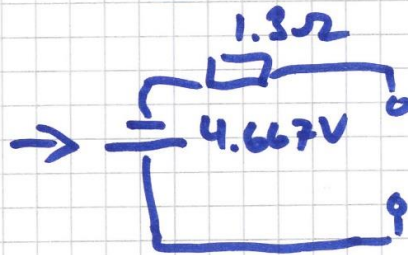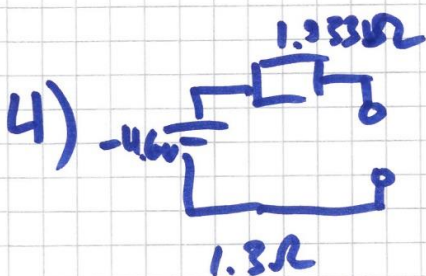


$$5) \quad I_1 = \frac{4.7}{1.3+1} = 2 A$$

$$I_{R_2} = 2 A \uparrow$$

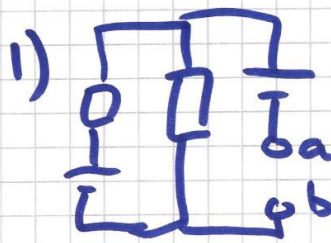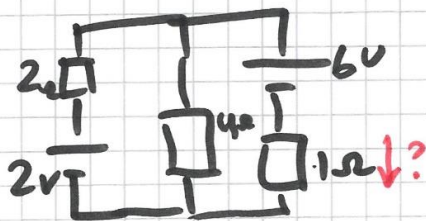


Norton Theorem

2) R_{TH}

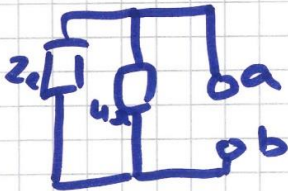

$$\underline{R_{TH} = R_{ab} = \frac{4 \cdot 2}{4 + 2} = \frac{8}{6} = 1.333 \Omega}$$

3) $I_N = I_2$

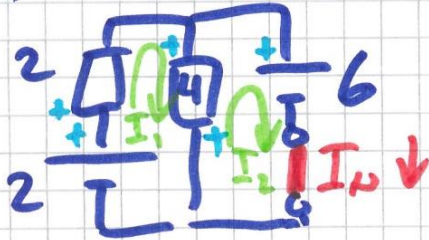

$$\begin{aligned} L_1: +2 - 2 \cdot I_1 - 4(I_1 - I_2) &= 0 \\ 2 - 2I_1 - 4I_1 + 4I_2 &= 0 \\ -6I_1 + 4I_2 + 2 &= 0 \end{aligned}$$

$$\begin{aligned} L_2: -4(I_2 - I_1) - 6 &= 0 \\ 4I_1 - 4I_2 - 6 &= 0 \end{aligned}$$

$$\begin{cases} -6I_1 + 4I_2 + 2 = 0 \\ 4I_1 - 4I_2 - 6 = 0 \end{cases}$$

$$-2I_1 - 4 = 0$$

$$I_1 = -2A$$



$$-6(-2) + 4I_2 + 2 = 0$$

$$12 + 4I_2 + 2 = 0$$

$$4I_2 = -14$$

$$I_2 = -3.5A$$

$$R_N = 1.333 \Omega$$

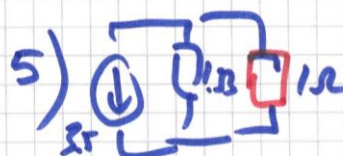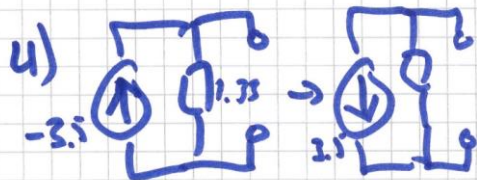


$$R_T = \frac{1.333 \cdot 1}{2.333} = 0.57 \Omega$$

$$V_T = 0.57 \cdot 3.5 = 2V$$


$$\uparrow I_{R_1} = \frac{2}{1} = 2V$$

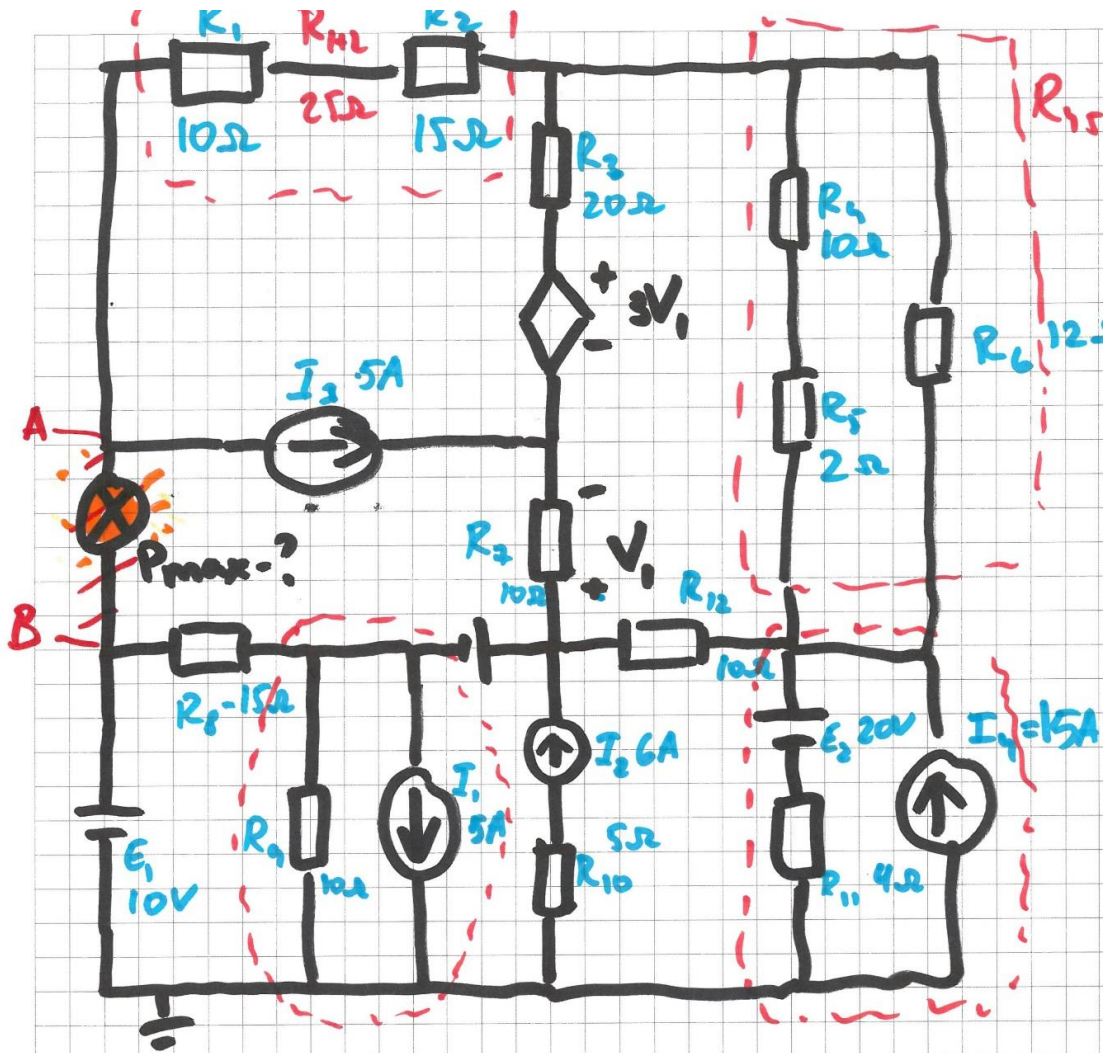Find what is maximum power of a light bulb




Since we need to find P_{max} it means we need to use maximum power theorem and Thevenin theorem

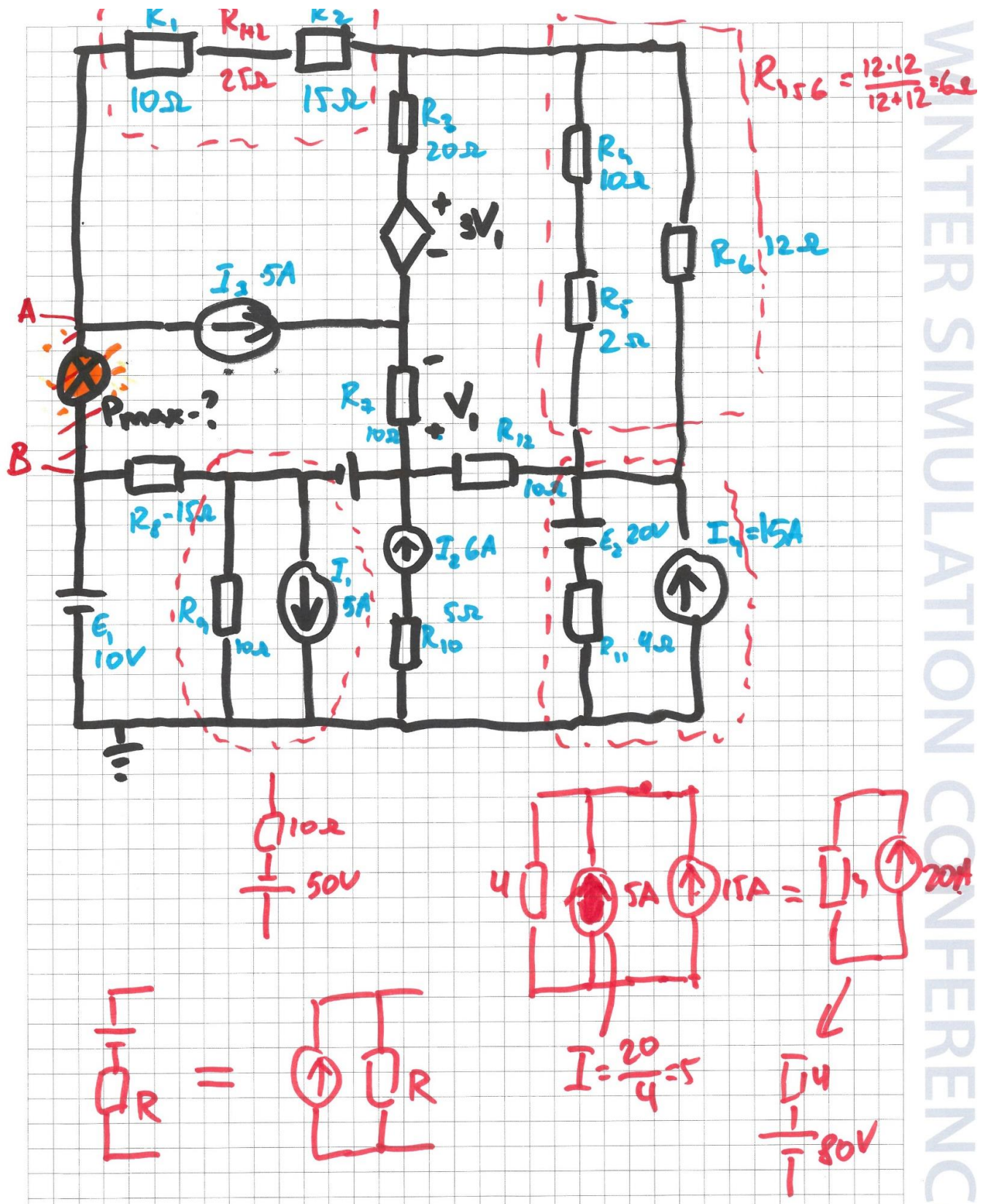Optional: first we simplify circuit using serial-parallel technique and source transformation



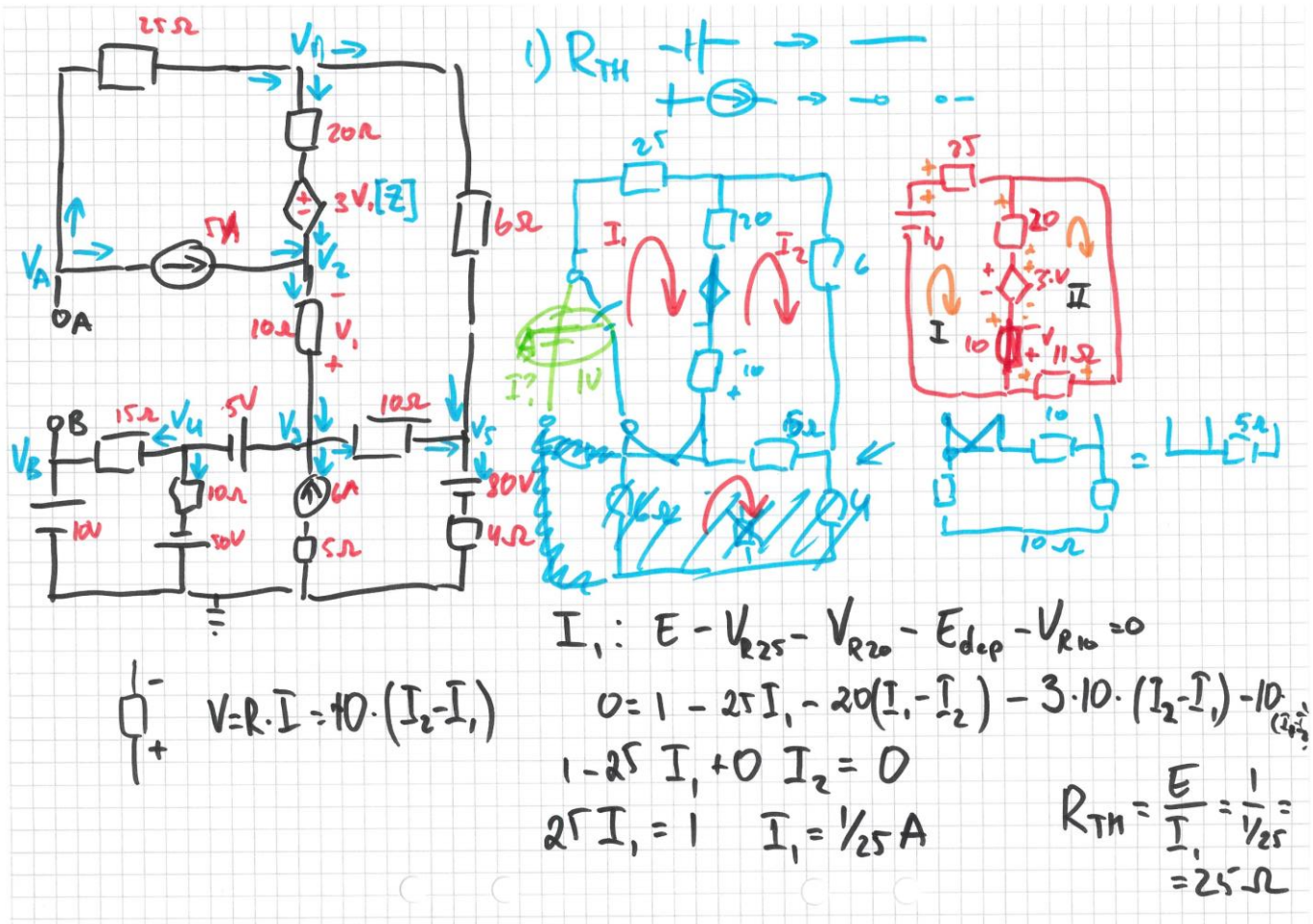We find R_{Th} . Important, that the circuit has a depended source!



We are calculating E_{Th} . The final answer is not correct, since we did not complete solving equations

$$E_{Th} = V_a - V_B = V_a - 10$$

$$V_a: (5A) + \left(\frac{V_a - V_1}{25}\right) = 0$$

$$\frac{V_a}{25} - \frac{V_1}{25} = -5$$

$$V_1: +\left(\frac{V_a - V_1}{25}\right) - \left(\frac{V_1 - V_2 - 3Z}{20}\right) - \left(\frac{V_1 - V_5}{6}\right) = 0$$

$$Z = V_3 - V_2$$

$$\frac{3V_a}{25} - \frac{V_1}{25} - \frac{V_1}{20} + \frac{V_2}{20} + \frac{3V_3}{20} - \frac{3V_2}{20} - \frac{V_1}{6} + \frac{V_5}{6} = 0$$

$$V_2: (5) + \left(\frac{V_1 - V_2 - 3V_2 + 3V_3}{20}\right) - \left(\frac{V_2 - V_3}{10}\right) = 0$$

$$V_3 \neq V_4 - \text{super node } V_4 + 5 = V_3$$


$$V_3 + V_4: -\left(\frac{V_4 - V_3}{15}\right) - \left(\frac{V_4 - 0 + 50}{10}\right) - (-6) + \left(\frac{V_2 - V_3}{10}\right) - \left(\frac{V_3 - V_5}{10}\right) = 0$$

$$V_5: +\left(\frac{V_1 - V_5}{6}\right) + \left(\frac{V_3 - V_5}{10}\right) - \left(\frac{V_5 - 80}{4}\right) = 0$$

$$V_B = 10V$$

$$\begin{array}{l} \text{guess} \\ V_a = 20V \\ E_{Th} = 20 - 10 = 10V \end{array}$$

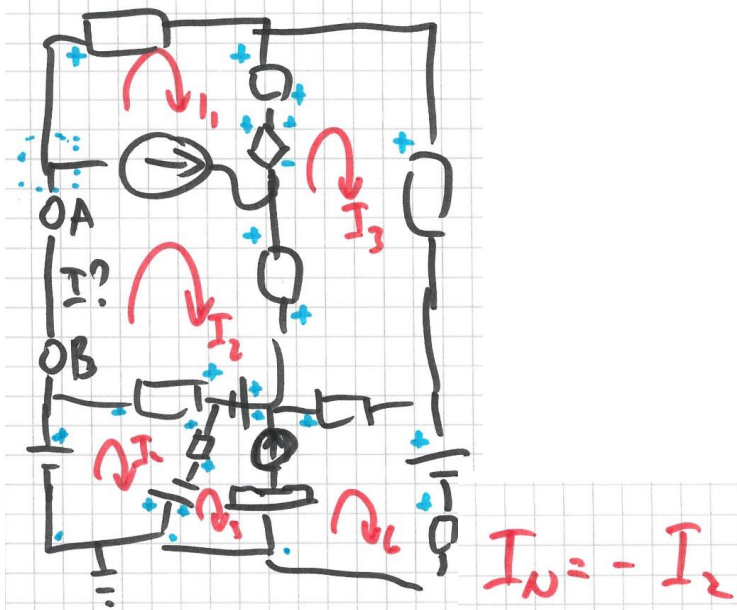Optional: We are calculating I_N . The final answer is not correct, since we did not complete solving equations



$$I_4: 10 - 15(I_4 - I_2) - 10(I_4 - I_1) + 50 = 0$$

$$I_3: 10(I_3 - I_2) + 3(10(I_3 - I_2)) - 20(I_3 - I_1) - 6I_3 = 0$$

$$I_1 + I_2: \begin{matrix} \uparrow I_1 \\ \uparrow I_2 \end{matrix} \xrightarrow{5A} I_2 = I_1 + 5$$

$$I_1 + I_2: -25I_1 - 20(I_1 - I_3) - 3(10(I_3 - I_2)) - 10(I_3 - I_2) - 5V - 15(I_2 - I_4) = 0$$


$$I_5 + I_6: \begin{matrix} \uparrow 6A \\ \leftarrow I_5 \\ \leftarrow I_6 \end{matrix} I_6 = I_5 + 6$$

$$-50 - 10(I_5 - I_4) + 5 - 10(I_6 - I_3) - 80 - 4I_6 = 0$$

$$\underbrace{I_2 = 5A}_{\text{guess}}$$


$$I_N = -5A$$

Finding final power

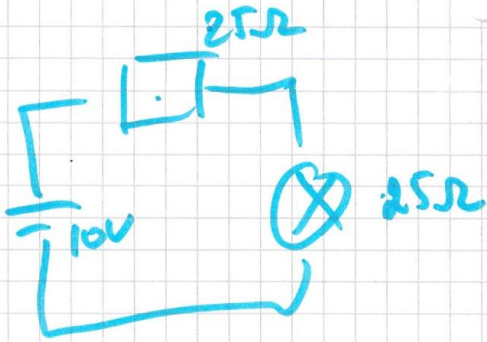

$$I_T = \frac{10}{25+25} = \frac{10}{50} = 0.2$$
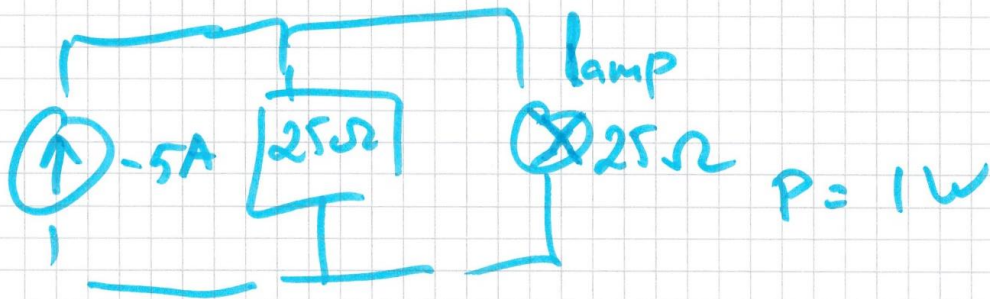
$$P = V \cdot I = I \cdot R \cdot I = 0.2^2 \cdot 25 = 1W$$



$$R_{Th} = \frac{E_{Th}}{I_N} = \frac{10V}{-5} = 25\Omega$$