




Kontrollskrivning KS1 i Ellära (HE1027)

Uppgift 1 [0.5p]

Två multimetrar (M_1 och M_2) är korrekt anslutna till kretsen nedan. Vad mäter dessa multimetrar och vilka värden läser de av?

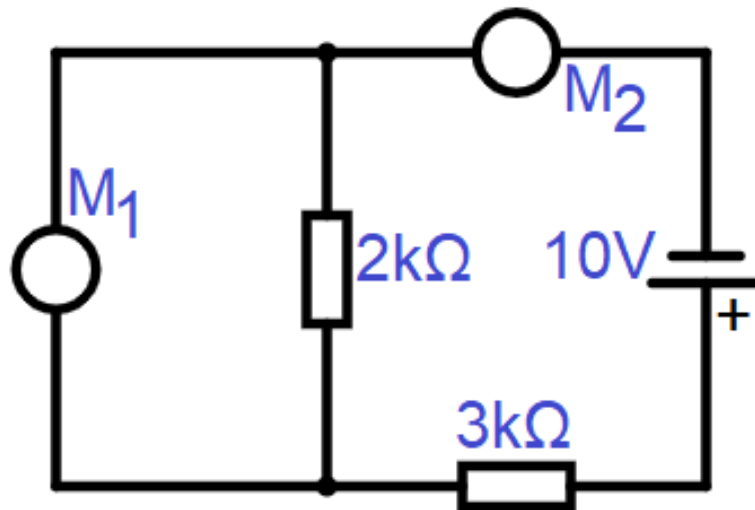Two multimeters (M_1 and M_2) are properly connected to the circuit below. What measure these multimeters and what values do they read?



Svar


Since M_1 is connected parallel to $2k\Omega$ resistor, it can be voltmeter or ohmmeter. But the network has a power supply, it cannot be ohmmeter. M_2 is connected in series to the network, so it is ammeter. R_T is $2k\Omega + 3k\Omega = 5k\Omega$. $I_T = V/R_T = 10/5k = 2mA$. Voltage consumption by the $2k\Omega$ resistor is $I_T \cdot R = 2m \cdot 2k = 4V$.

So M_1 is a voltmeter and it shows 4V and M_2 is an ammeter and it shows 2mA

Uppgift 2 [1.5p]

Bestäm resistansen R_{AB} mellan A och B i kretsen nedan.

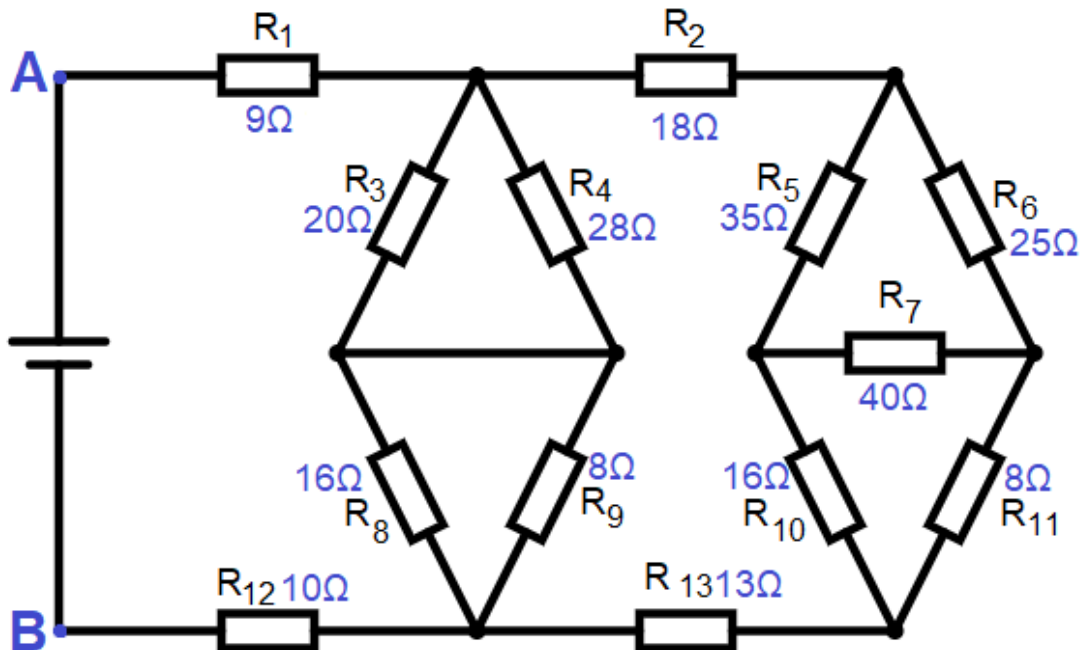Determine resistance R_{AB} between A and B in the following circuit.




Svar:

We need to transform resistors R_5 , R_6 and R_7 from the triangle to the Y (there are several options what we can transform).

$$R_x = \frac{R_5 \cdot R_6}{R_5 + R_6 + R_7} = \frac{35 \cdot 25}{35 + 25 + 40} = \frac{875}{100} = 8.75\Omega$$

$$R_y = \frac{35 \cdot 40}{35 + 25 + 40} = 14\Omega$$
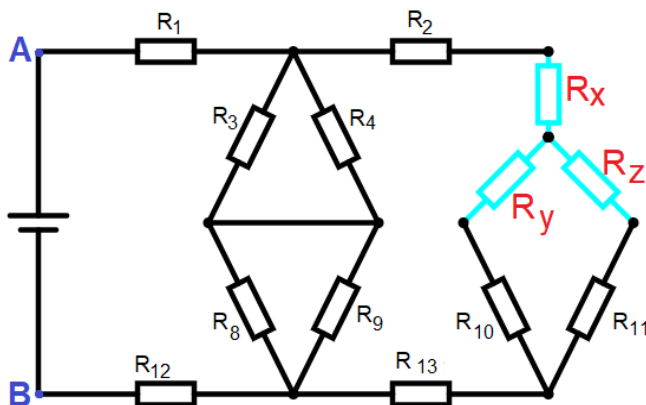
$$R_z = \frac{25 \cdot 40}{35 + 25 + 40} = 10\Omega$$




$$R_{AB} = R_1 + ((R_3 // R_4) + (R_8 // R_9)) // (R_2 + R_x + (R_y + R_{10}) // (R_z + R_{11}) + R_{13}) + R_{12} = 31.75\Omega$$

Uppgift 3 [2p]

Bestäm strömmarna genom varje resistor genom att använda maskanalys.

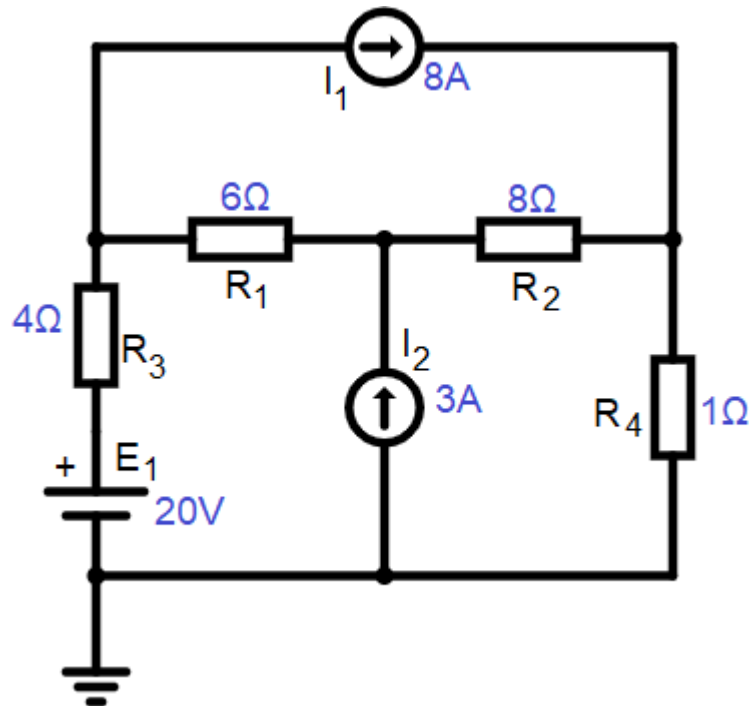Determine current through all resistors using mesh analysis.



Svar:

Since we need to use mesh analysis, we need to assign currents: I_a in top loop, I_b in bottom left loop and I_c in bottom right loop. All currents flow clockwise.

I_a : I_a is equal to I_1 , so $I_a=8A$

I_b and I_c is a supermesh because they have only one current source in between, and $I_b=I_c-3$ or $I_b=I_c-3$

$$I_b+I_c: E_1-R_3 \cdot I_b-R_1(I_b-I_a)-R_2(I_c-I_a)-R_4 \cdot I_c=0$$

$$20-4I_b-6I_b+6 \cdot 8-8I_c+8 \cdot 8-1I_c=0$$

Now I will substitute I_b with I_c-3 (since $I_b=I_c-3$)

$$20-4I_c+12-6I_c+18+48-8I_c+64-1I_c=0$$

$$-19I_c+162=0$$


$$I_c=8.526A$$

Hence, $I_{R4}=I_c=8.526A$, $I_{R3}=I_b=I_c-3=5.526A$, $I_{R1}=I_a-I_b=2.474A$ and $I_{R2}=I_a-I_c=0.526A$

Uppgift 4 [2p]


Bestäm spänningen V_o genom att använda nodanalys.

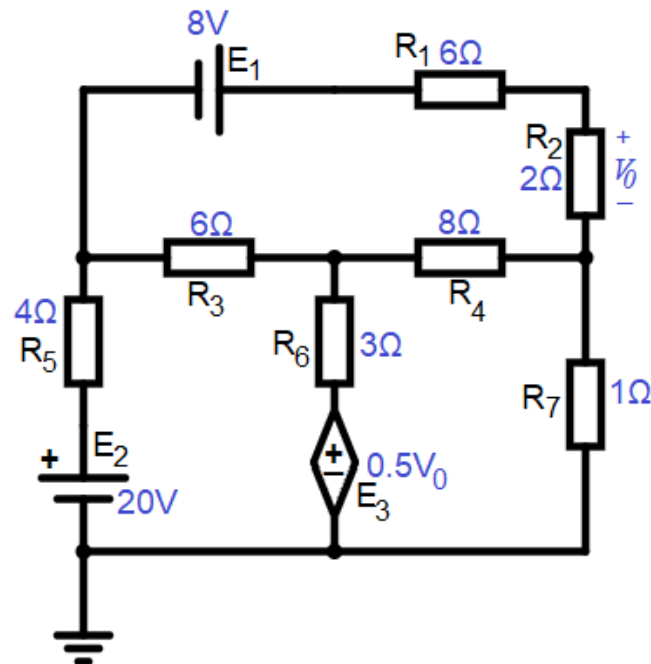Determine the voltage V_o using node analysis.



Svar:

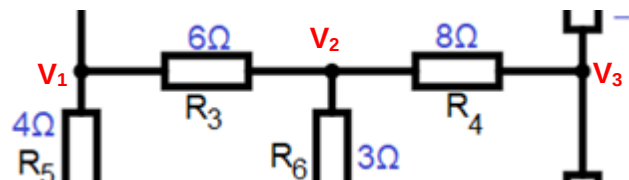The circuit has 3 nodes, all currents will be leaving the nodes.



$$V1: -\frac{V_1-20}{4} - \frac{V_1-V_2}{6} - \frac{V_1+8-V_3}{6+2} = 0$$

We have calculated current over R_2 ($I_{R_2} = \frac{V_1+8-V_3}{6+2}$), so we can get its voltage: $V_o = V_{R_2} = I_{R_2} \cdot R_2 = 2 \cdot \frac{V_1+8-V_3}{6+2} V$.

$$V2: -\frac{V_2-V_1}{6} - \frac{V_2-0.5V_o}{3} - \frac{V_2-V_3}{8} = 0$$

I will keep V_o as a fourth unknown and I will have a system of 4 equations.

$$V3: -\frac{V_3-8-V_1}{6+2} - \frac{V_3-V_2}{8} - \frac{V_3}{1} = 0$$

Solving our system, we get values: $V_1 = 9.04348V$, $V_2 = 3.82609V$, $V_3 = 2.08696V$ and $V_o = 3.73913V$.


Uppgift 5 [3p]

Bestäm driftseffektiviteten η (kvoten mellan den nuvarande effekten och maximal möjlig effekt) för R_1 . [2.5p]

Bestäm nuvarande resistansen R_1 . [0.5p]


Determine operating efficiency η (ratio of the actual power to maximum possible power) of R_1 . [2.5p]

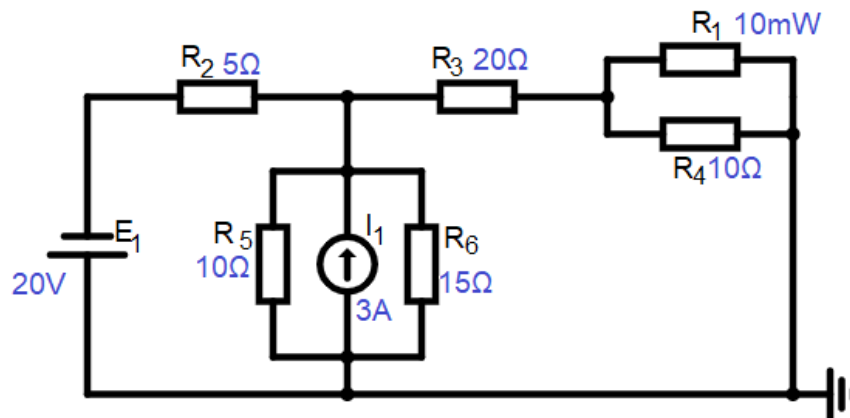Determine current resistance of R_1 . [0.5p]



Svar:

We need to find maximum possible power, and the formula for it is $P_{max} = \frac{E_{Th}^2}{4 \cdot R_{Th}}$. Hence, we will need to solve using Thevenin theorem. Before doing we can simplify the network a little bit. R_5 and R_6 are in parallel, so their combine resistance is $10//15=6\Omega$. And the current source with the parallel 6Ω resistor we can transform into voltage source $3A \cdot 6\Omega = 18V$ with a 6Ω resistor in series. We can calculate R_{Th} by as resistance between terminals a and b with short-circuited all voltage sources. $R_{Th} = R_4 // (R_3 + R_2 // 6\Omega) = 6.944\Omega$.

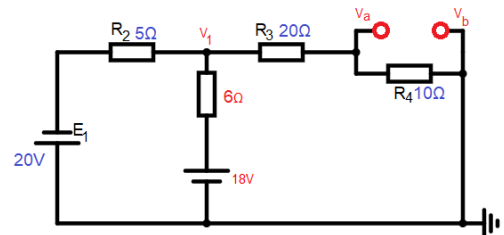

E_{Th} is $V_a - V_b$ and since V_b is grounded and equal zero, $E_{Th} = V_a$. We will use nodal analysis to solve it. While there is only one real node V_1 , I will use two nodes: V_1 and V_a . All currents are leaving nodes.

$$V_1: -\frac{V_1+20}{5} - \frac{V_1-18}{6} - \frac{V_1-V_a}{20} = 0 \text{ and } V_a: -\frac{V_a-V_1}{20} - \frac{V_a}{10} = 0$$

Solving two equations we get an answer: $V_1 = -2.5V$ and $V_a = -0.833V$. Hence $E_{Th} = -0.833V$.

$$P_{max} = \frac{E_{Th}^2}{4 \cdot R_{Th}} = \frac{(-0.833)^2}{4 \cdot 6.944} = 0.025W \text{ and } \eta = \frac{P_{now}}{P_{max}} = \frac{0.01}{0.025} = 0.4 \text{ or } 40\%.$$

To find resistance of R_1 , we will work in Thevenin equivalent circuit: $0.833V$ voltage source, 6.944Ω resistor and R_1 in series. We know that $P_{R1} = VI = I^2 R$. I is the same all over the circuit and equal to voltage source divided by total resistance: $I = \frac{0.833}{6.944 + R_1}$. Now combining these, we get that

$$P_{R1} = \left(\frac{0.833}{6.944 + R_1} \right)^2 \cdot R_1 = \frac{0.833^2 \cdot R_1}{(6.944 + R_1)^2} = 0.01$$

$$0.833^2 \cdot R_1 = 0.01 \cdot (6.944 + R_1)^2 = 0.01 \cdot (6.944^2 + 2 \cdot 6.944 \cdot R_1 + R_1^2)$$

$$-0.01 \cdot R_1^2 + 0.833^2 \cdot R_1 - 0.01 \cdot 2 \cdot 6.944 \cdot R_1 - 0.01 \cdot 6.944^2 = 0$$

$$R_1^2 - 55.501R_1 + 48.219 = 0$$

$$R_1 \text{ is equal to } 0.883\Omega \text{ or } 54.618\Omega$$