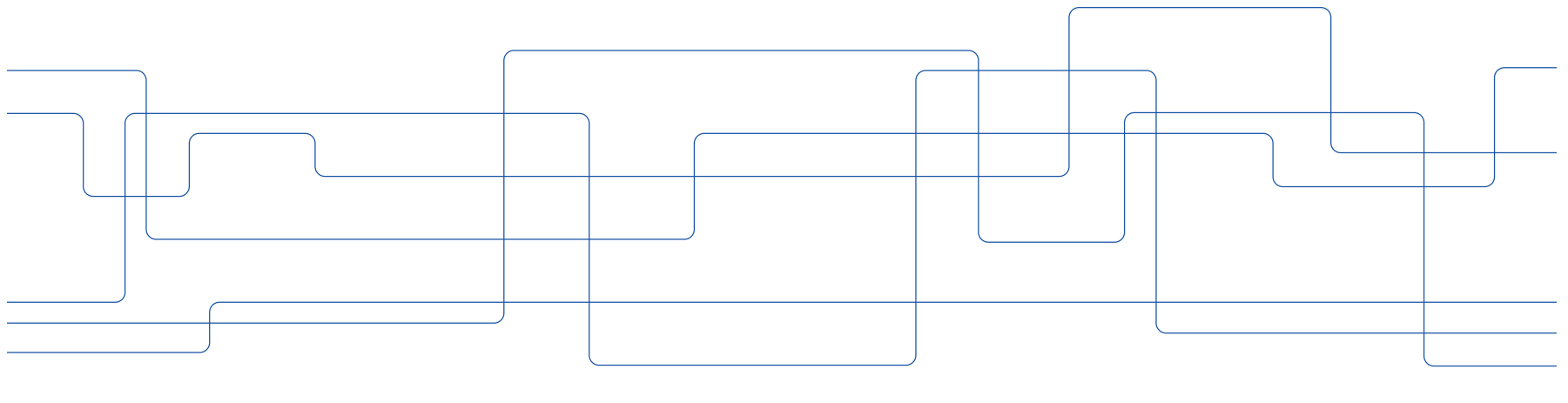







HE1027 Electrical Principals

Capacitors and Inductors




Electric Field

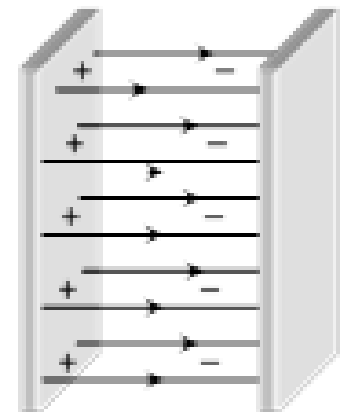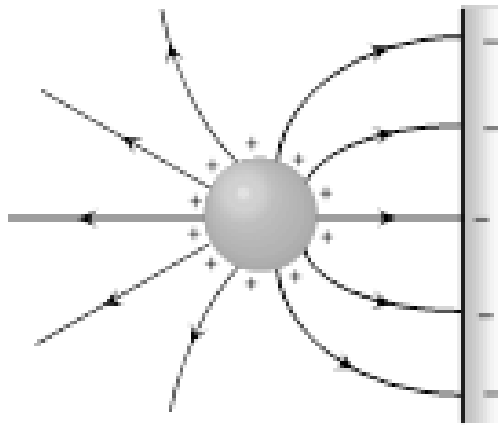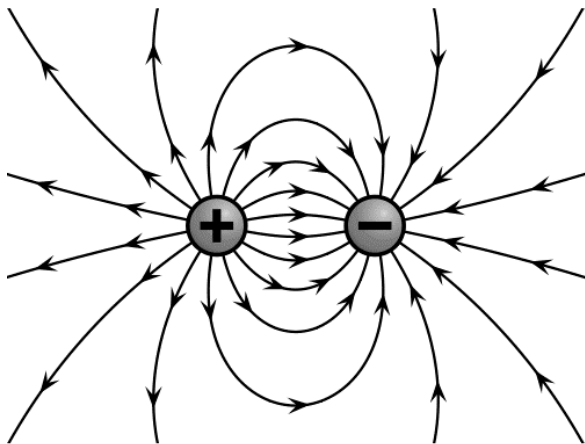- Around each point in space when charge is present in any form exists an electric field
- The strength of electric field is drawn using electric flux lines
- Electric flux lines always go from a positively charged points to negative
- Electric flux lines always go from a perpendicular to charged surfaces



Capacitor (*kondensator*)

- If two parallel plates are connected to a circuit, these plates will collect a charge
- These plates separated by a gap are known as capacitors
- **Take two electrical conductors and separate them with an insulator and you make a capacitor**
- Capacitors store electrical energy
 - adding electrical energy to a capacitor is called charging
 - releasing the energy from a capacitor is known as discharging
 - a capacitor generally releases its energy much more rapidly (ex. flash camera)

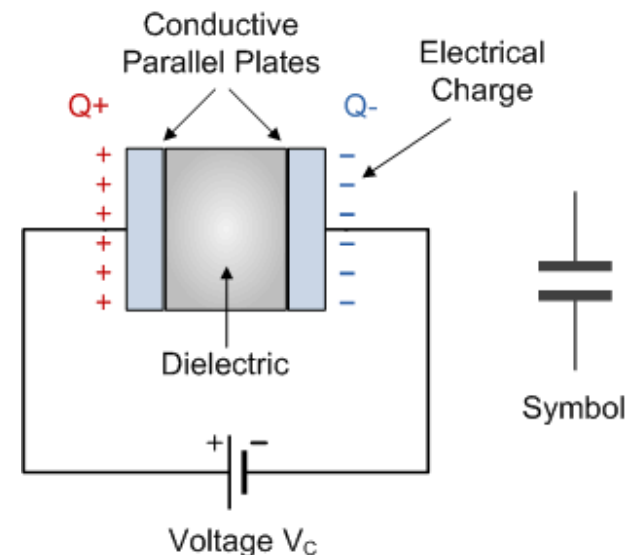



Capacitance

- Capacitance is a measure of a capacitor's ability to store charge on it (to store capacity)
- Capacitance is measured in units called farads: 1-farad capacitor can store one coulomb of charge at 1 volt:


$$C(\text{capacitance}) = \frac{Q(\text{charge})}{V(\text{voltage})}$$

A 1-farad capacitor would typically be pretty big. It might be as big as a can of tuna or a 1-liter soda bottle, depending on the voltage it can handle. For this reason, capacitors are typically measured in microfarads

- Capacitance value and depends upon three main factors:
 - the type of material which separates the two plates (ϵ)
 - surface area of conductive plates (A)
 - distance between the two plates (d)



$$C = \epsilon \frac{A}{d}$$

Charging Phase in Capacitive Network

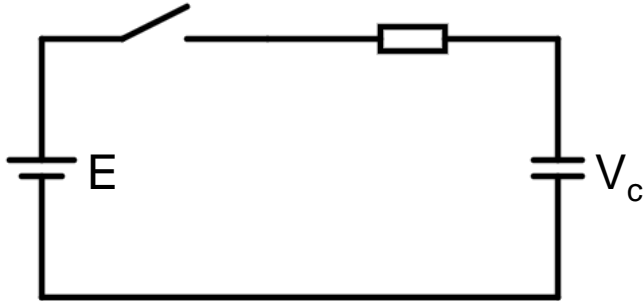


Time	E	V_c	$E - V_c$	Current
0	100	0	100	Really fast
1	100	50	50	Fast
2	100	80	20	Medium
3	100	90	10	Slow
4	100	95	5	Very slow
5	100	96	4	Very slow
6	100	97	3	Very slow
7	100	98	2	Very slow
8	100	99	1	Very slow
9	100	100	0	Stopped

Concept of t_{0-} and t_{0+}

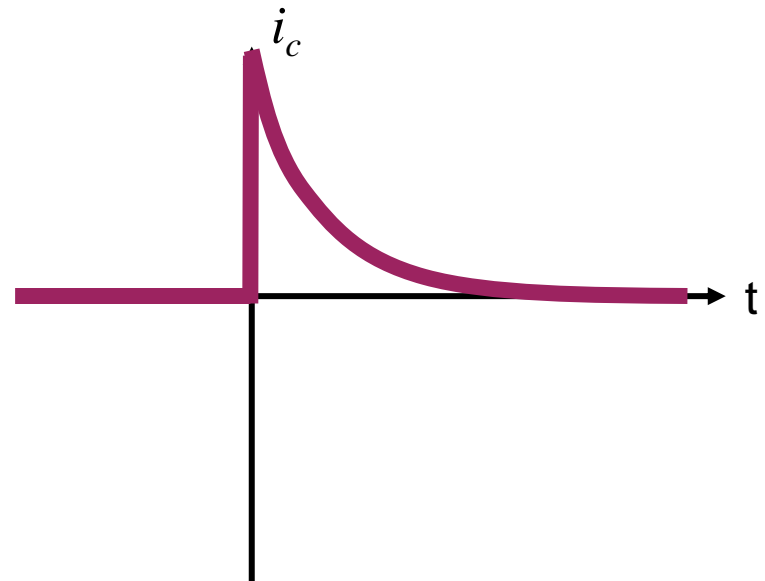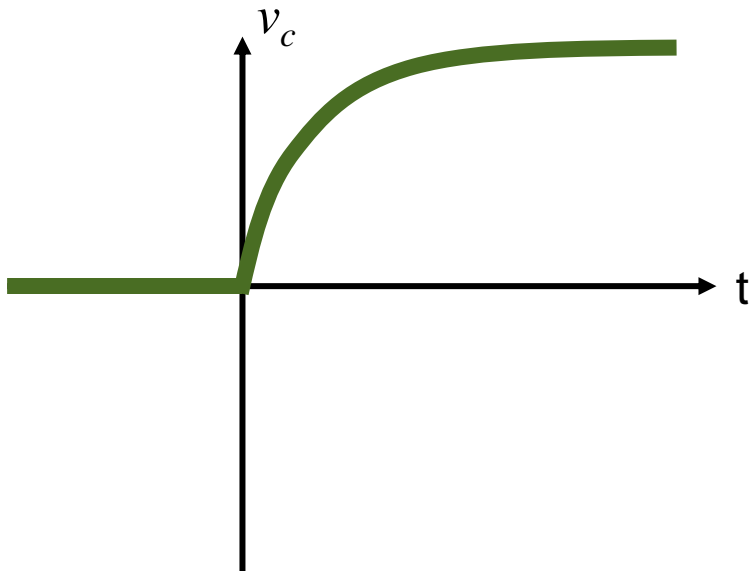

Switching between Contacts

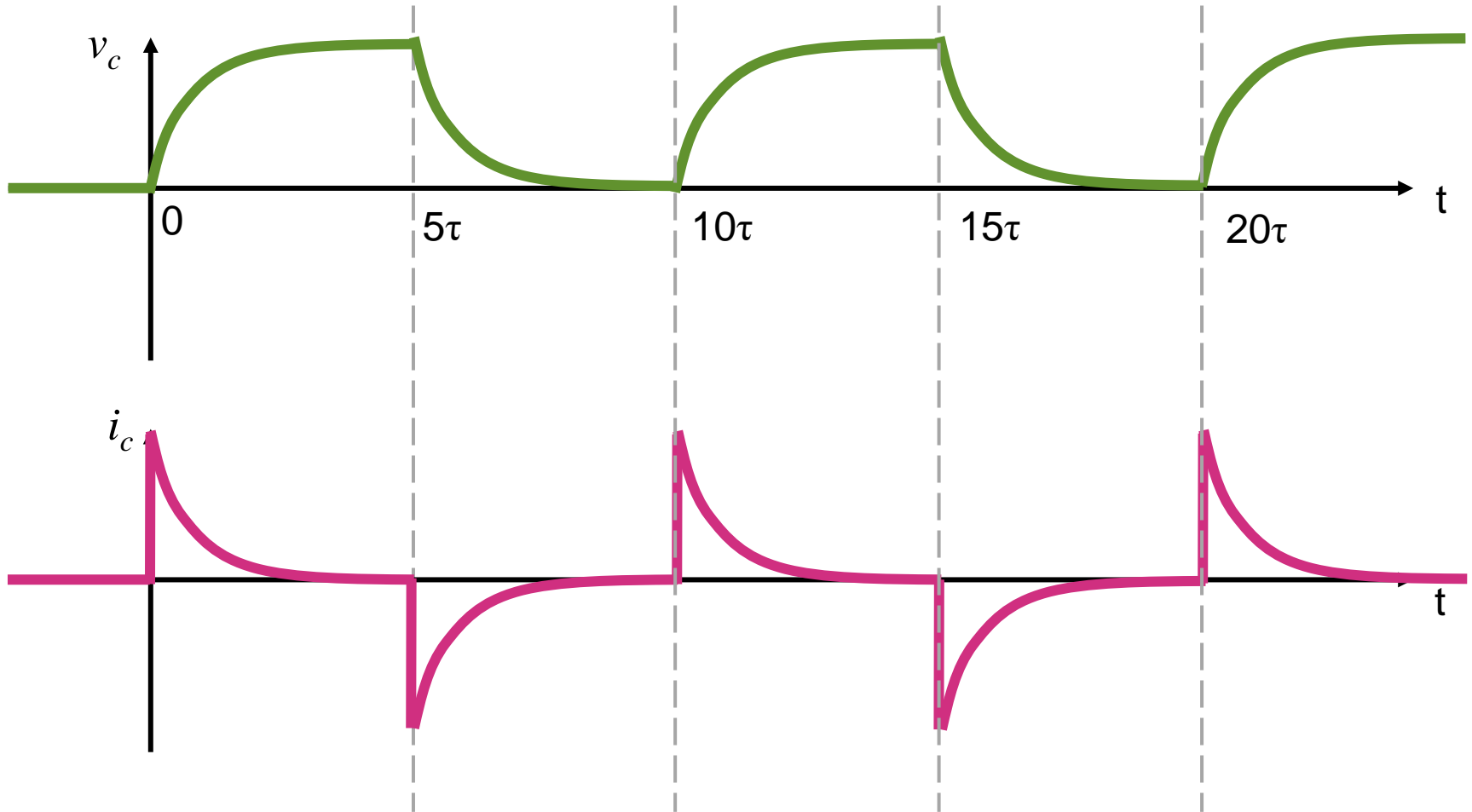



R-C Circuit

RC circuit is a circuit with both a resistor (R) and a capacitor (C)

Time constant τ (tau)	$\tau = RC$
Voltage of charging capacitor over time with an initial value $V_{initial}$	$v_c(t) = V_{final} + (V_{initial} - V_{final})e^{-\frac{t}{\tau}}$
Voltage of charging capacitor over time with no initial value ($V_{initial}=0$ and $V_{final}=E$)	$v_c(t) = E + (0 - E)e^{-\frac{t}{\tau}} = E\left(1 - e^{-\frac{t}{\tau}}\right)$
Voltage of discharging capacitor over time	$v_c(t) = E - E\left(1 - e^{-\frac{t}{\tau}}\right) = Ee^{-\frac{t}{\tau}}$
Current of capacitor over time	$i_c(t) = \frac{E}{R} = \frac{E}{R}e^{-\frac{t}{\tau}}$
Voltage of a resistor over time	$v_r(t) = i_c R = \left(\frac{E}{R}e^{-\frac{t}{\tau}}\right)R = Ee^{-\frac{t}{\tau}}$
Math constant e	$e \approx 2.718$



R-C Circuit

$$v_c = E(1 - e^{-t/\tau})$$

$$i_c = \frac{E}{R} e^{-t/\tau}$$

$$t=0$$

$$v_c = E(1 - e^0) = E(1 - 1) = 0V$$

$$i_c = (E/R) * e^0 = (E/R) * 1 = E/R$$

$$t=\tau$$

$$\begin{aligned} v_c &= E(1 - e^{-\tau/\tau}) = E(1 - e^{-1}) = \\ &= E(1 - 0.368) = 0.632E \end{aligned}$$

$$i_c = (E/R) * e^{-\tau/\tau} = 0.368 * (E/R)$$

$$t=2\tau$$

$$\begin{aligned} v_c &= E(1 - e^{-2\tau/\tau}) = E(1 - e^{-2}) = \\ &= E(1 - 0.135) = 0.865E \end{aligned}$$

$$i_c = (E/R) * e^{-2\tau/\tau} = 0.135 * (E/R)$$

$$t=5\tau$$

$$\begin{aligned} v_c &= E(1 - e^{-5\tau/\tau}) = E(1 - e^{-5}) = \\ &= E(1 - 0.007) = 0.993E \approx E \end{aligned}$$

$$i_c = (E/R) * e^{-5\tau/\tau} = 0.007 * (E/R) \approx 0$$

R-C Circuit

A capacitor is a short-circuit at the moment when a switch is just closed

$$i_c = \frac{E}{R} e^{-t/\tau}$$

$t=0$

$$v_c = E(1 - e^0) = E(1 - 1) = 0V$$

$$i_c = (E/R) * e^0 = (E/R) * 1 = E/R$$

$t=\tau$

$$v_c = E(1 - e^{-1}) = E(1 - 0.368) = 0.632E$$

During charging, the major change in voltage and current happens during the first time constant

$$i_c = 0.368 * (E/R)$$

$t=2\tau$

$$v_c = E(1 - e^{-2\tau/\tau}) = E(1 - e^{-2}) = 0.865E$$

$$i_c = (E/R) * e^{-2\tau/\tau} = 0.135 * (E/R)$$

The charging phase of a capacitor has essentially ended after 5 time constants

The current is essentially 0A after 5 time constants

$t=5\tau$

$$v_c = E(1 - e^{-5\tau/\tau}) = E(1 - e^{-5}) = E(1 - 0.007) = 0.993E \approx E$$


$$i_c = (E/R) * e^{-5\tau/\tau} = 0.007 * (E/R) \approx 0$$

A capacitor is an open-circuit at the moment when it is fully charged



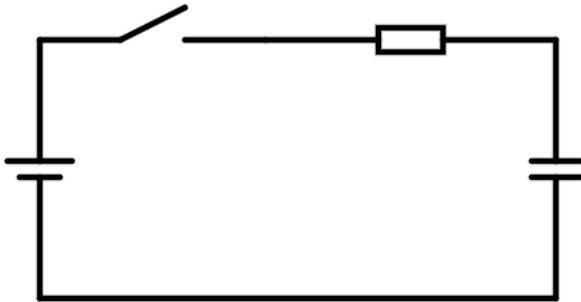Example:

Find voltage of capacitor 50ms after the connection if $E=20V$, $C=4\mu F$ and $R=5k\Omega$



Determine time τ

$$\tau = RC = 4\mu F * 5k\Omega = 0.02s$$

Determine v_c

$$v_c(t) = V_{final} + (V_{initial} - V_{final})e^{-\frac{t}{\tau}}$$

$$v_c(t) = 20 + (0 - 20)e^{-\frac{t}{\tau}}$$


$$v_c(0.05) = 20 - 20e^{-\frac{0.05}{0.02}}$$

$$v_c(0.05) = 20 - 20e^{-2.5}$$


$$v_c(0.05) = 20 - 1.64$$

$$v_c(0.05) = 18.36V$$

Capacitors in Series and Parallel

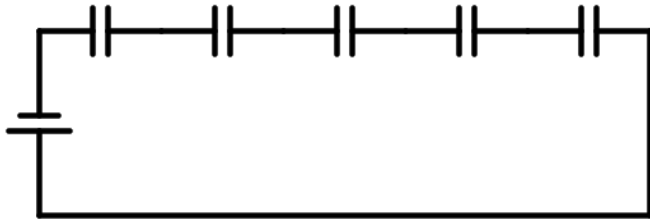
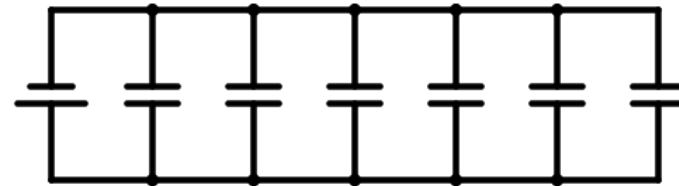
$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4} + \dots + \frac{1}{C_n}$$



$$C_T = C_1 + C_2 + C_3 + C_4 + \dots + C_n$$



Inductor (*spole*)

- Current flowing through a conductor generates a magnetic field
 - The magnetic field starts out small, as current yet flows in only part of the conductor. Once steady current is established, magnetic field quantity will be stable
 - Magnetic field stores charge
 - Faraday's law of induction says that we should have very long conductor as a coil for best result. A magnet inside the coil will help. Such element is called inductor
 - Inductance L
 - Used for signal filtering, sensors, dynamics
 - Two inductors form a transformer
-




R-L curcuit

Time constant $\tau = \frac{L}{R}$

Current of an inductor over time with an initial value $I_{initial}$

$$i_L(t) = I_{final} + (I_{initial} - I_{final})e^{-\frac{t}{\tau}}$$


$$I_{final} = \frac{E}{R_{Total}}$$

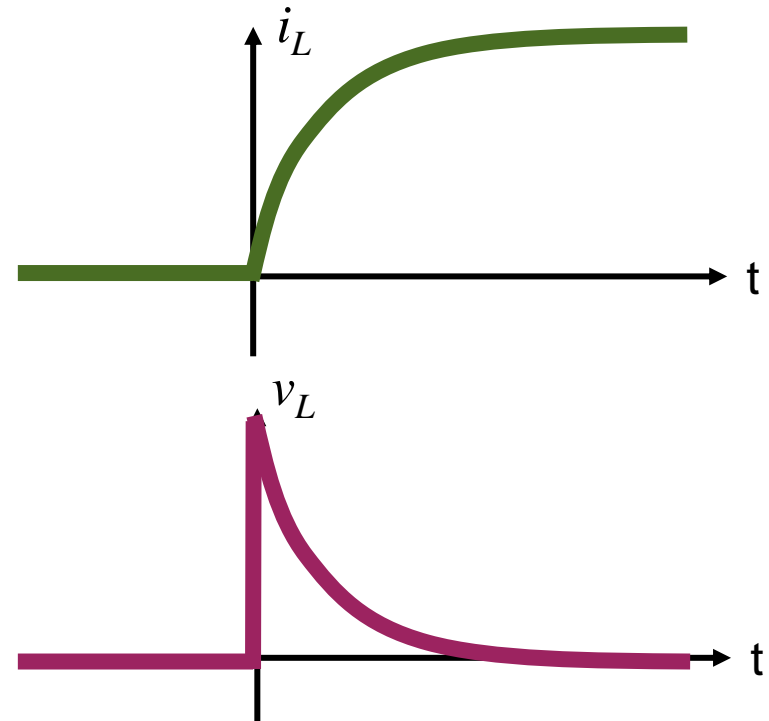

Inductors in Series and Parallel




$$L = L_1 + L_2 + L_3$$

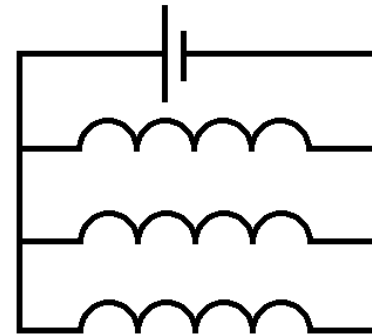



$$\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

Inductor and Magnetic Field

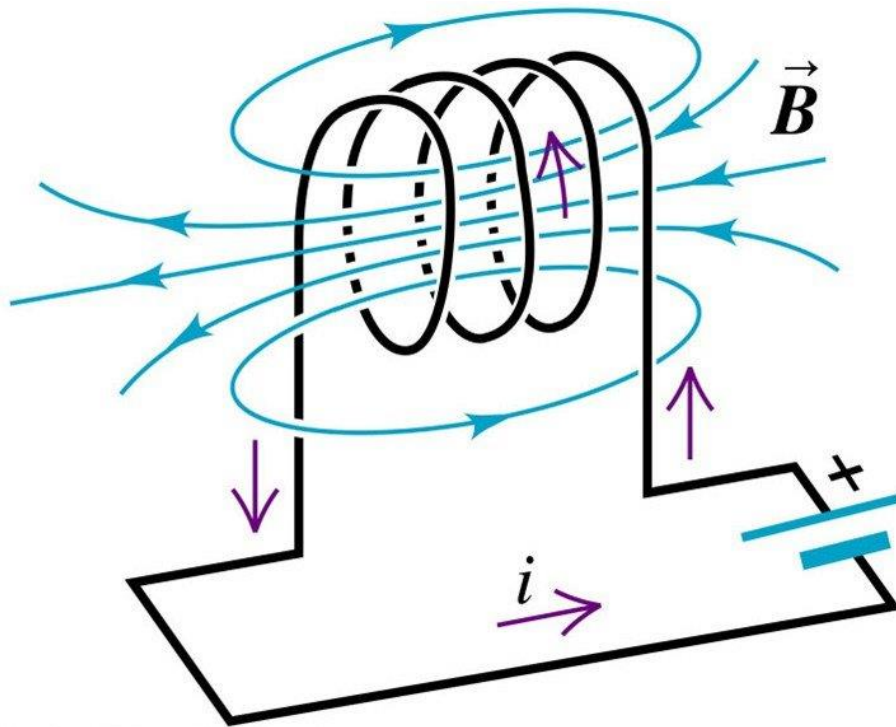


- Movement of electrons causes magnetic field
- BECAUSE electrons and magnetic field are friends
- SO moving magnetic field causes movement of electrons



Transformer

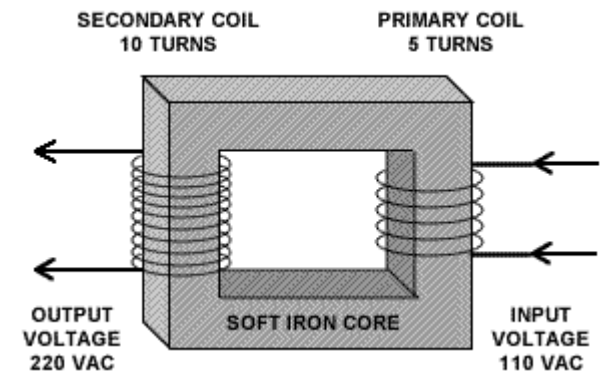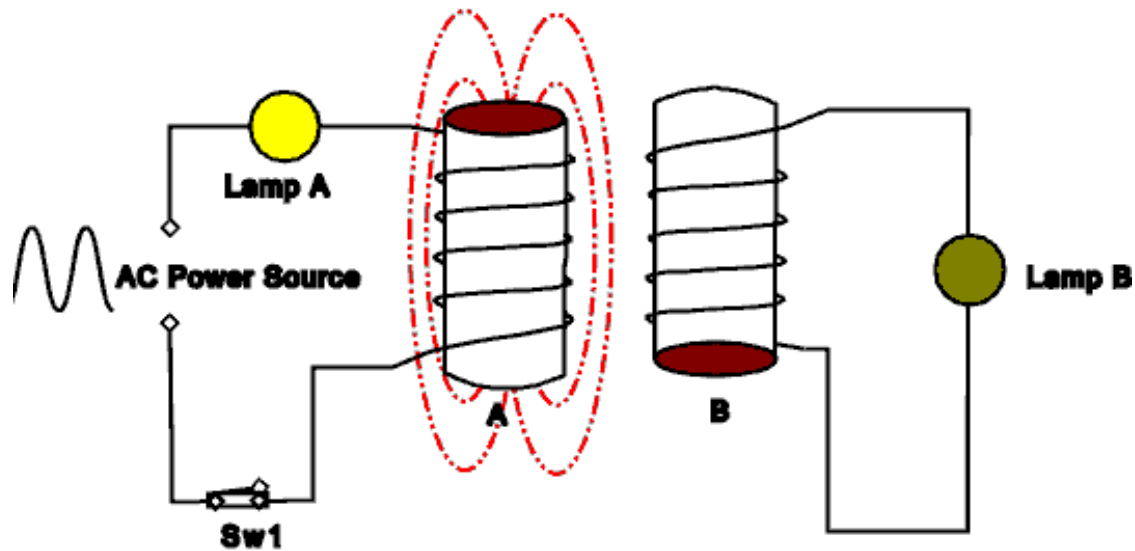



Magnet Produces Electricity

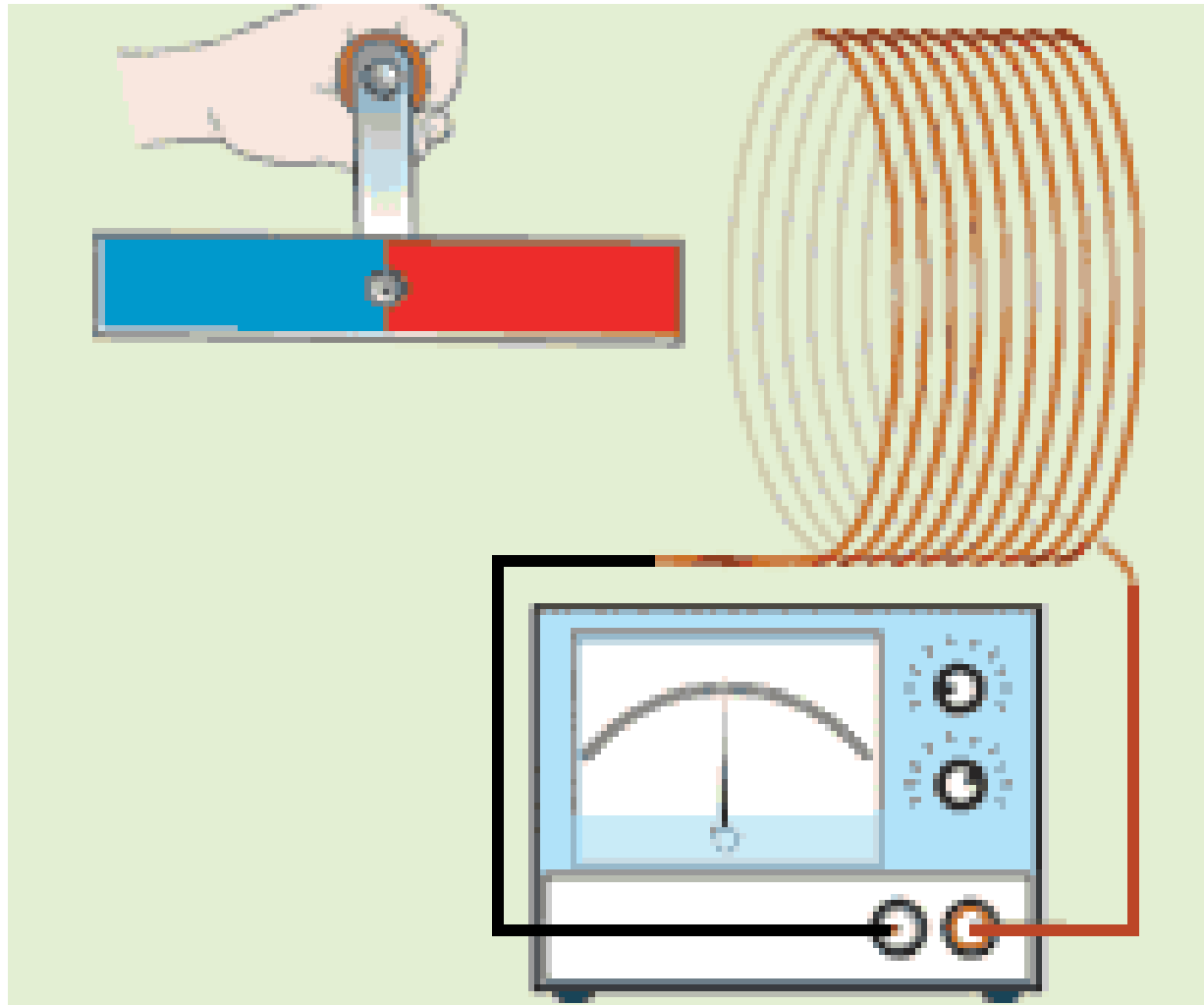

One Phase Electricity

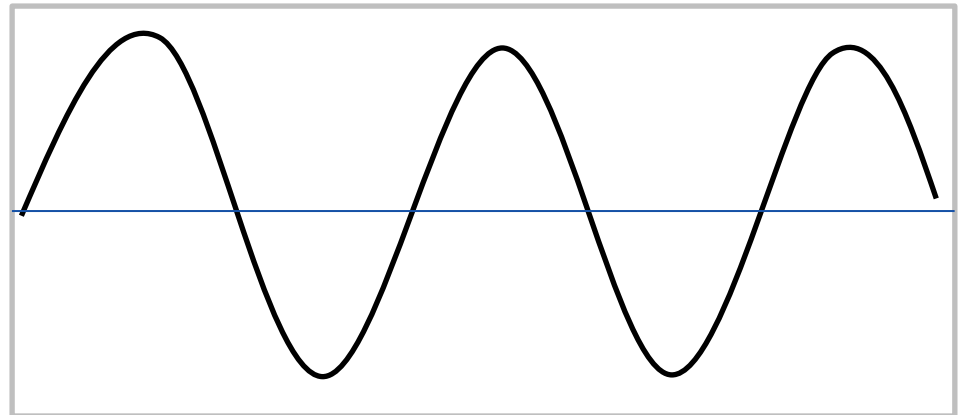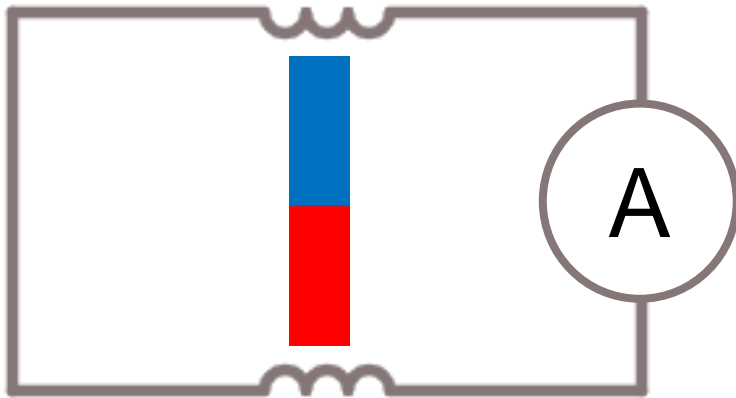

Three Phase Electricity

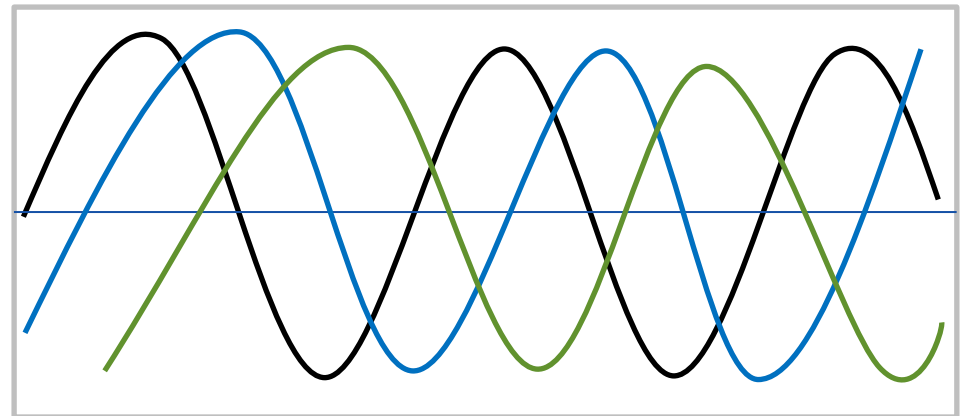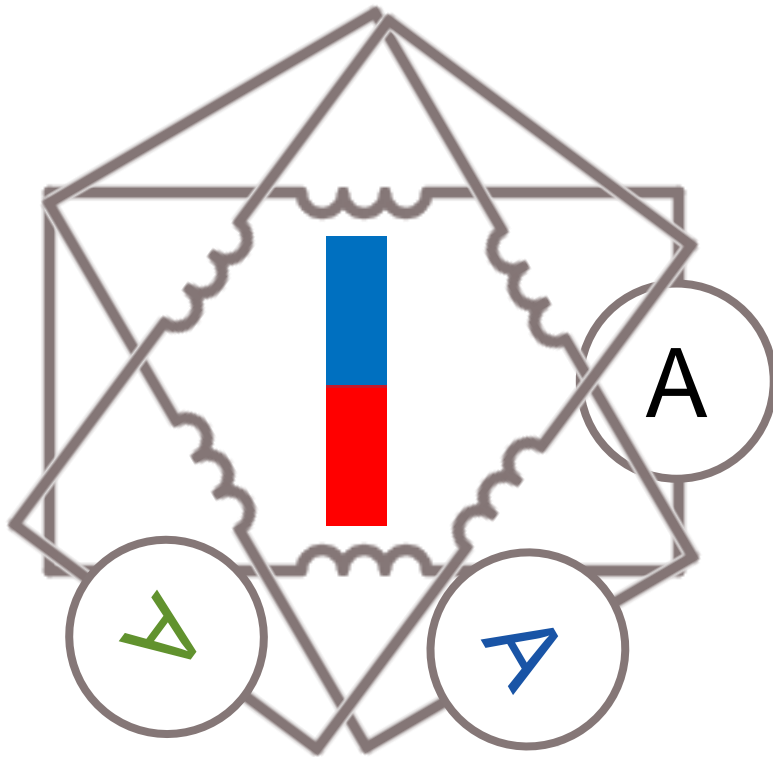



Suggested reading

Introductory Circuit Analysis

- Kap 10: 10.2 - 10.4, **10.5 - 10.9**, 10.11 - 10.13
- Kap 11: 11.2 - 11.3, **11.4 - 11.8**, 11.9 - 11.12
- Kap 23: 23.1 - 23.3
- Kap 24: 2



Suggested exercises

- Capacitors (kapitel 10): 19, 21, 25, 29, 37, 42, 43
- Inductors (kapitel 11): 11, 13, 15, 17, 21, 23, 24