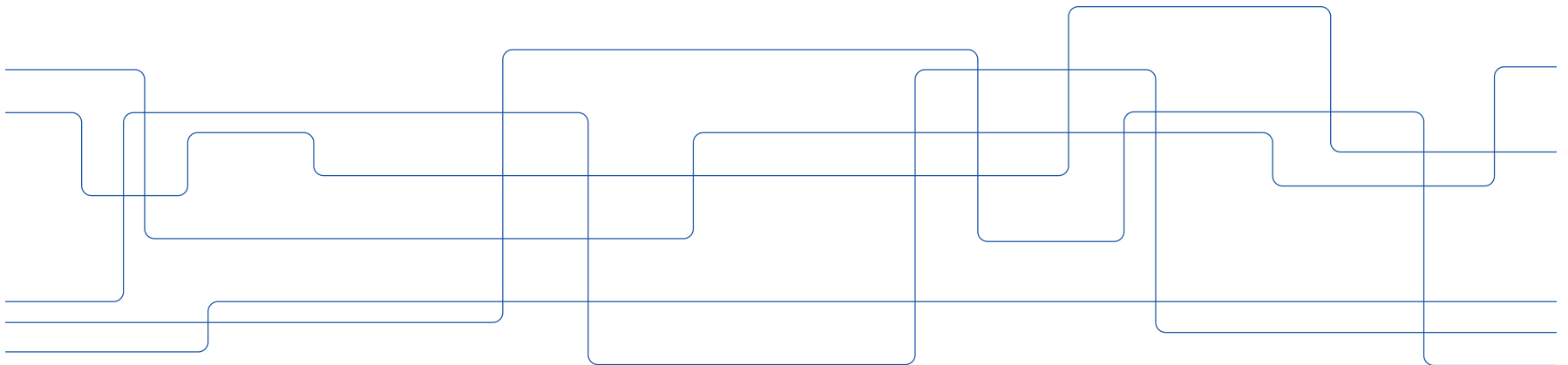




HE1027 Electrical Principals

Series and Parallel AC Circuits



Inductor in AC Current

Voltage across the inductor is directly related to the inductance of the coil and the rate of change of current through the coil

$$V_L = L \frac{di_L}{dt}$$


From before, instantaneous value of current $i = I_m \sin \alpha = I_m \sin \omega t$
and $\frac{d}{dt}(\sin 2x) = 2\cos 2x$

$$V_L = L \frac{d}{dt} I_m \sin \omega t = L I_m \frac{d}{dt} (\sin \omega t) = L I_m (\omega \cos \omega t) = \omega L I_m \sin(\omega t + 90^\circ)$$

$\omega L = X_L$ - reactance of an inductor

$$X_L = \frac{V_m}{I_m}$$

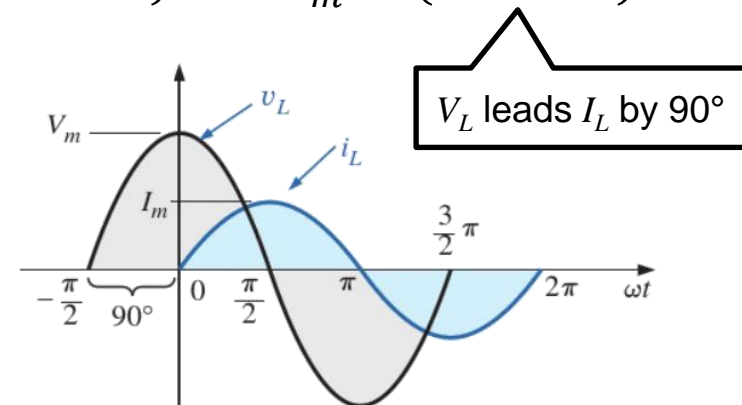Since v_L leads i_L by 90° , impedance of inductive element is $Z_L = X_L \angle 90^\circ = iX_L$



Capacitor in AC Current

The capacitive current is directly related to the rate of the voltage across the capacitor and the rate of change of involved voltage

$$i_C = C \frac{dV_C}{dt}$$


From before, instantaneous value of voltage $v = V_m \sin \alpha = V_m \sin \omega t$

$$i_C = C \frac{d}{dt} V_m \sin \omega t = CV_m (\omega \cos \omega t) = \omega C V_m \sin(\omega t + 90^\circ)$$


$$\frac{1}{\omega C} = X_C \text{ - reactance of a capacitor}$$

$$X_C = \frac{V_m}{I_m}$$

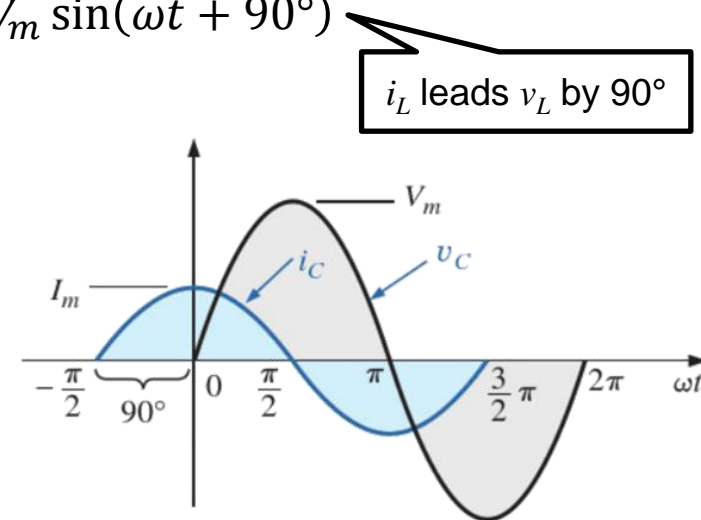Since i_C leads v_C by 90° , impedance of capacitive element is $Z_C = X_C \angle -90^\circ = -iX_C$




Impedance Diagram

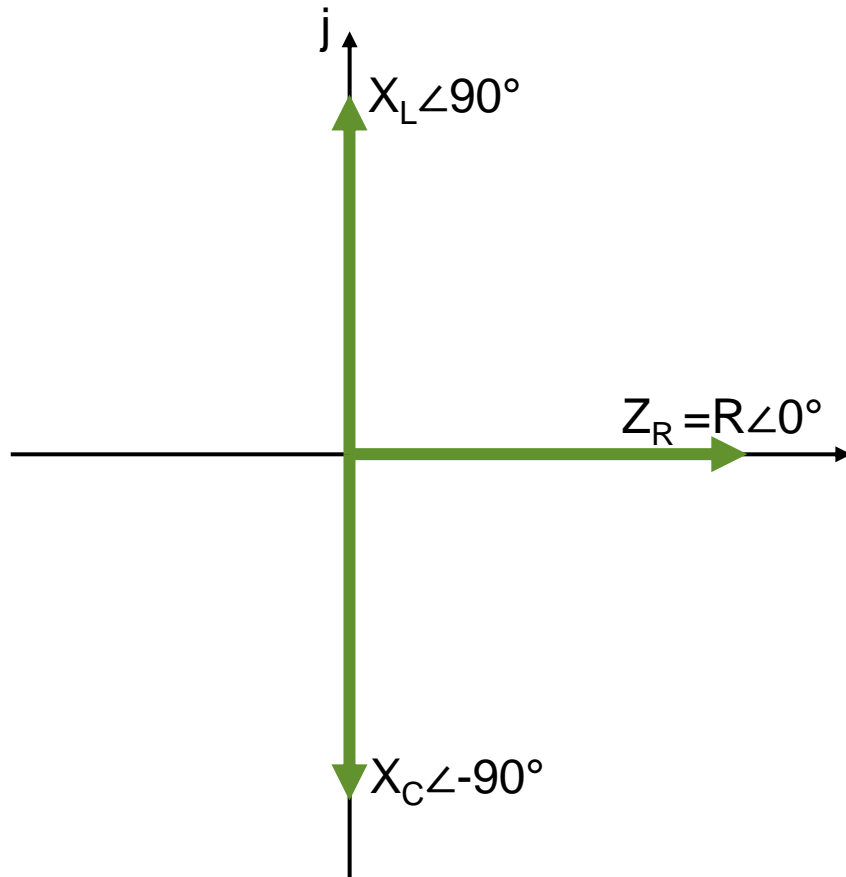


- Combination of different elements will have total impedances that extend from -90° to $+90^\circ$
- If the total impedance is close to 0° , it is resistive in nature
- If it is closer to 90° , it is inductive in nature
- If it is closer to -90° , it is capacitive in nature

Frequency and Inductor

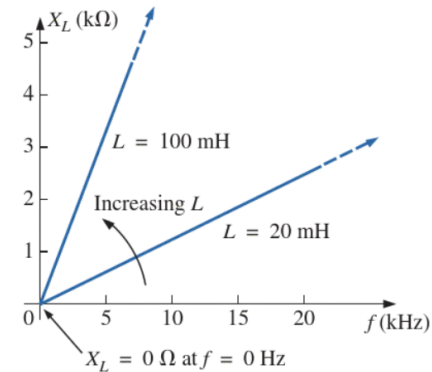
- $\omega = 2\pi f$
- $X_L = \omega L = 2\pi f L$



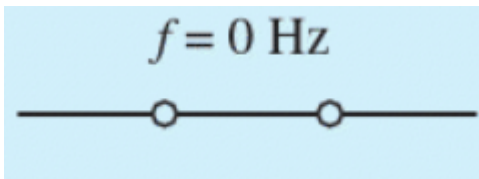
If $f=0\text{Hz} \rightarrow X_L=0\Omega$



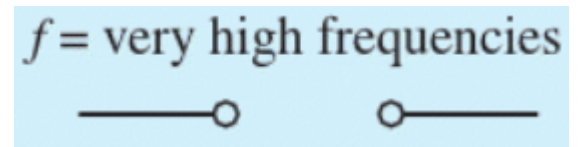If $f=\infty\text{Hz} \rightarrow X_L=\infty\Omega$




Reality:

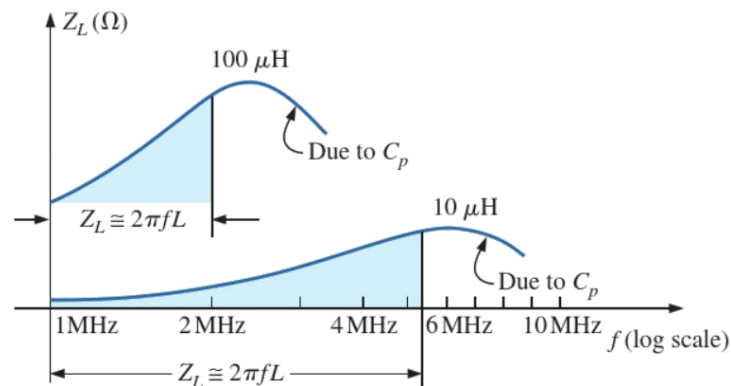


Frequency and Capacitor

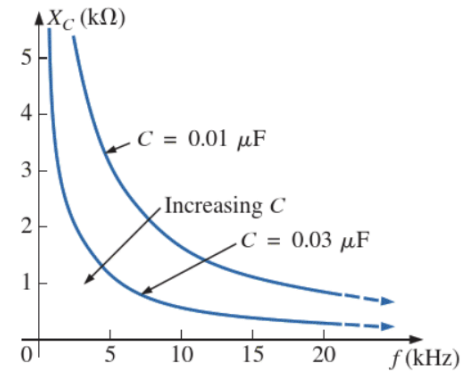
$$\bullet X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$



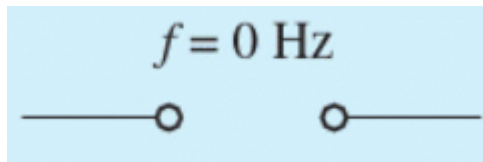
If $f=0Hz \rightarrow X_C = \infty \Omega$



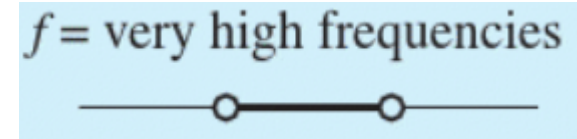If $f=\infty Hz \rightarrow X_C = 0\Omega$




Reality:

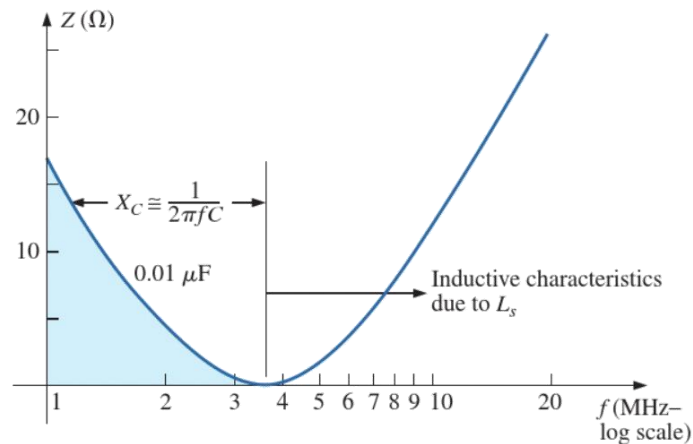

Series Configuration

- Total impedance is a sum of all individual impedences

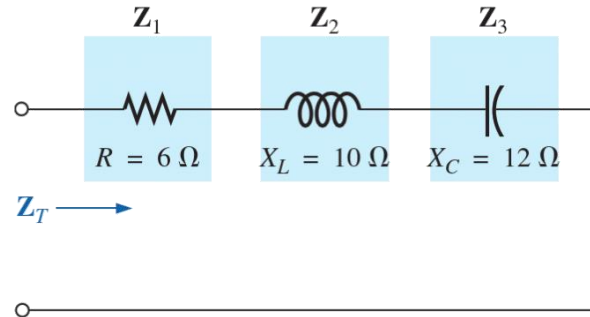
$$Z_T = Z_1 + Z_2 + Z_3 + Z_4 + \dots + Z_n$$



- $Z_T = Z_1 + Z_2 + Z_3 = R + iX_L - iX_C = 6 + i10 - i12 = 6\Omega - i2\Omega$ $Z_T = 6.32\Omega \angle -18.43^\circ$
- $I_T = I_1 = I_2 = I_3 = \dots = I_n$
- $E = V_1 + V_2 + V_3 + V_4 + \dots + V_n$
- $P = EI^* \cos|\theta_E - \theta_I|$

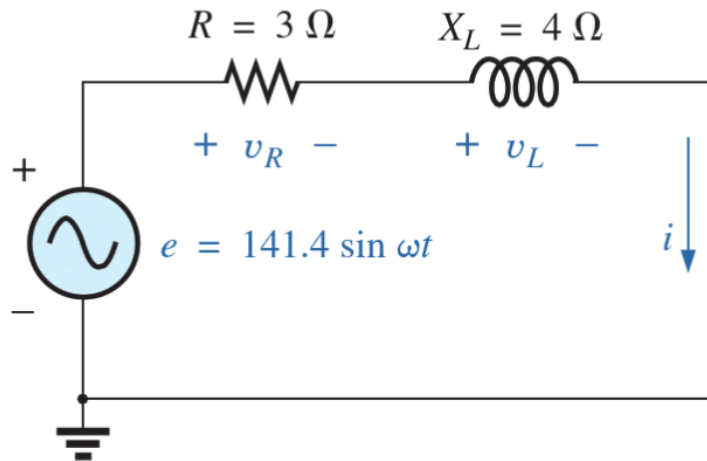Example

Find total impedance, current, V_R , V_L and P_T .
Draw Impedance Diagram



1. Convert e into phasor notation

$$e = 141.4 \sin \omega t = 100 \angle 0^\circ$$

2. Find total impedance

$$Z_T = Z_R + Z_L = 3 \Omega + i4 \Omega = 5 \Omega \angle 53.13^\circ$$

3. Find current

$$I = E/Z_T = (100 \angle 0^\circ) / (5 \angle 53.13^\circ) = 100/5 \angle (0^\circ - 53.13^\circ) = 20 A \angle -53.13^\circ$$

4. Find V_R


$$V_R = I Z_R = 20 A \angle -53.13^\circ \cdot 3 \Omega \angle 0^\circ = 60 V \angle -53.13^\circ$$

5. Find V_L

$$V_L = I Z_L = 20 A \angle -53.13^\circ \cdot 4 \Omega \angle 90^\circ = 80 V \angle 36.87^\circ$$




6. Find P_T

$$P_T = EI \cos |\theta_E - \theta_I| = 100 \cdot 20 \cdot \cos |0^\circ - 53.13^\circ| = 2000 \cdot \cos(53.13^\circ) = 1200 W$$

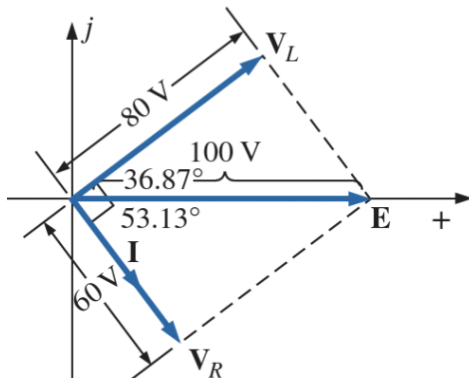

Frequency Response for Series AC Circuits

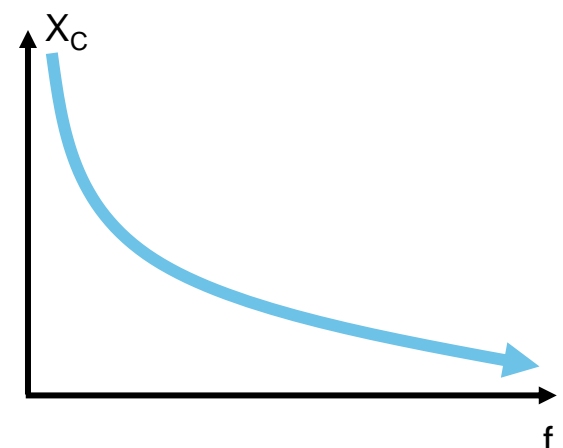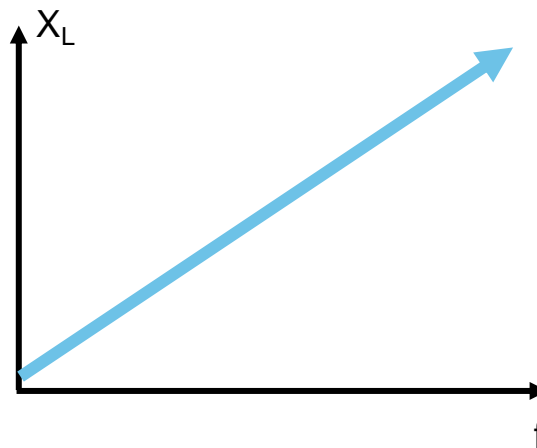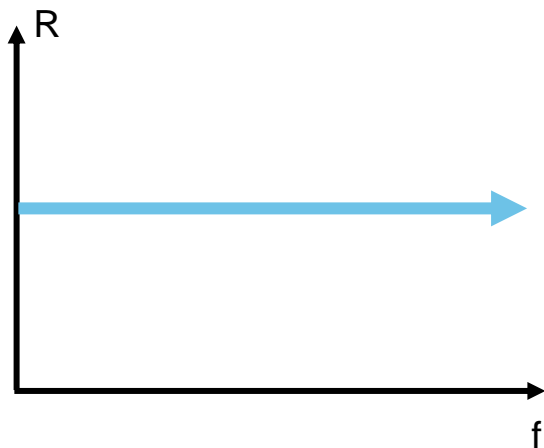
- For ideal resistor frequency has no effect
- $X_L = 2\pi fL$
- $X_C = \frac{1}{2\pi fC}$




In series connection, element with largest impedance has the greatest impact

Series R-C (Resistor-Capacitor) AC Circuit






- $Z_T = Z_1 + Z_2$

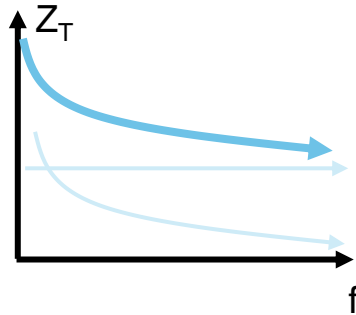

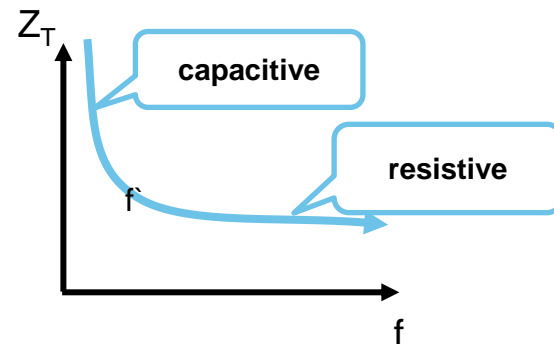
- At low frequency impedance of capacitor has a larger impact
- At high frequency impedance of resistor has a larger impact
- Breaking point is at $X_c = R$
- Since $X_C = \frac{1}{2\pi f C}$, then $f' = \frac{1}{2\pi RC}$



R-C low pass filter and high pass filter

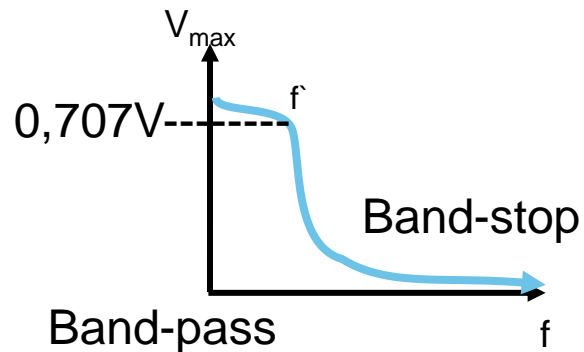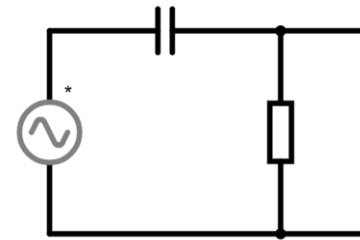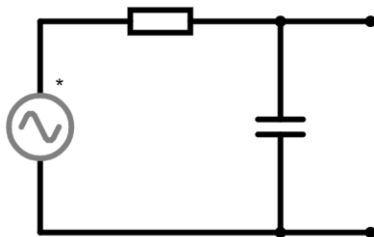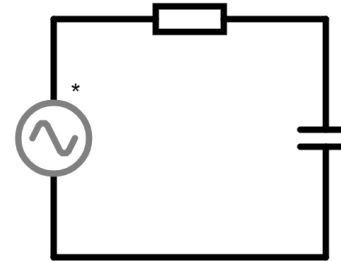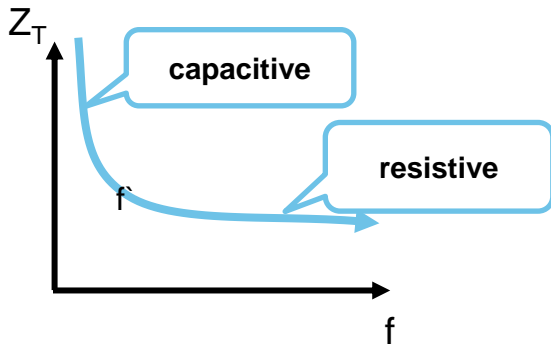


RC low pass filter

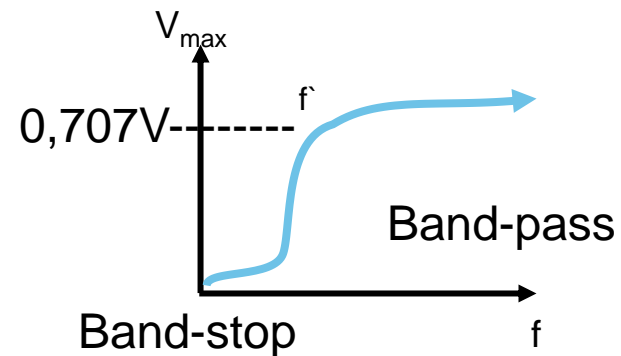


RC high pass filter

Series R-L (Resistor-Inductor) AC Circuit






- $Z_T = Z_1 + Z_2$

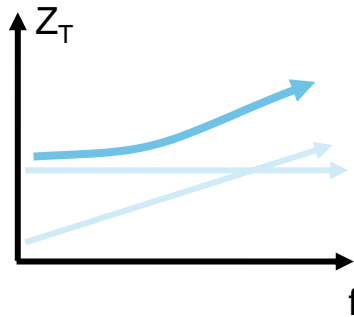

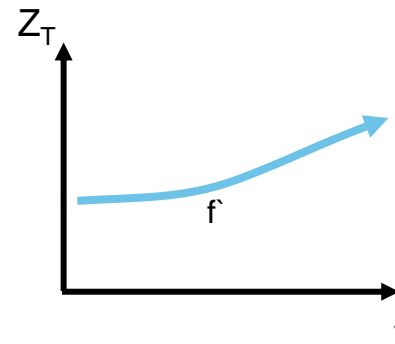
- At low frequency impedance of resistor has a larger impact
- At high frequency impedance of inductor has a larger impact
- Breaking point is at $X_L = R$
- Since $X_L = 2\pi fL$, then $f' = \frac{R}{2\pi L}$



R-L low pass filter and high pass filter

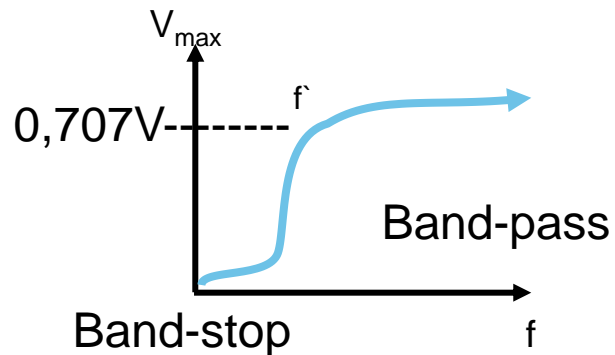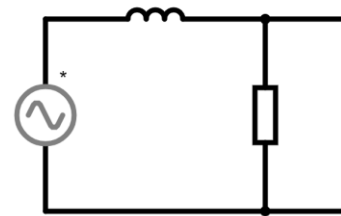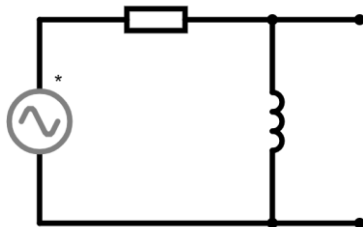
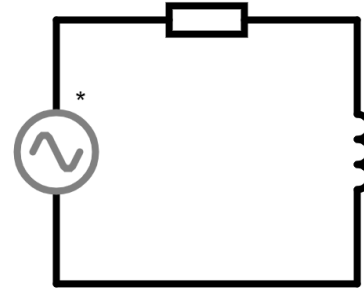
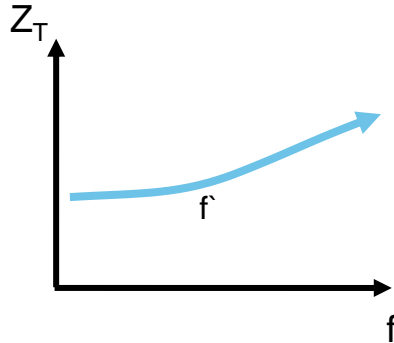


RL high pass filter

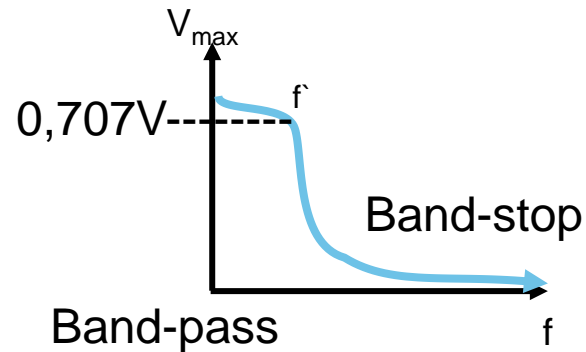


RL low pass filter

Band-pass filter and band-stop filter

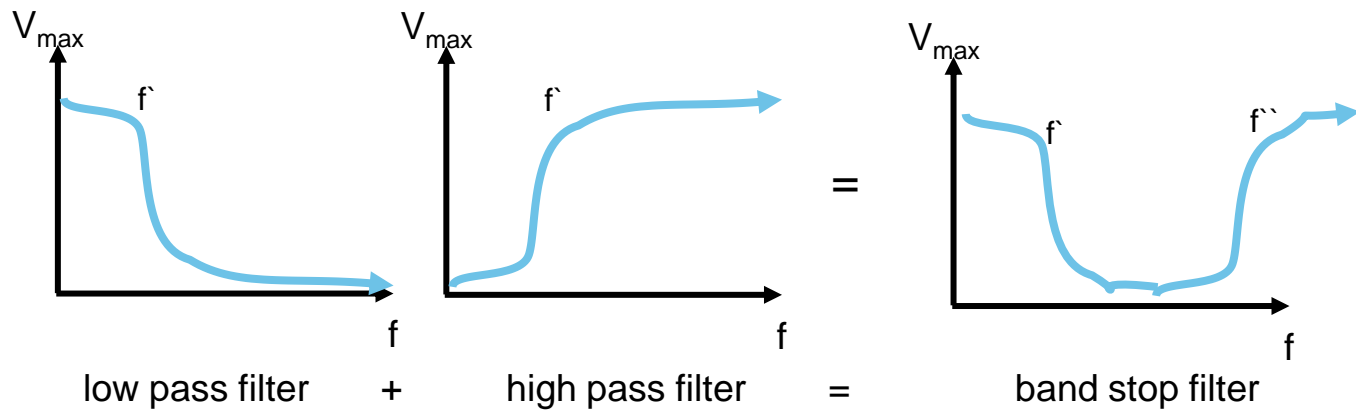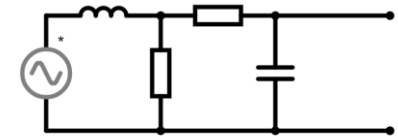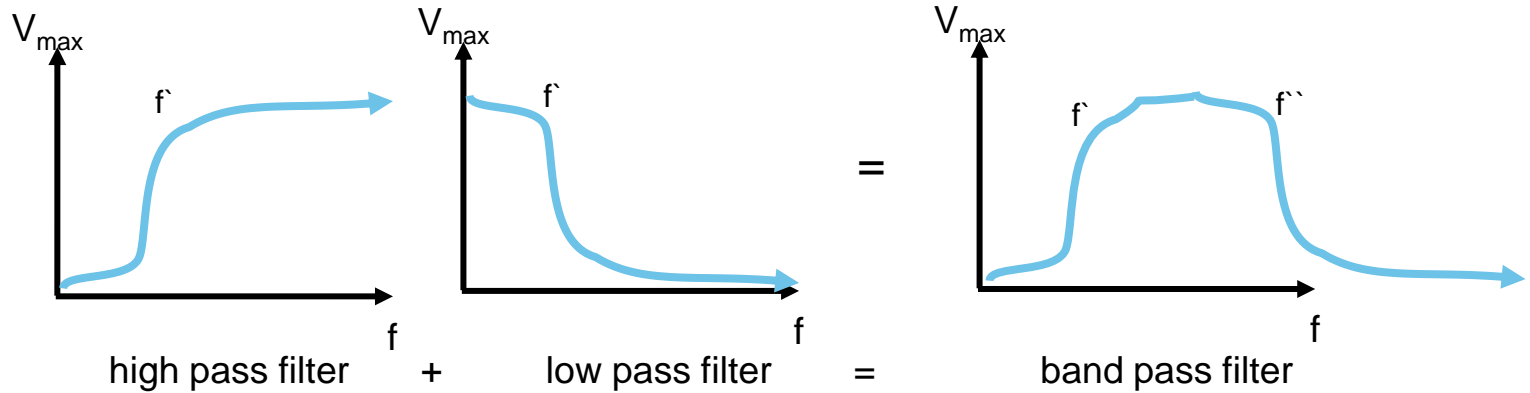



Series R-L-C (Resistor-Inductor-Capacitor) AC Circuit

- $Z_T = Z_1 + Z_2 + Z_3$

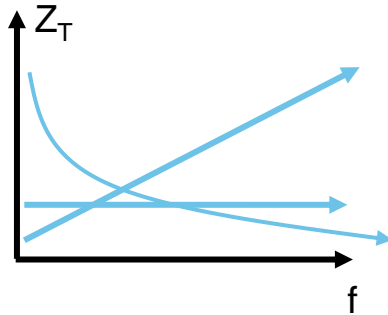

- Since resistor don't change over time it basically just ignored
- At low frequency impedance of capacitor has a larger impact
- At high frequency impedance of inductor has a larger impact

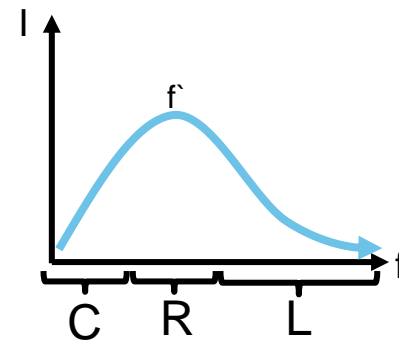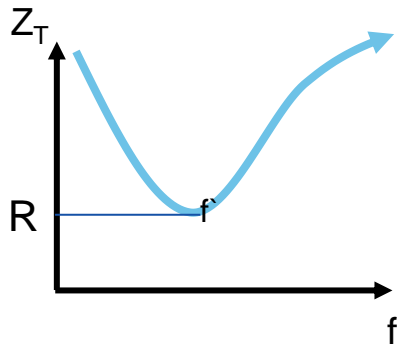- Breaking point is at $X_L = X_C \rightarrow 2\pi fL = \frac{1}{2\pi fC} \rightarrow f' = \frac{1}{2\pi\sqrt{LC}}$




Parallel Configuration

$$\frac{1}{Z_T} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots + \frac{1}{Z_n}$$

$$E = V_1 = V_2 = V_3 = \dots = V_n$$


$$I_T = I_1 + I_2 + I_3 + \dots + I_n$$

$$P = EI^* \cos|\theta_E - \theta_I|$$

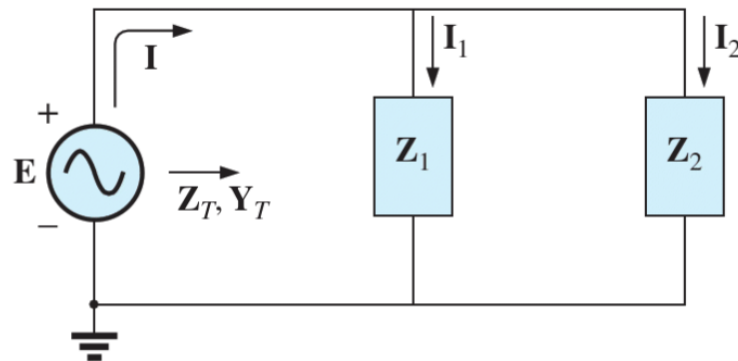

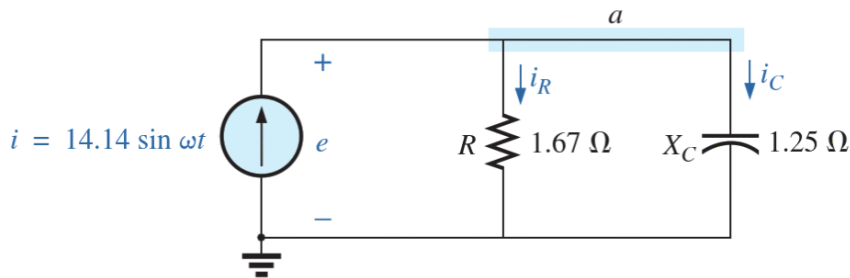Example

Find total impedance, current, V_R , V_L and P_T .
Draw Impedance Diagram



1. Convert i into phasor notation

$$i = 14.14 \sin \omega t = 10 \angle 0^\circ$$


2. Find total impedance

$$1/Z_T = 1/Z_R + 1/Z_C = 1/1.67\Omega + 1/j1.25\Omega = 0.599\Omega + j0.8\Omega$$

$$Z_T = 1 \Omega \angle -53.13^\circ$$

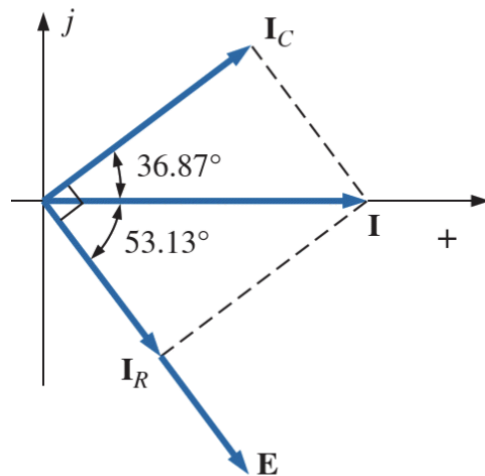3. Find voltage

$$E = I \cdot Z_T = (10 \angle 0^\circ) \cdot (1 \angle -53.13^\circ) = 10 \angle -53.13^\circ$$



4. Find I_R

$$I_R = E/Z_R = (10 \angle -53.13^\circ) / (1.67 \angle 0^\circ) = 6 \angle -53.13^\circ$$

5. Find I_C



$$I_C = E/Z_C = (10 \angle -53.13^\circ) / (1.25 \angle -90^\circ) = 8 \angle 36.87^\circ$$

6. Find P_T

$$P_T = EI \cos |\theta_E - \theta_I| = 10 \cdot 10 \cdot \cos |-53.13^\circ - 0^\circ| = 100 \cdot \cos(53.13^\circ) = 60 \text{ W}$$

Parallel R-L (Resistor-Inductor) AC Circuit

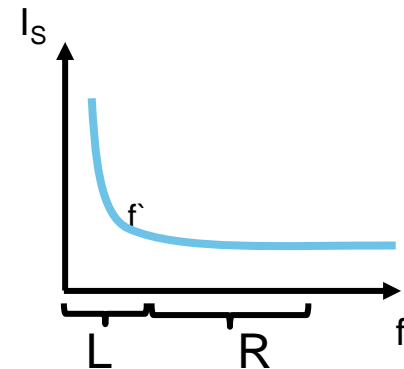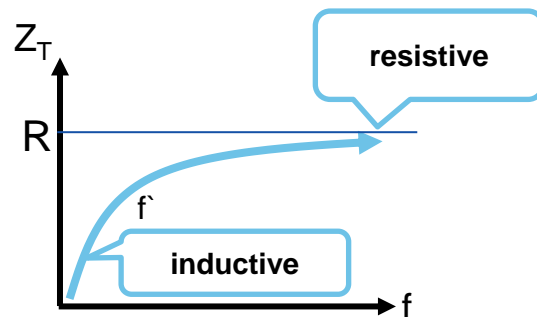
- $1/Z_T = 1/Z_1 + 1/Z_2$
- In parallel connection, element with smallest impedance has the greatest impact
- At low frequency impedance of inductor has a larger impact
- At high frequency impedance of resistor has a larger impact
- Breaking point is at $X_L = R$
- Since $X_L = 2\pi fL$, then $f' = \frac{R}{2\pi L}$





Parallel R-C (Resistor-Capacitor) AC Circuit

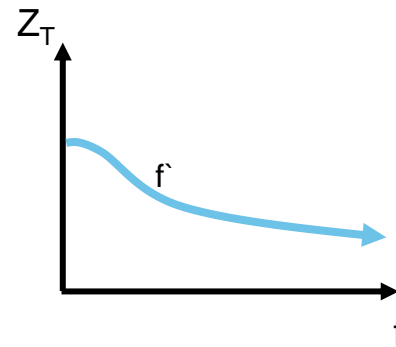- $Z_T = Z_1 + Z_2$
- At low frequency impedance of resistor has a larger impact
- At high frequency impedance of capacitor is larger than of capacitor
- Breaking point is at $X_C = R$
- Since $X_C = \frac{1}{2\pi f C}$, then $f' = \frac{1}{2\pi R C}$



Resonance

- $Z_L = 2\pi fL$




- $Z_C = \frac{1}{2\pi fC}$

At 159.155Hz:

$$Z_L = 2\pi * 159.155 * 0.1 = 100\angle 90^\circ$$

$$Z_C = \frac{1}{2\pi * 159.155 * 0.0001} = 100\angle -90^\circ$$
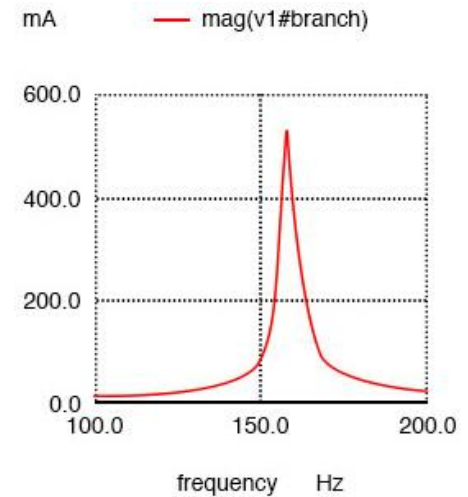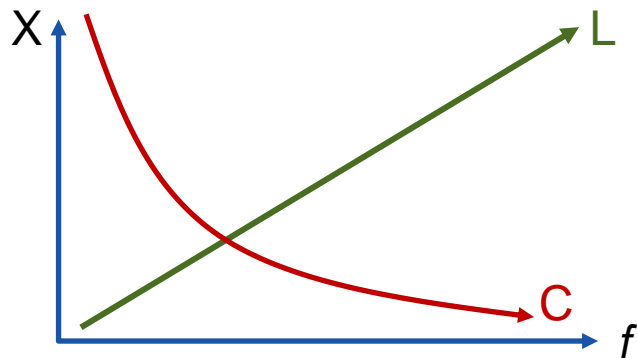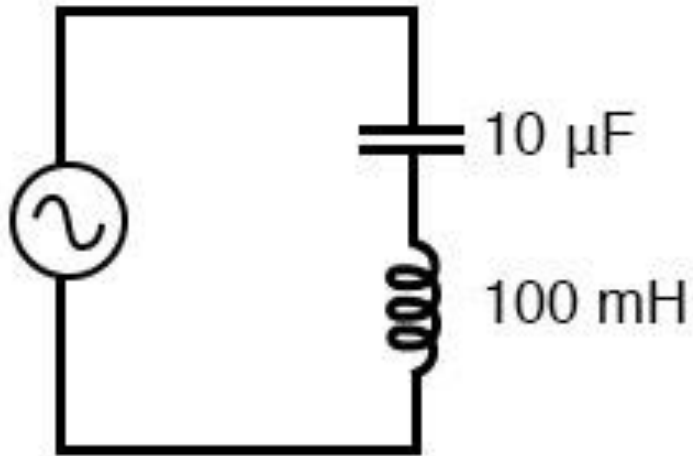
$$Z_T = 100\angle 90^\circ + 100\angle -90^\circ = 0\Omega$$





Suggested reading

Introductory Circuit Analysis

- Kap 14: **14.2 - 14.9**
- Kap 22: 22:1-22.8, 22.11



Suggested exercises

- Kap 14: 5, 17, 35, 37, 39, 41, 43, 49, 53, 55
- Kap 22: 19, 21, 23, 25