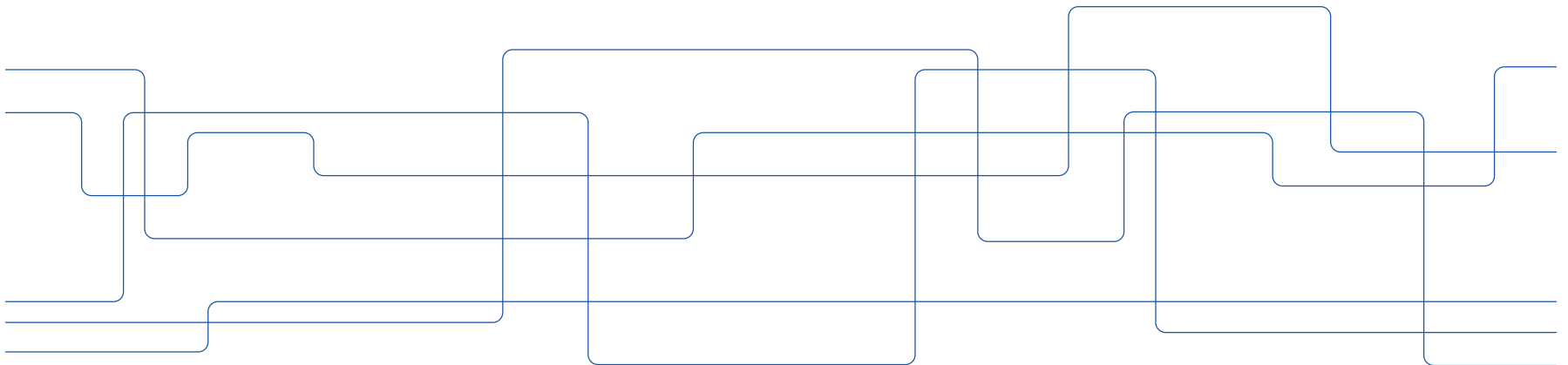





HE1027 Electrical Principals


AC Circuits Analysis Methods and Theorems



Total Impedance Z_{Total}

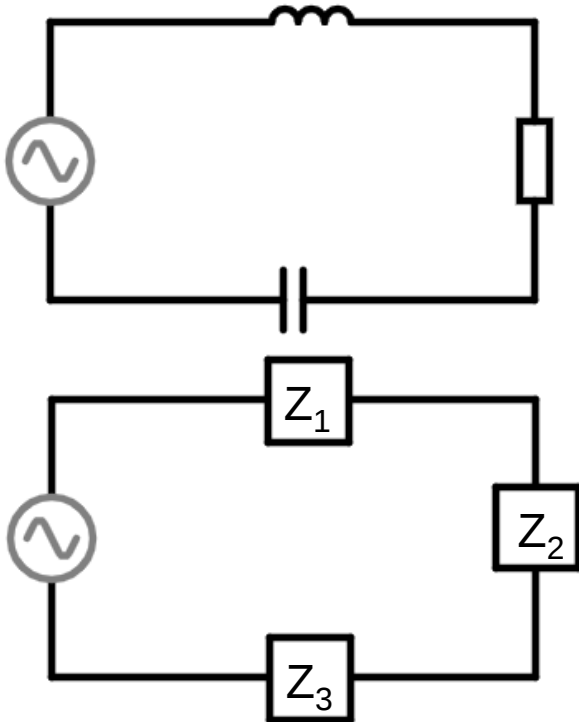

$$Z_{\text{Total}} = Z_1 + Z_2 + Z_3$$

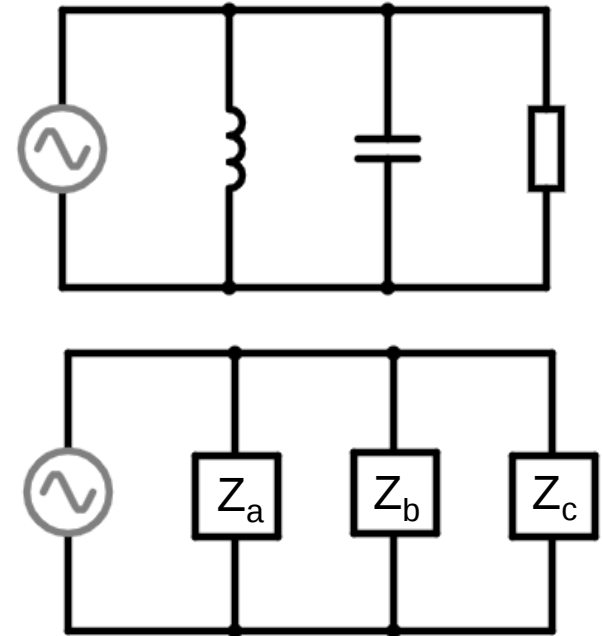


$$\frac{1}{Z_{\text{Total}}} = \frac{1}{Z_a} + \frac{1}{Z_b} + \frac{1}{Z_c}$$



Example

Determine voltage $e(t)$

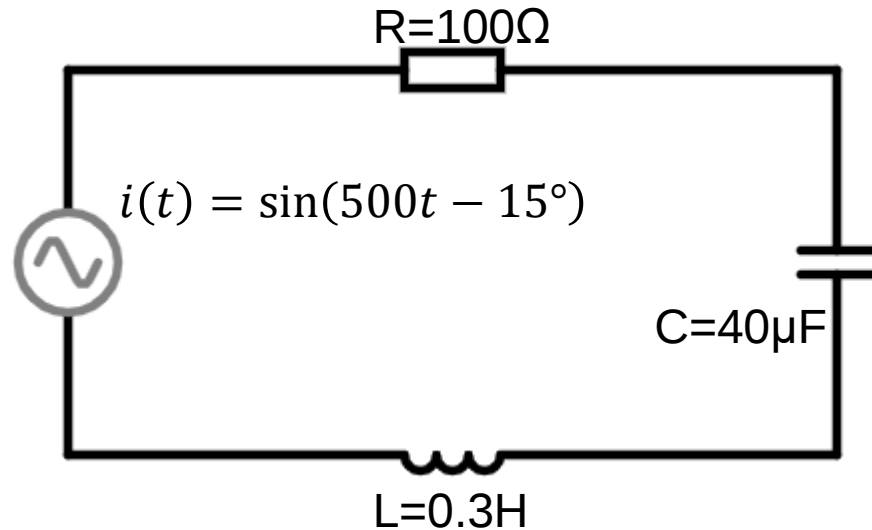

$$I = 0.707 \angle -15^\circ$$

$$\omega = 500 \text{ s}^{-1}$$

$$Z_R = R = 100\Omega$$

$$X_C = 1/\omega C$$

$$Z_C = -iX_C = -i/\omega C = -i/500 * 40^{-6} = -50i \Omega$$

$$Z_L = i\omega L = i * 500 * 0.3 = 150i \Omega$$

$$Z_{\text{total}} = 100 - 50i + 150i = 100 + 100i = 141.42 \angle 45^\circ$$

$$E = I * Z_{\text{total}} = 0.707 \angle -15^\circ * 141.42 \angle 45^\circ = 100 \angle 30^\circ$$


$$e(t) = 141 \sin(500t + 30^\circ)$$

Same logic as for DC networks



Example


Determine voltage E

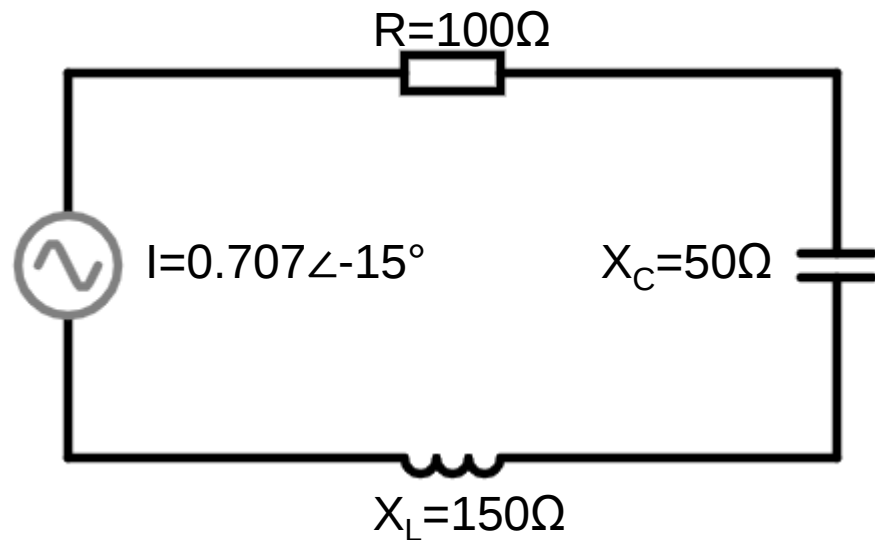

$$Z_{\text{total}} = 100 - 50i + 150i = 100 + 100i = 141.42\angle 45^\circ$$

$$E = I * Z_{\text{total}} = 0.707\angle -15^\circ * 141.42\angle 45^\circ = 100\angle 30^\circ$$

Mesh analysis

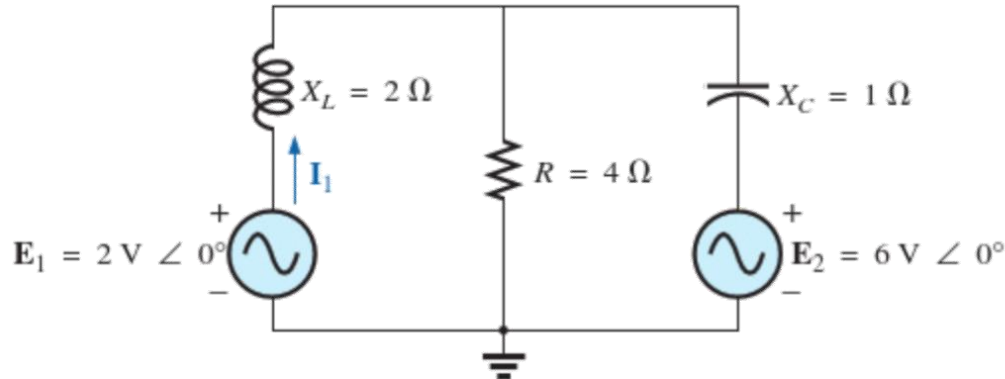

I_1 loop

$$E_1 - Z_L * I_1 - Z_R(I_1 - I_2) = 0$$


$$2 - 2\angle 90^\circ * I_1 - 4I_1 + 4I_2 = 0$$

I_2 loop

$$-Z_R(I_2 - I_1) - Z_C * I_2 - E_2 = 0$$

$$-4I_2 + 4I_1 - 1\angle -90^\circ * I_1 - 6 = 0$$

Mesh analysis with depended source

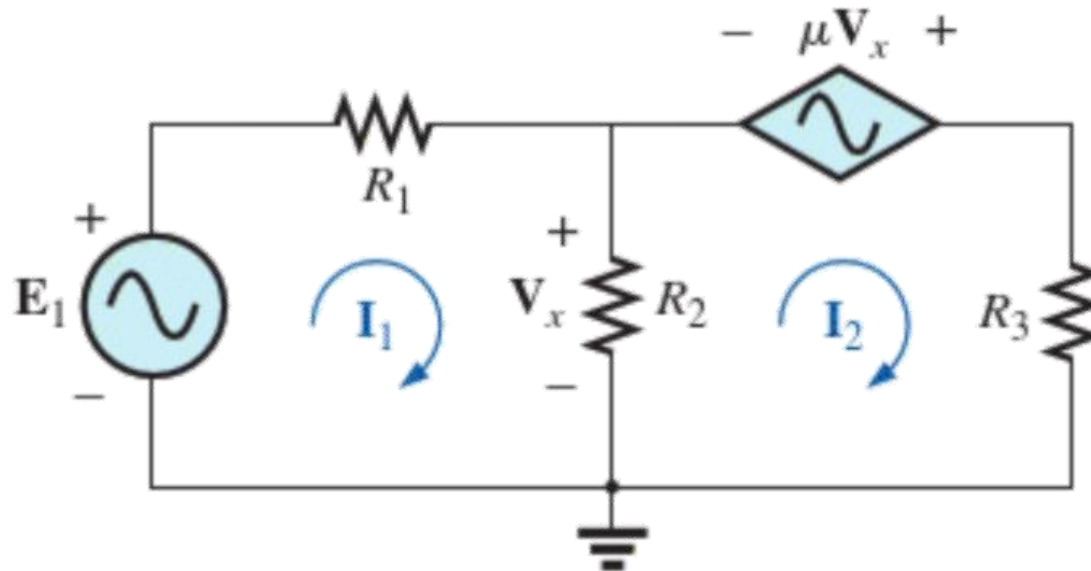


I_1 loop

$$E_1 - R_1 I_1 - R_2 (I_1 - I_2) = 0$$

I_2 loop

$$-R_2 (I_2 - I_1) + \mu R_2 (I_1 - I_2) - R_3 I_2 = 0$$


Supermesh

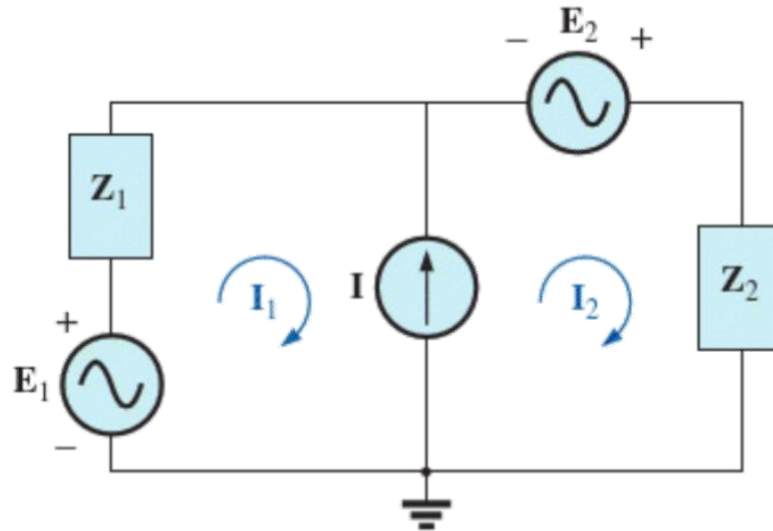

Supermesh: $I_1 + I = I_2$

$$E_1 - Z_1 * I_1 + E_2 - Z_2 * I_2 = 0$$


Supermesh with depended source

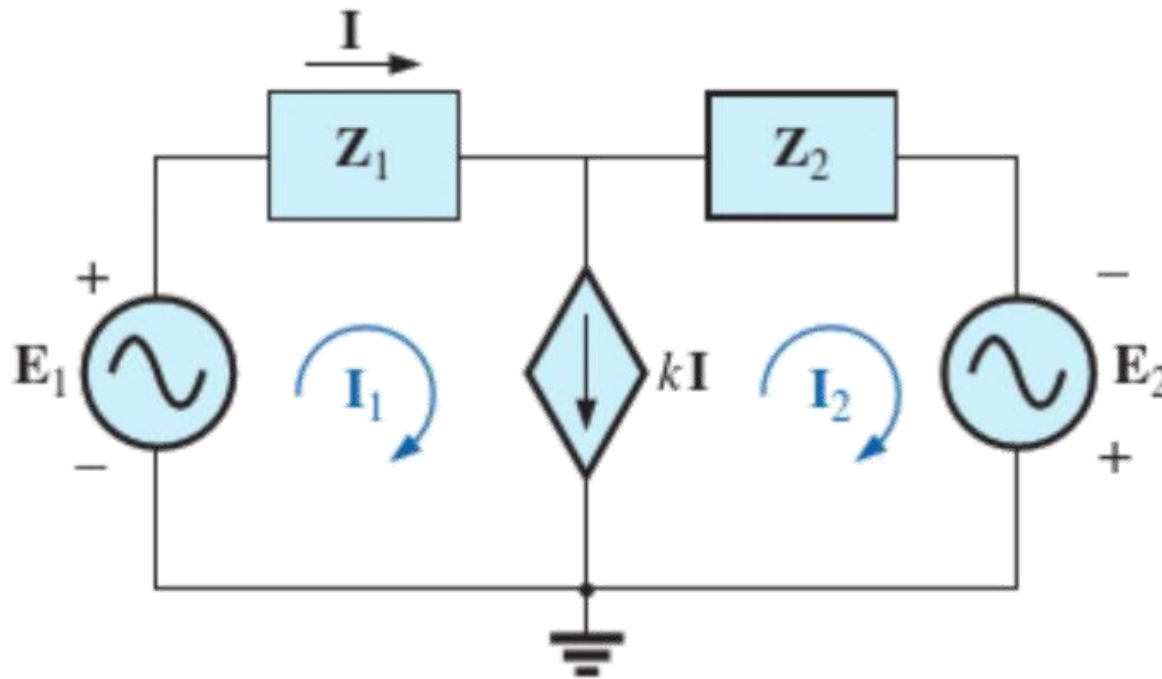

Supermesh: $I_1 - I_2 = kI = kI_1$

$$E_1 - Z_1 * I_1 - Z_2 * I_2 + E_2 = 0$$


Nodal analysis

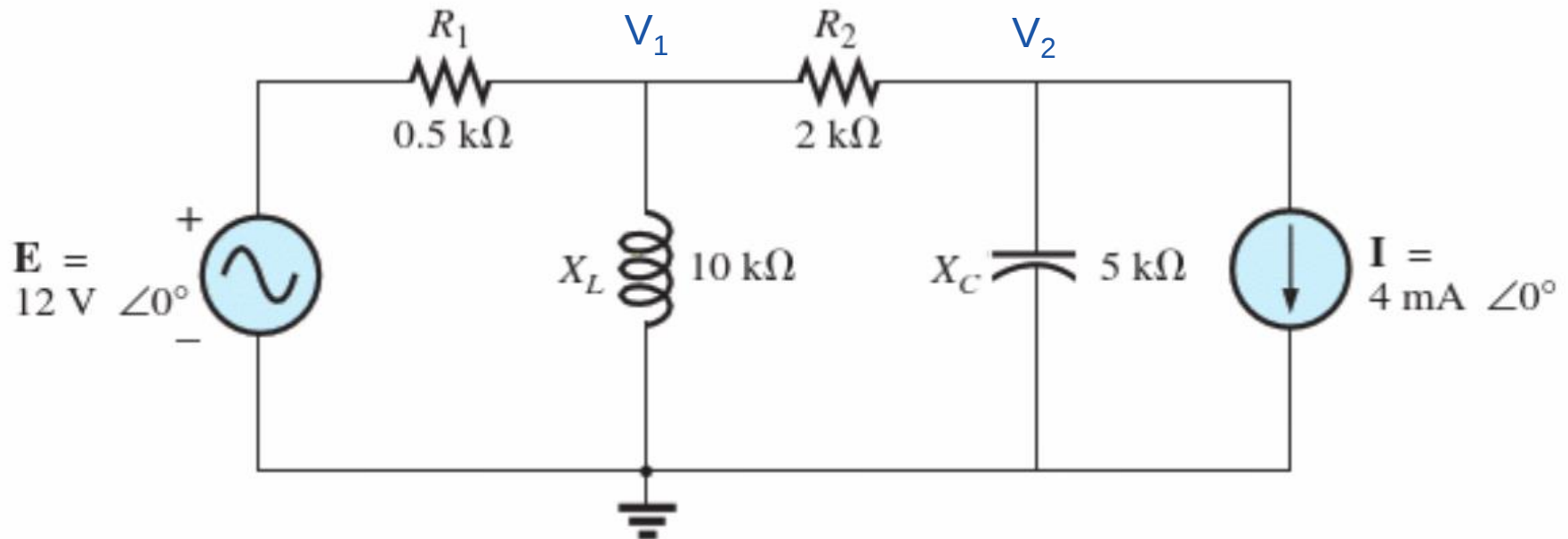

$$-\frac{V_1 - E}{R_1} - \frac{V_1}{Z_L} - \frac{V_1 - V_2}{R_2} = 0$$

$$\frac{V_1 - V_2}{R_2} - \frac{V_2}{Z_C} - I = 0$$


Nodal analysis with depended source

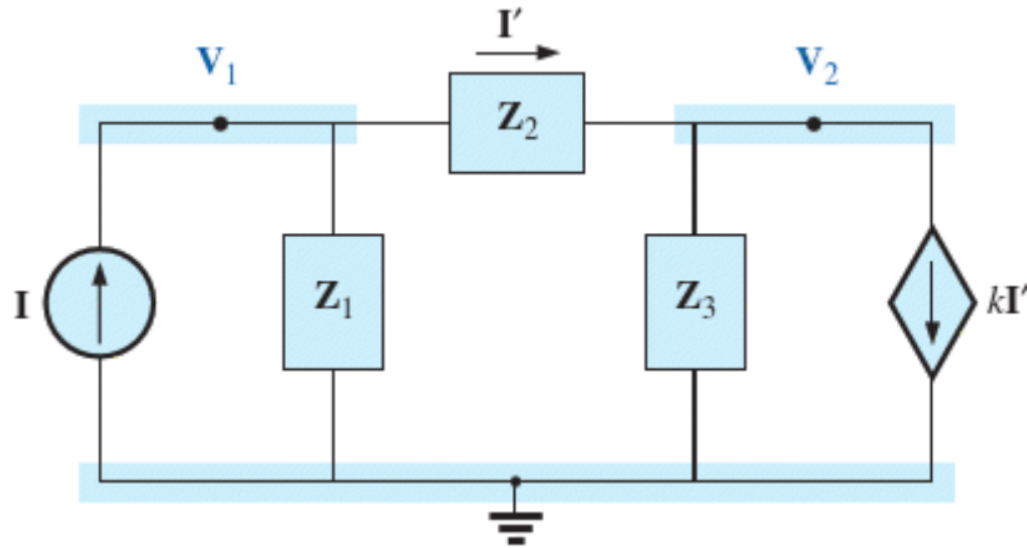

$$I - \frac{V_1}{Z_1} - \frac{V_1 - V_2}{Z_2} = 0$$

$$\frac{V_1 - V_2}{Z_2} - \frac{V_2}{Z_3} - k \frac{V_1 - V_2}{Z_2} = 0$$




Supernode

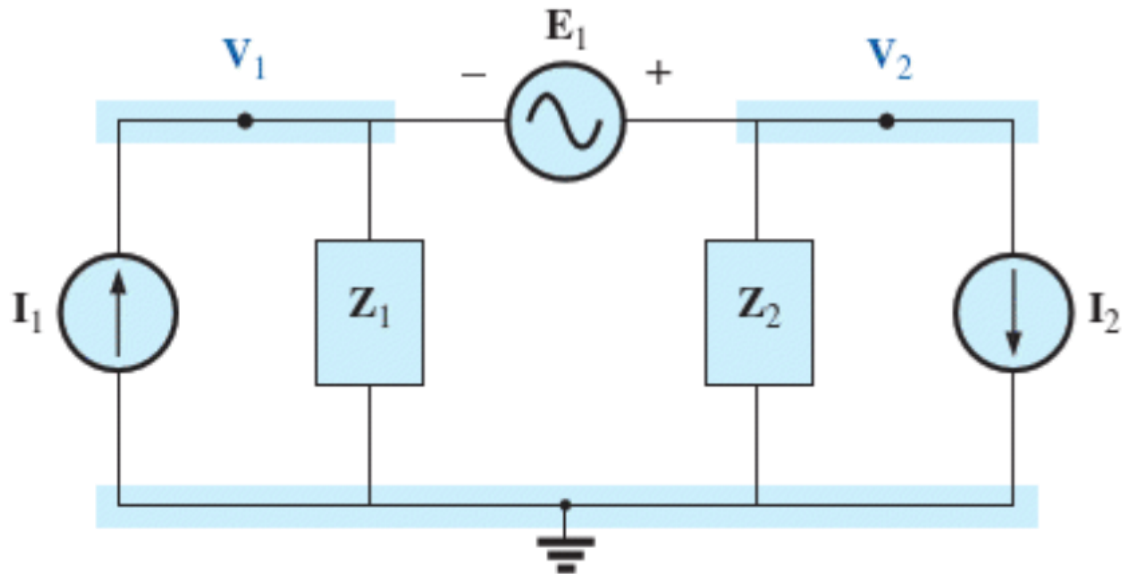

Supernode: $V_2 - V_1 = E_1$


$$I_1 - \frac{V_1}{Z_1} - \frac{V_2}{Z_2} - I_2 = 0$$

Superposition

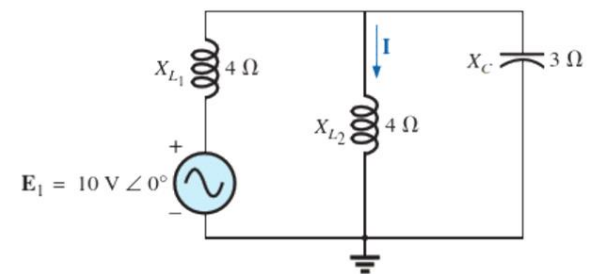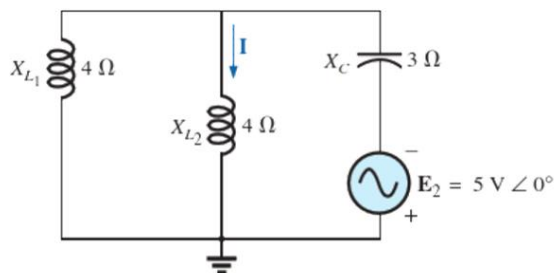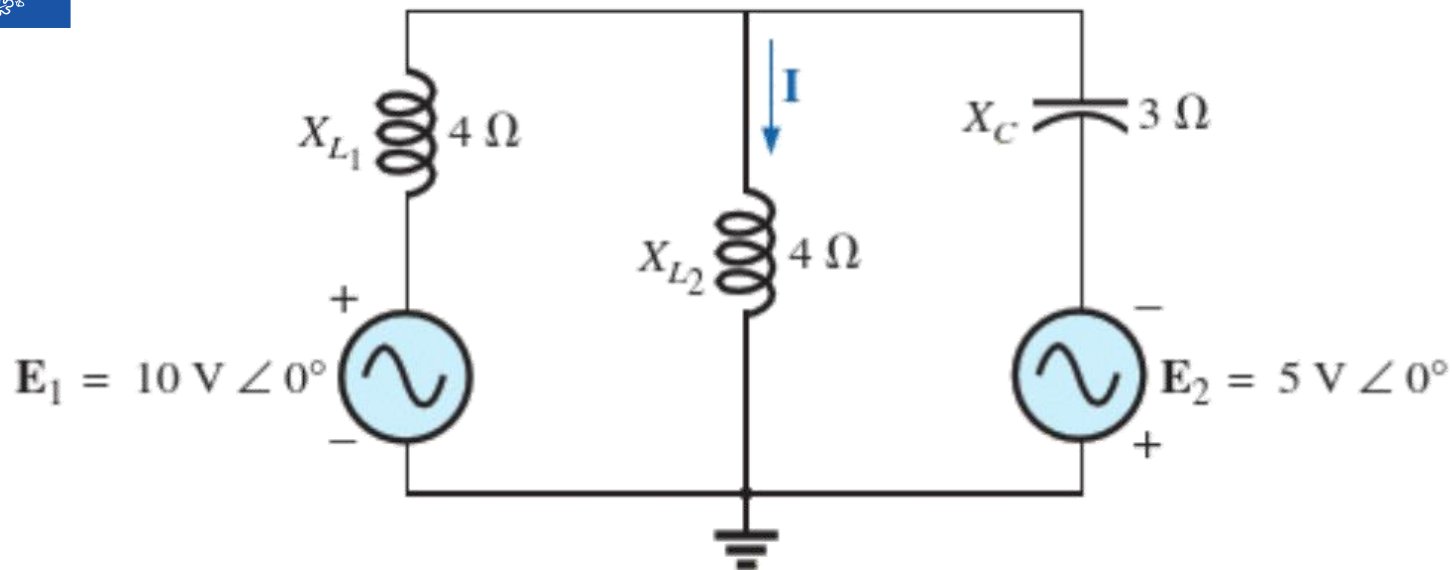


$$I_{Total} = \frac{E_2}{Z_{L1} // Z_{L2} + Z_C}$$

Thevenin Theorem

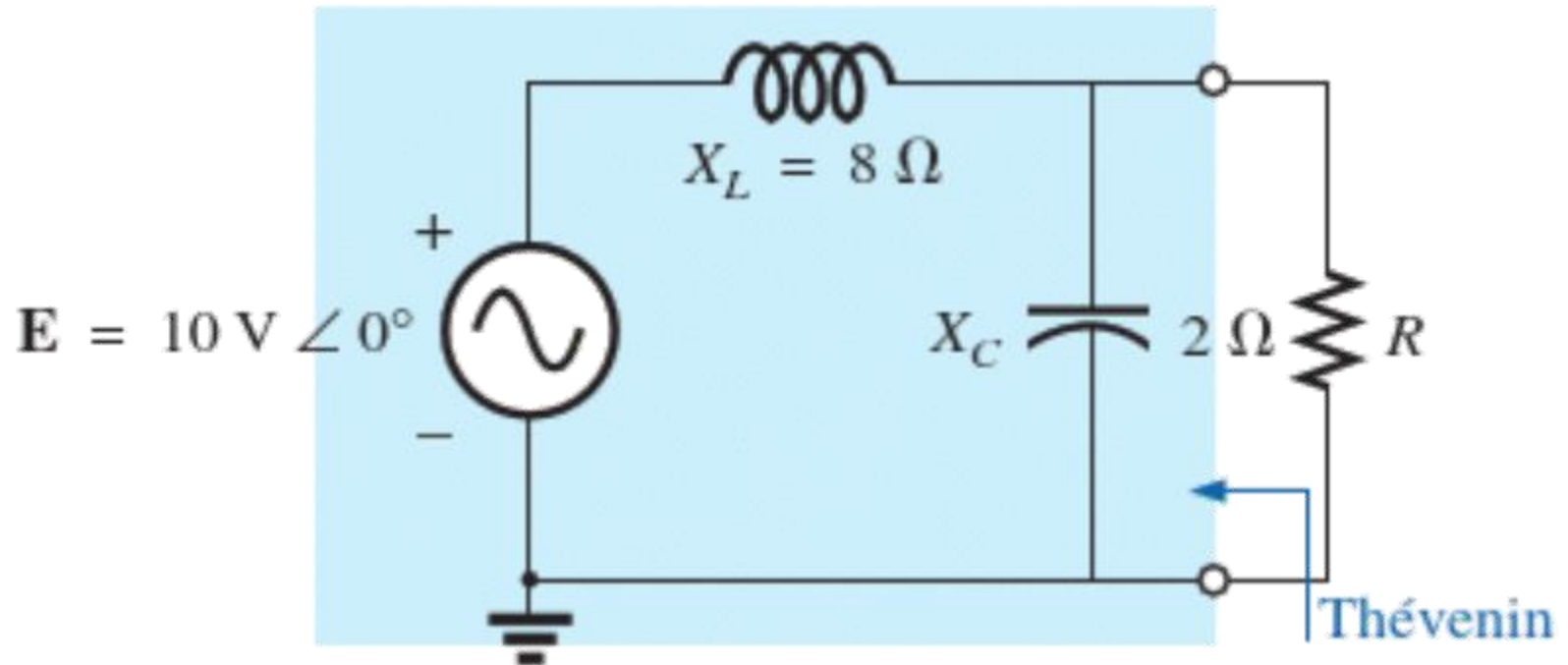


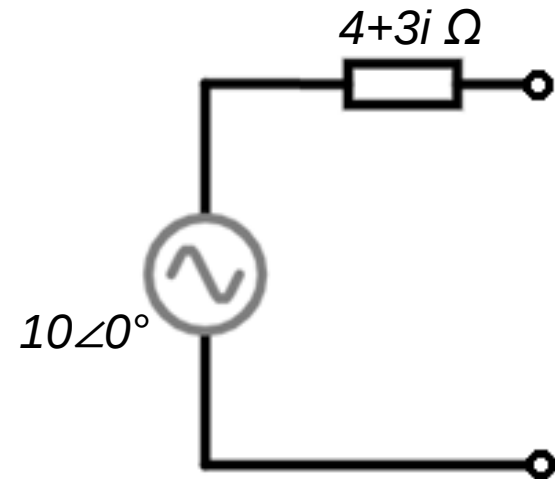Example


Draw a Thevenin equivalent circuit if $E=10\angle 0^\circ$ and $R_{Th}=4+3i\ \Omega$



OR

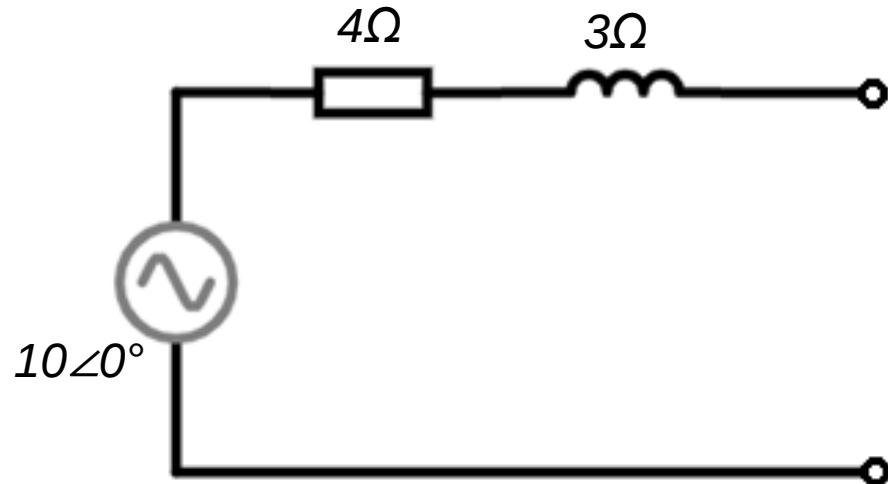

Norton's Theorem

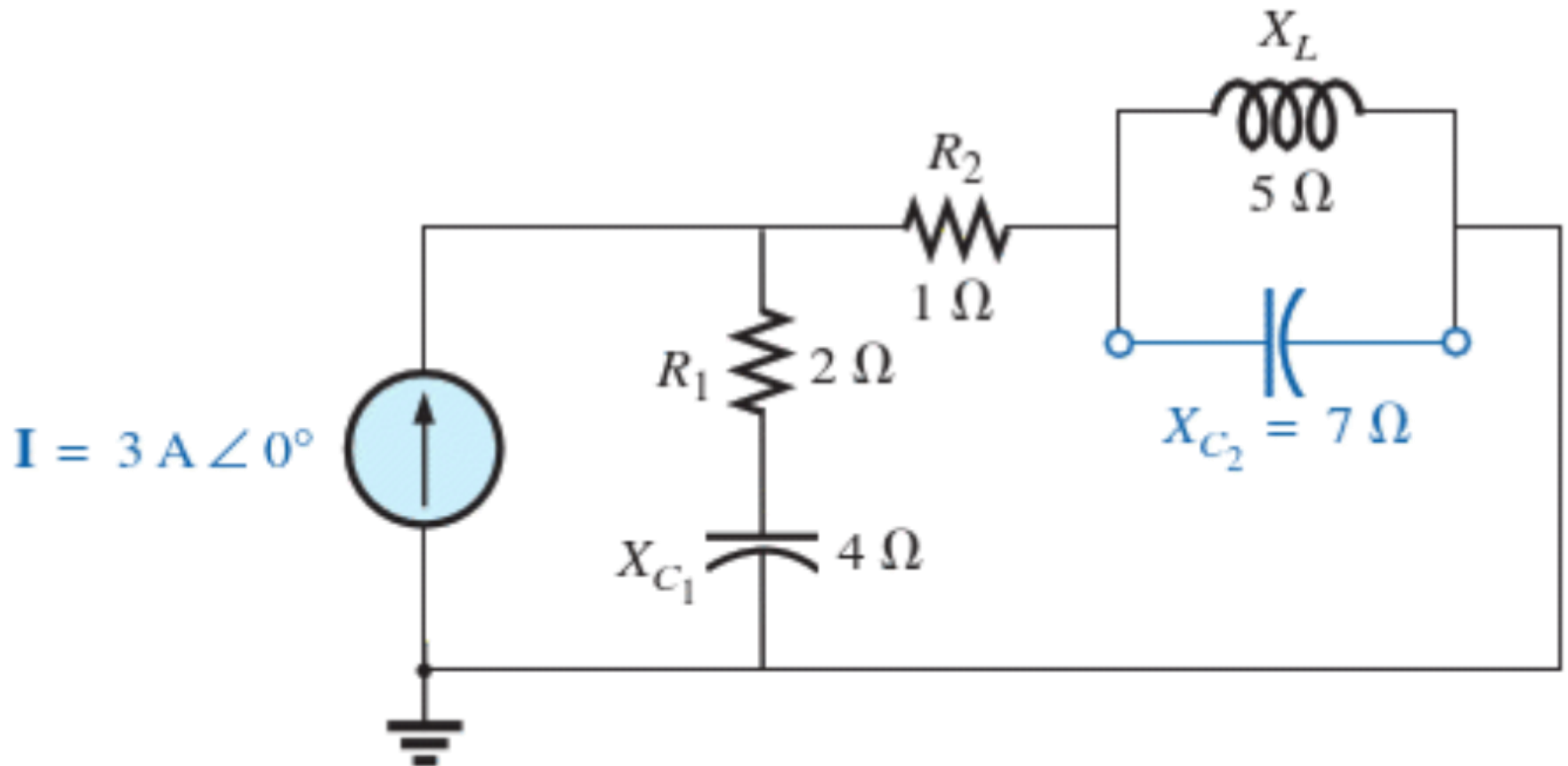



Suggested reading

Introductory Circuit Analysis

- Kap 15: 15.1, **15.2 - 15.4**, 15.5, **15.6 - 15.10**
- Kap 16: **16.1 - 16.8**
- Kap 17: **17.2 - 17.3**
- Kap 18: **18.2 - 18.6**
- Kap 19: **19.2 - 19.5**



Suggested exercises

- Kap 15: 15, 19, 21, 33
 - Kap 16: 9, 12
 - Kap 17: 1, 5, 7
 - Kap 18: 5, 9, 14, 19, 21, 25
 - Kap 19: 1, 7, 13, 15, 17, 27, 35, 43, 47, 49
-